

Digital IC Design

Exercise 0

Design a 64-bit comparator

Professor Po-Tsang Huang

**International College of Semiconductor Technology
National Yang Ming Chiao Tung University**



Exercise

- Design a 64-bit comparator


**If (a==b) out = 1
else out = 0**

- ◆ The driving ability of all the inputs cannot be infinite.
- ◆ Use vector file(pattern_array.vec) for your inputs
- Implement this comparator in static CMOS circuit
 - ◆ Measure the propagation delay
 - ◆ Measure the leakage power

- pattern_array.vec

3

Static CMOS Waveform

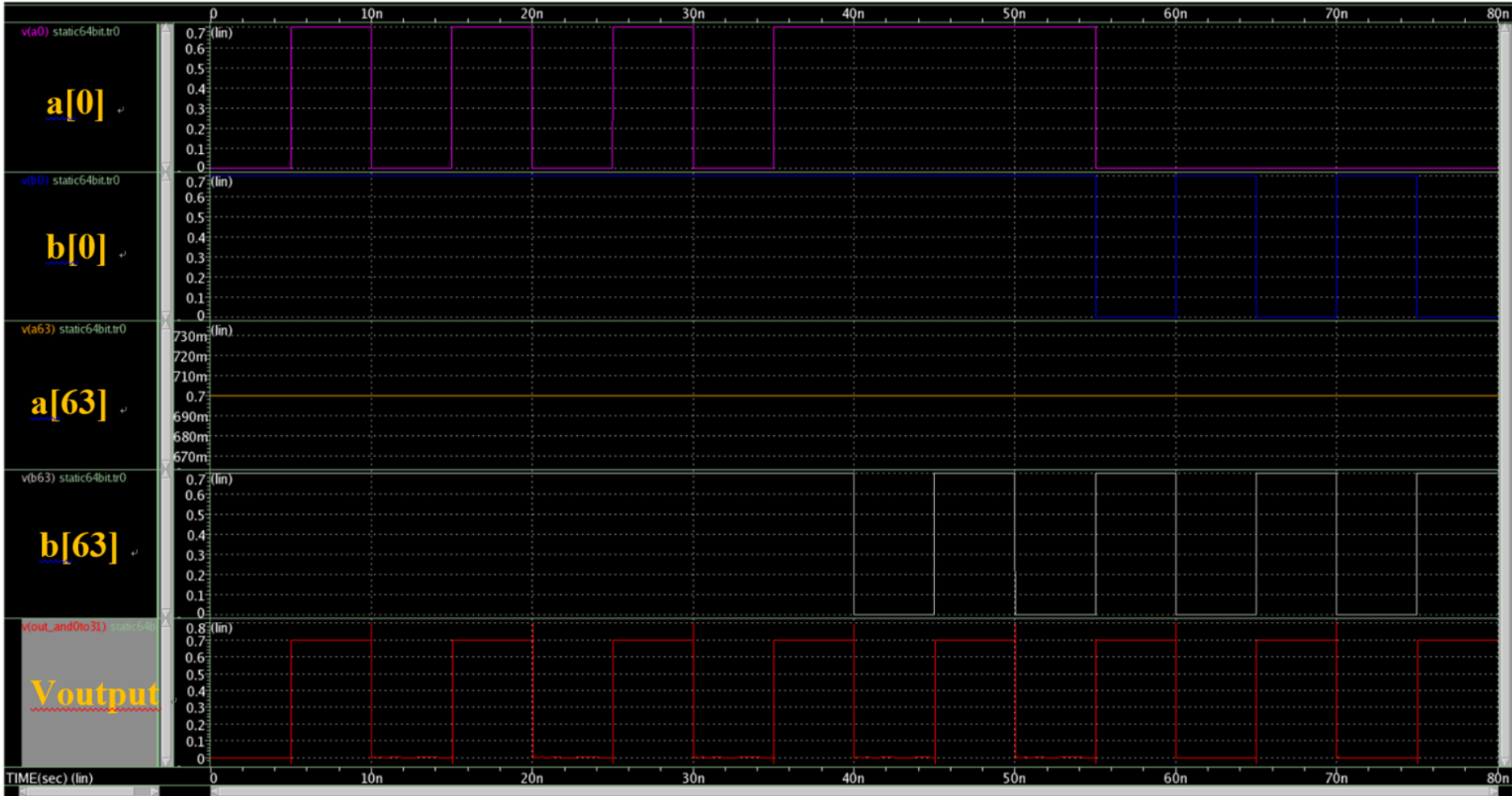

Delay Time and Power

■ .mt0 file

```
1 $DATA1 SOURCE='HSPICE' VERSION='H-2013.03-SP2 32-BIT'
2 .TITLE '.title static cmos 64bit comparator'
3 tphh_a0tooutput    dynamic_pwr    static_pwr    temper
4 alter#
5 2.410e-11          1.976e-04      4.702e-05      25.000
6 1
```

Check function right or false

■ .err0 file

```
***** temperature = 25.000000 *****  
Time          Signal          Simulated          Expected  
=====
```