

# Digital IC Design

## Lec 4-3:

### Combinational Circuits — Dynamic Logic

黃柏蒼 Po-Tsang (Bug) Huang

bughuang@nycu.edu.tw

International College of Semiconductor Technology  
National Chiao Tung Yang Ming University

國立陽明交通大學



NATIONAL YANG MING CHIAO TUNG UNIVERSITY

# Dynamic and Static CMOS

---

- In **static** circuits at every point in time (except when switching) the output is **connected to either  $GND$  or  $V_{DD}$**  via a low resistance path.
  - ◆ fan-in of  $n$  requires  **$2n$**  ( $n$  N-type +  $n$  P-type) devices
- **Dynamic** circuits rely on the **temporary storage** of signal values on the **capacitance** of high impedance nodes.
  - ◆ requires on  $n + 2$  ( $n+1$  N-type + 1 P-type) transistors
  - ◆ takes a sequence of **precharge** and conditional **evaluation** phases to realize logic functions

# Dynamic Gate

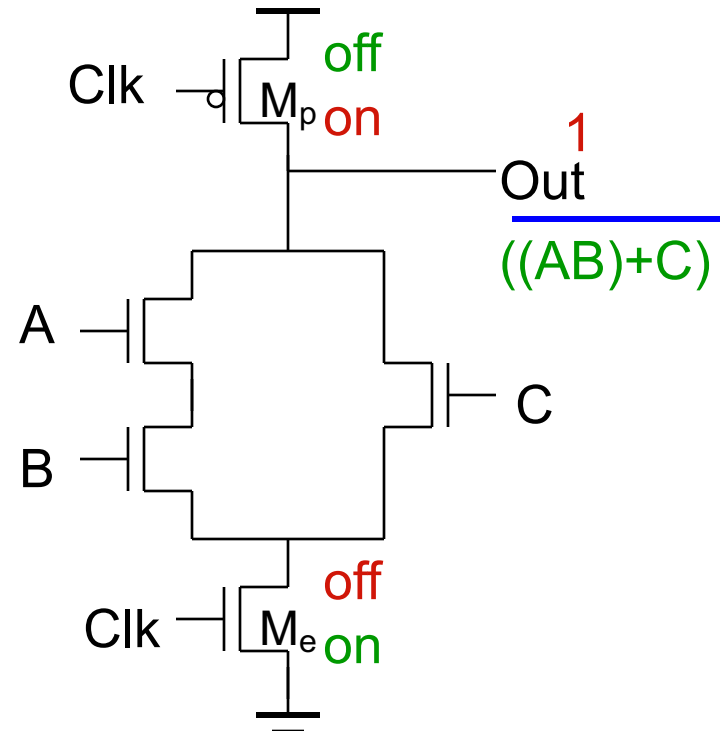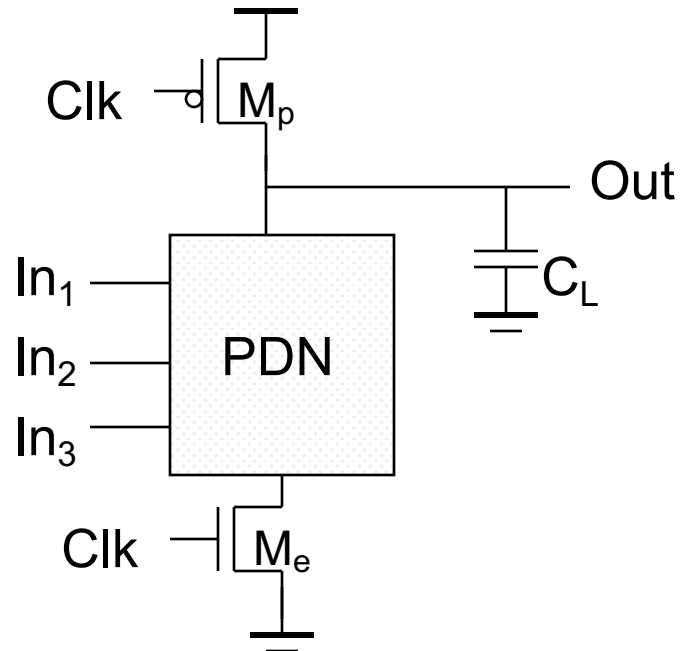

Two phase operation

Precharge (Clk = 0)

Evaluate (Clk = 1)

# Problems of Dynamic Logic

---

- Cascading dynamic logic

- ◆ Domino logic

- Non-inverting logic

- Signal integrity problems

- ◆ Charge leakage

- Add keeper

- ◆ Charge sharing

- Precharge internal node

- ◆ Capacitive coupling

- ◆ Clock feedthrough

# Cascade Dynamic Gates: Monotonicity


■ Dynamic gates require *monotonically rising* inputs during evaluation

◆  $0 \rightarrow 0$

◆  $0 \rightarrow 1$

◆  $1 \rightarrow 1$



◆ But not  $1 \rightarrow 0$

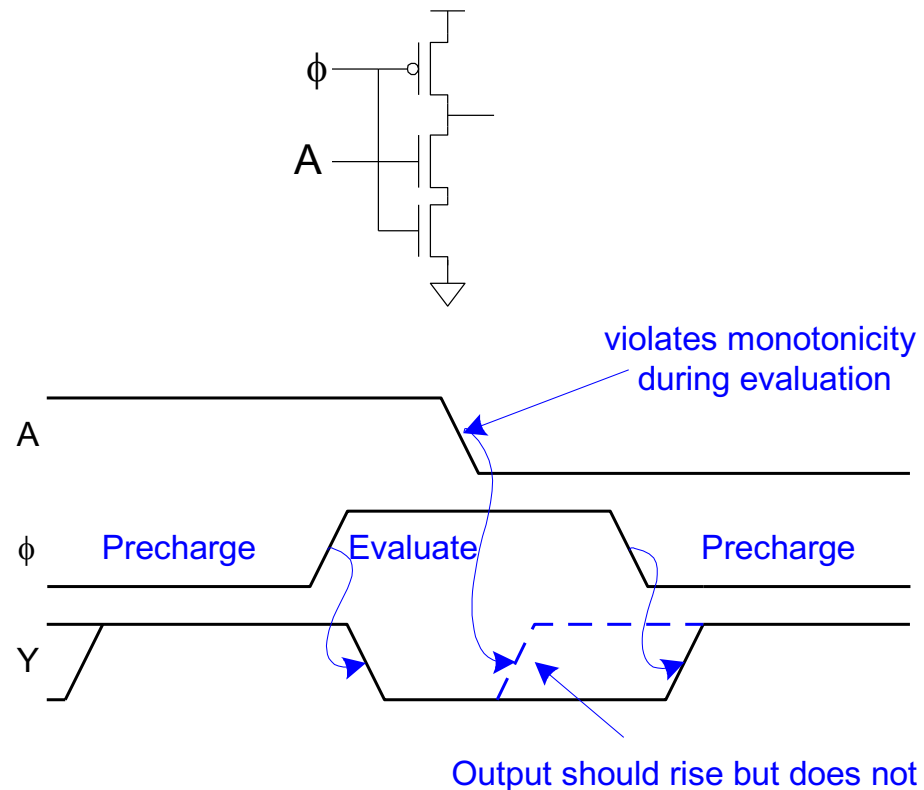

Only  $0 \rightarrow 1$  transitions allowed at inputs!
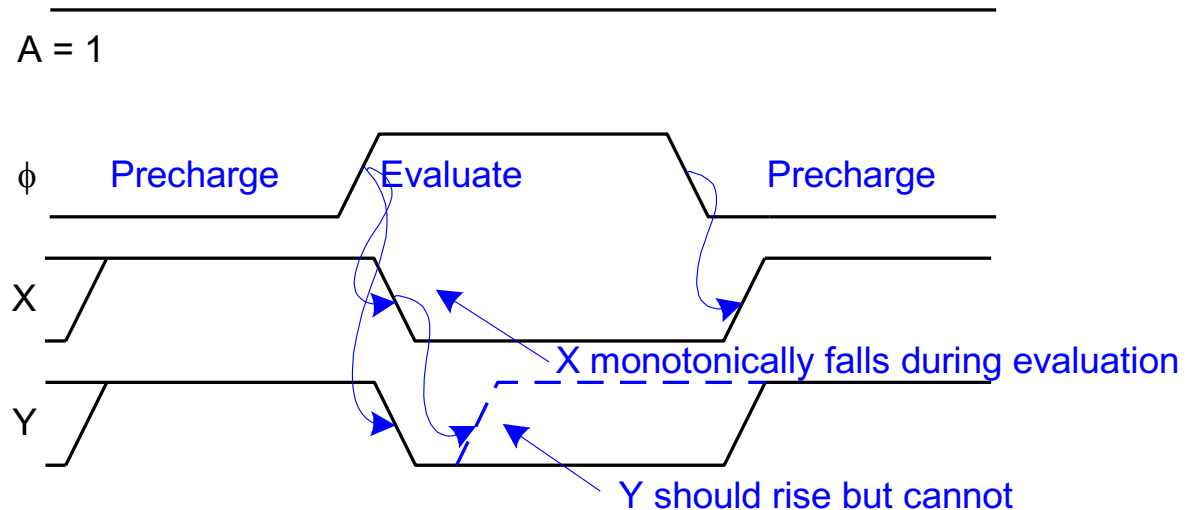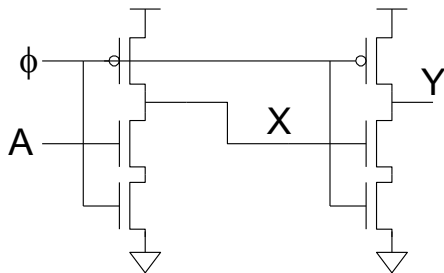
# Monotonicity Problem

- But dynamic gates produce monotonically falling outputs during evaluation
- **Illegal for one dynamic gate to drive another!**




# Conditions on Output

---

- Once the output of a dynamic gate is discharged, it cannot be charged again until the next precharge operation.
- ◆ Inputs to the gate can make *at most one transition* during evaluation.
- ◆ This could be a problem when you cascade the dynamic logic
  - Extra transition will destroy the logic
- Output can be in the high impedance state during and after evaluation (PDN off), state is stored on  $C_L$

# np-CMOS (Zipper)

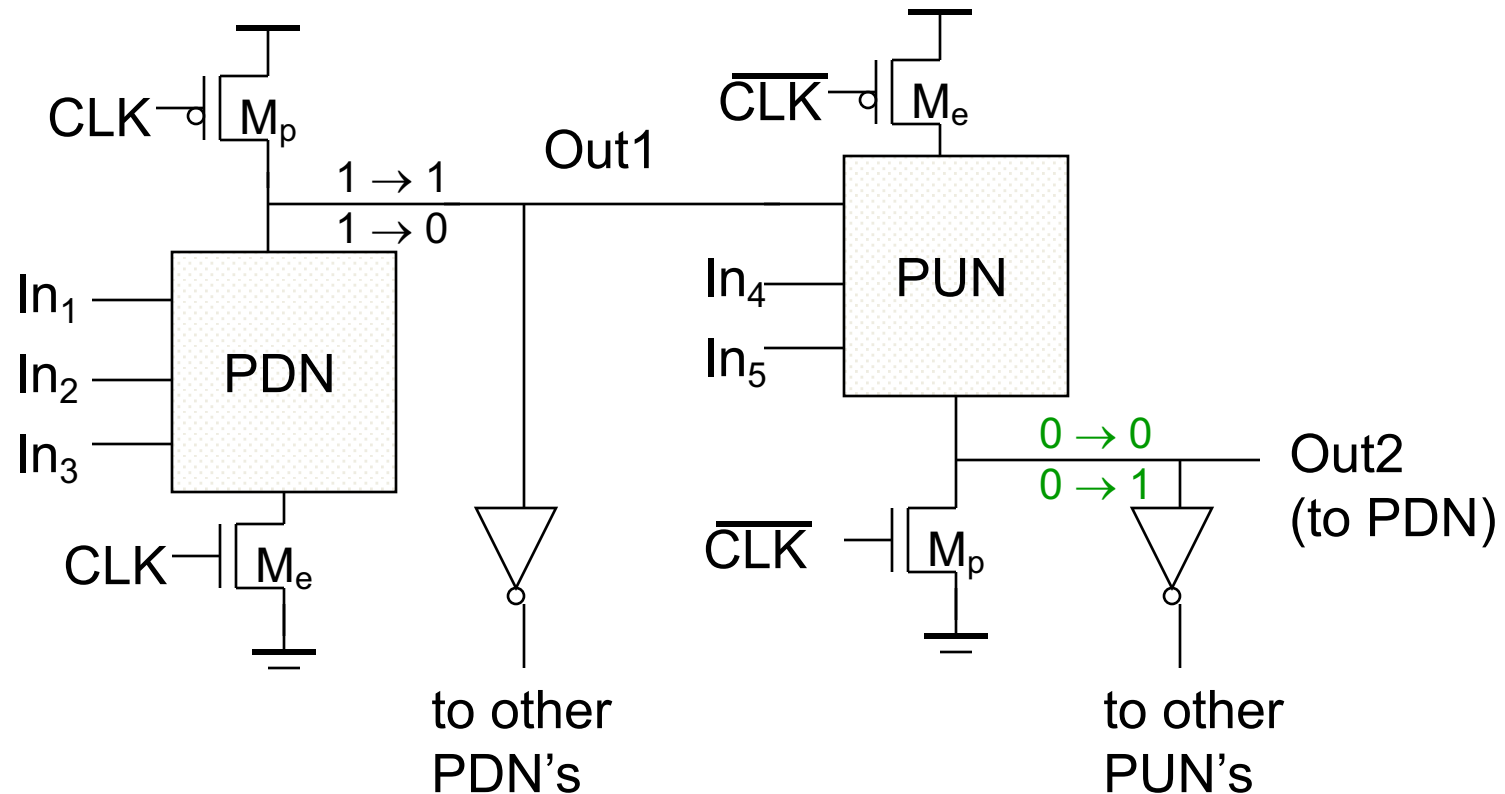


Only  $0 \rightarrow 1$  transitions allowed at inputs of PDN


Only  $1 \rightarrow 0$  transitions allowed at inputs of PUN




# np-CMOS Adder Circuit

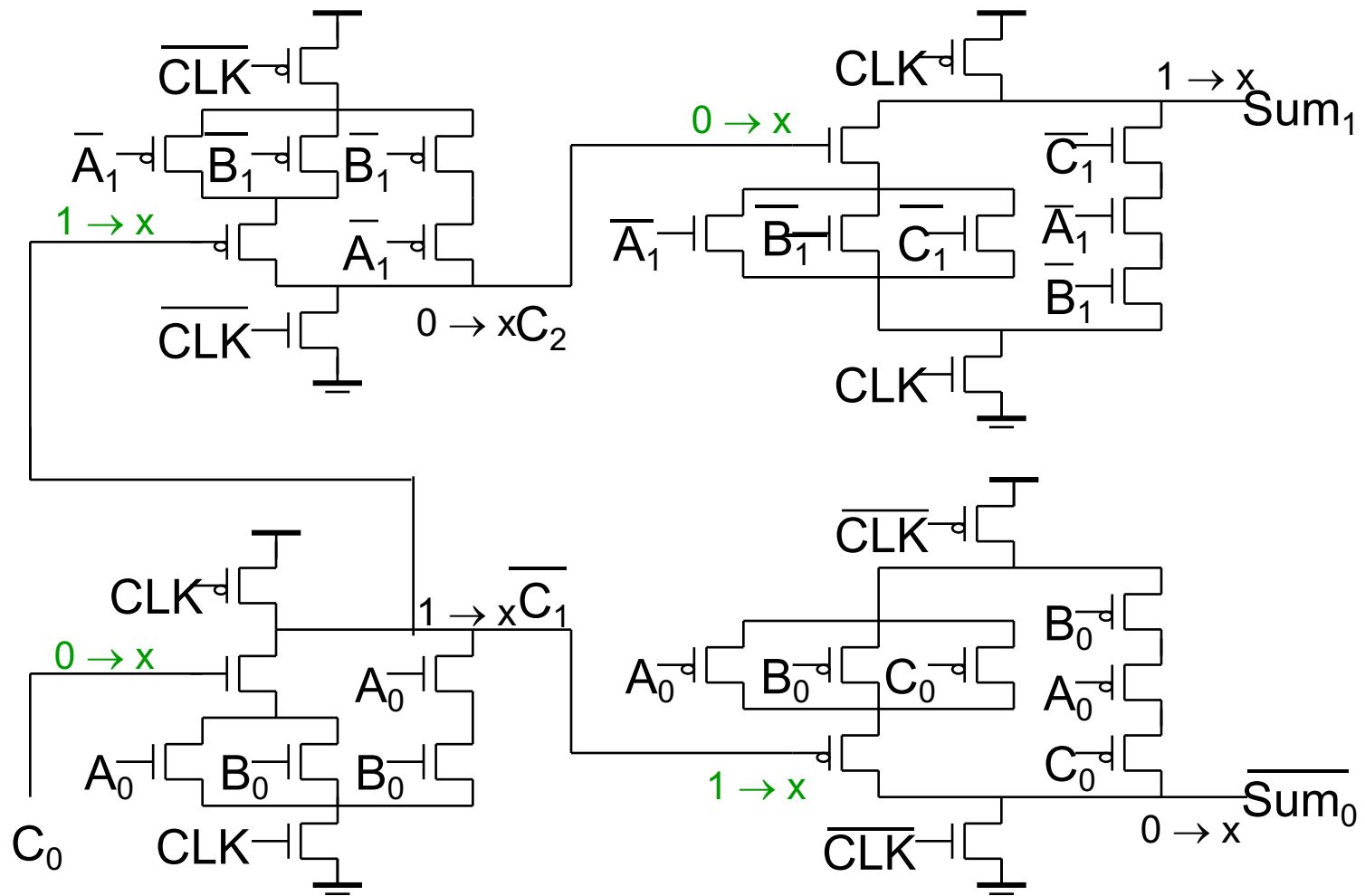

# Solution: Domino Logic

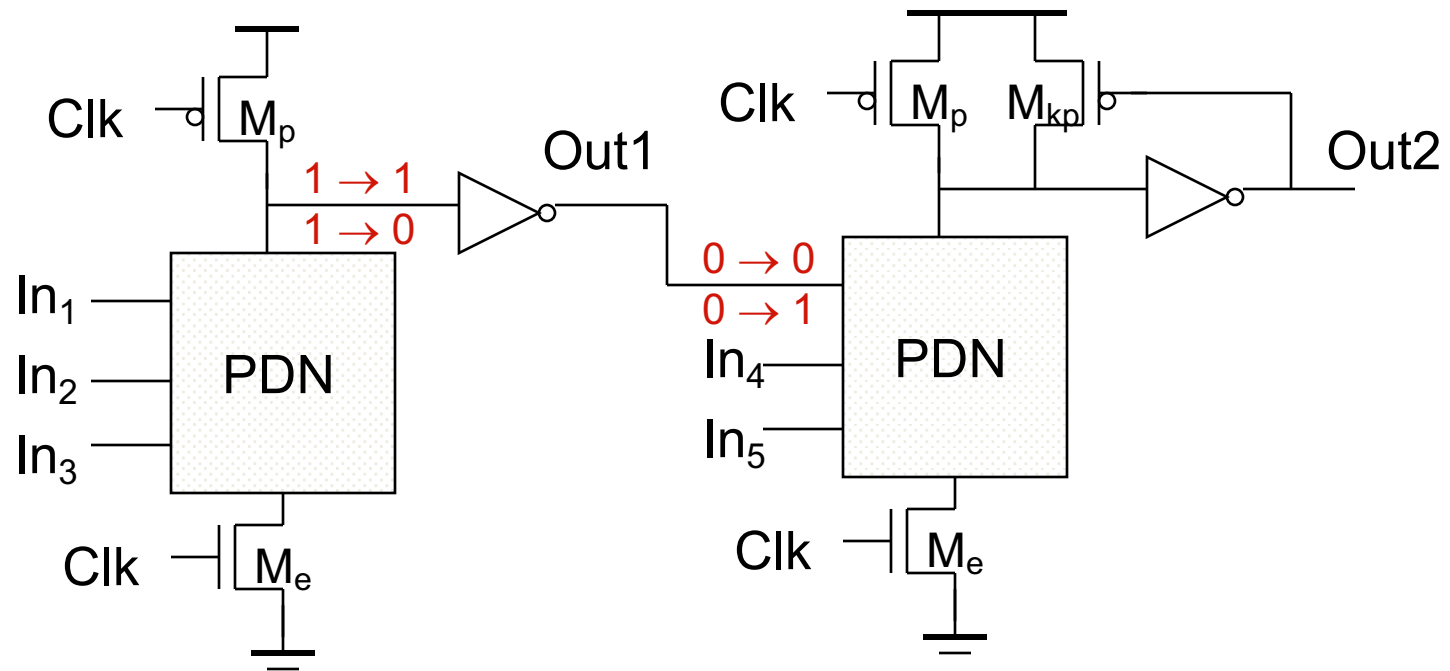

# Why Domino?

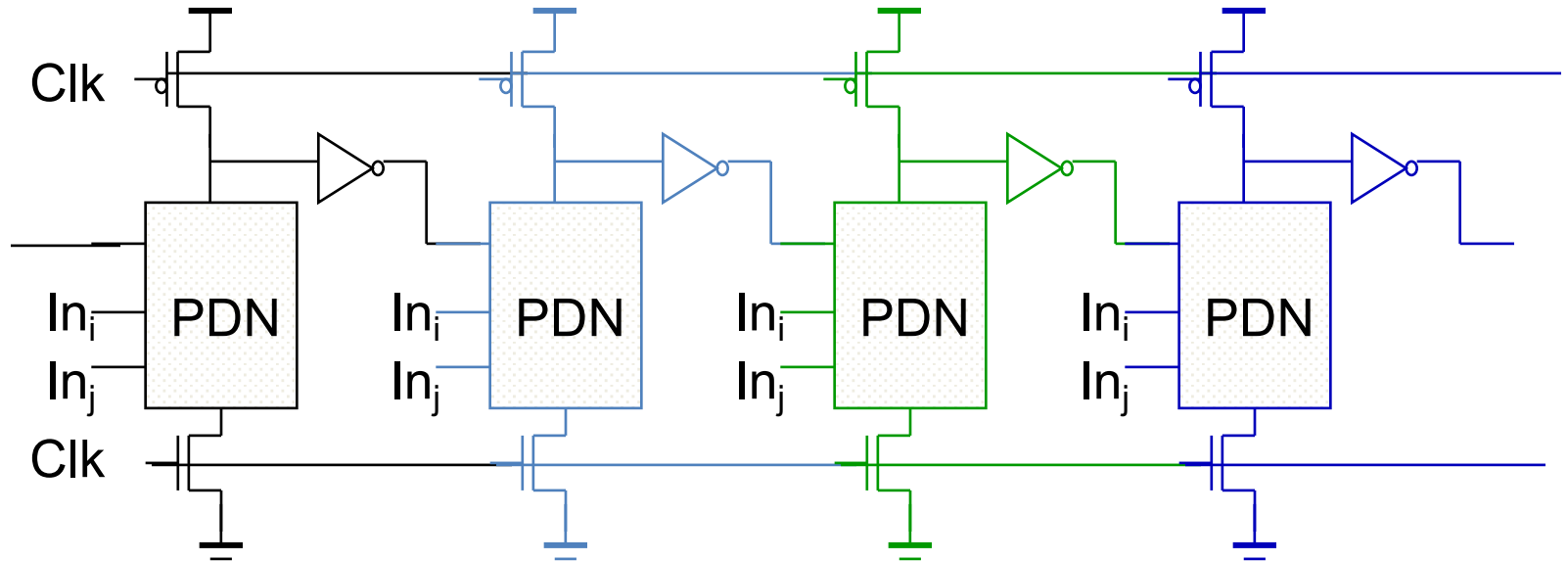

Like falling dominos!




# Properties of Domino Logic

---

- Only **non-inverting** logic can be implemented for dynamic circuits, fixes include
  - ◆ can reorganize the logic using Boolean transformations
  - ◆ use differential logic (dual rail)
  - ◆ use np-CMOS (zipper)
- Very high speed
  - ◆  $t_{pHL} = 0$
  - ◆ static inverter can be optimized to match fan-out (separation of fan-in and fan-out capacitances)

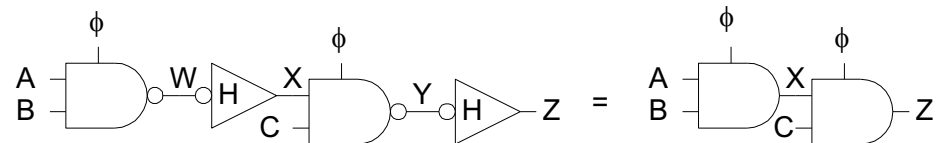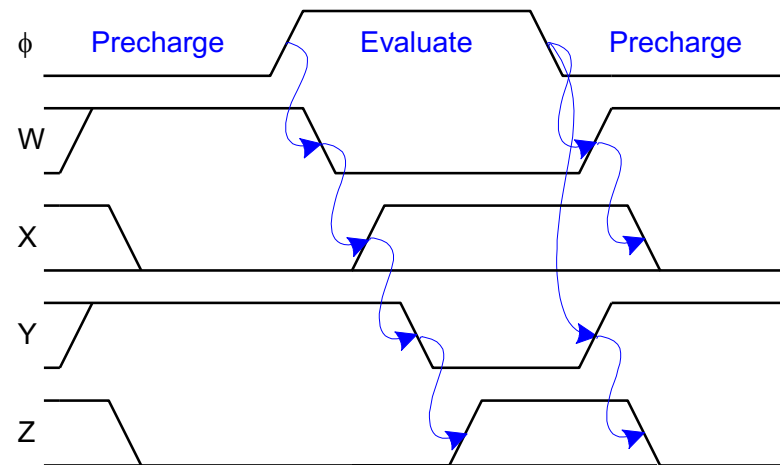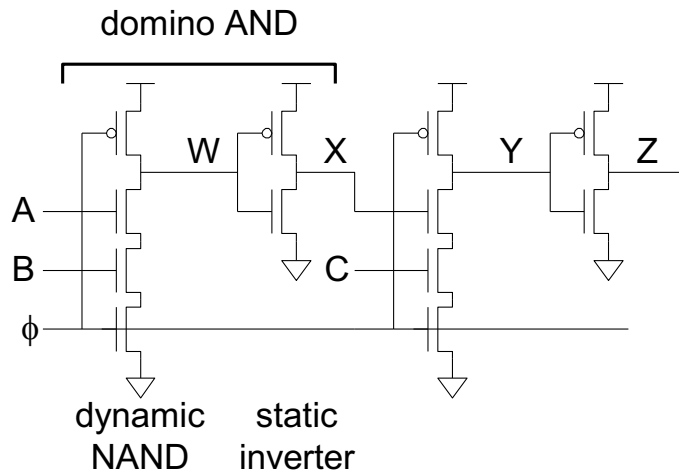
# Domino Gates

- Follow dynamic stage with inverting static gate
  - ◆ Dynamic / static pair is called domino gate
  - ◆ Produces monotonic outputs



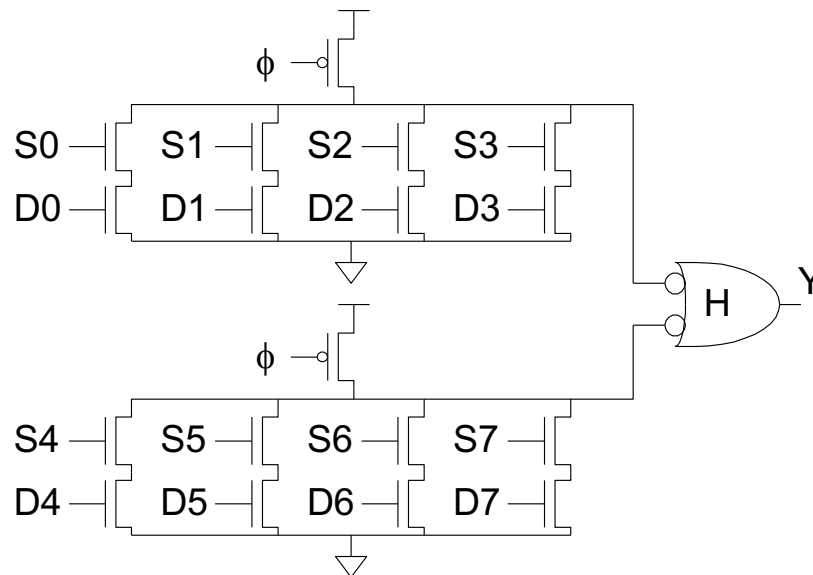
# Domino Optimizations

- Each domino gate triggers next one, like a string of dominos toppling over
- Gates evaluate sequentially but precharge in parallel
- Thus evaluation is more critical than precharge
- HI-skewed static stages can perform logic




# Domino Zero Detector

## ■ Large Fan-in circuits

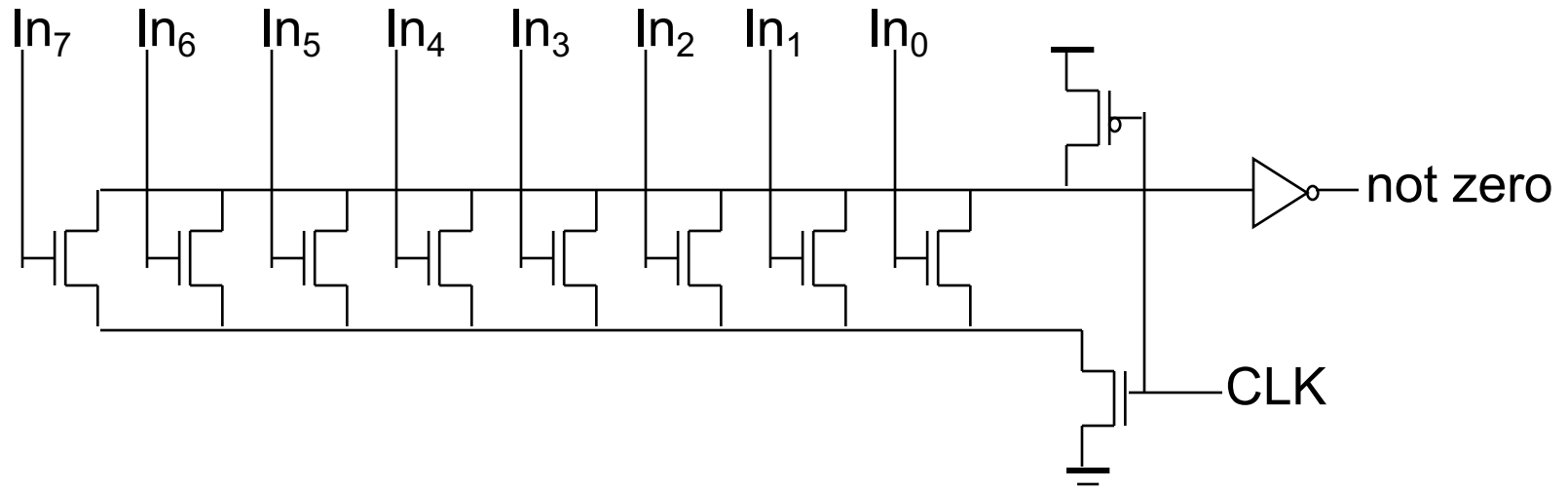

# Domino Comparator

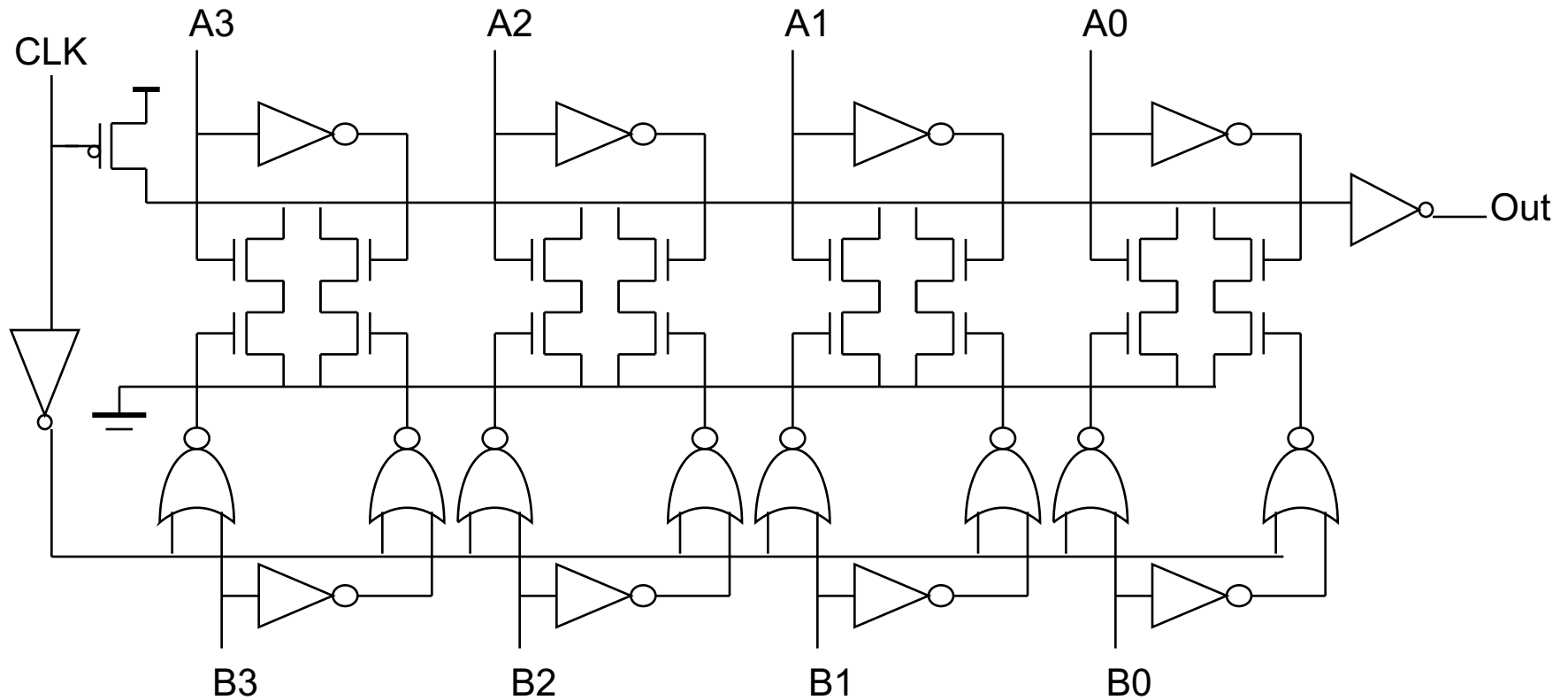



# Properties of Domino Logic


---

- Only non-inverting logic can be implemented, fixes include
  - ◆ can reorganize the logic using Boolean transformations
  - ◆ use differential logic (dual rail)
  - ◆ use np-CMOS (zipper)
  
- Very high speed
  - ◆  $t_{pHL} = 0$
  - ◆ static inverter can be optimized to match fan-out (separation of fan-in and fan-out capacitances)

# Dual-Rail Domino


- Domino only performs noninverting functions:
  - ◆ AND, OR but not NAND, NOR, or XOR
- Dual-rail domino solves this problem
  - ◆ Takes true and complementary inputs
  - ◆ Produces true and complementary outputs

sig_h	sig_l	Meaning
0	0	Precharged
0	1	'0'
1	0	'1'
1	1	invalid

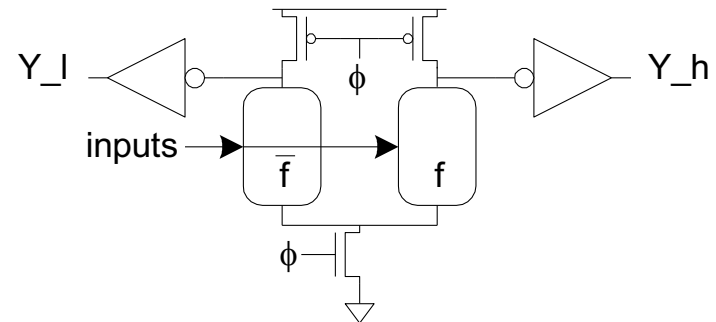

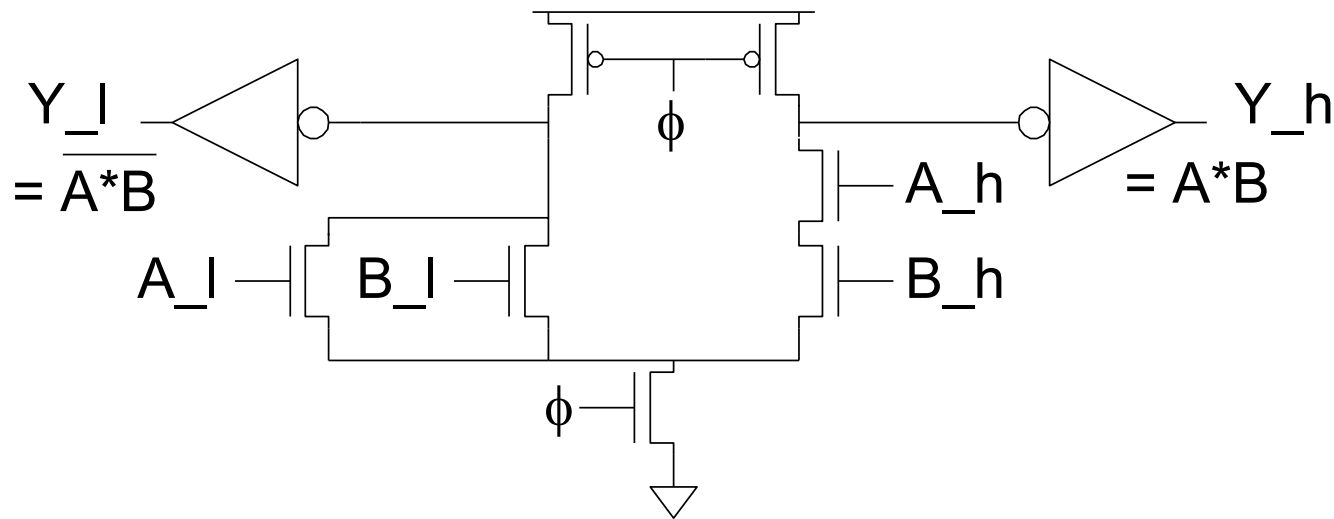
# Example: AND/NAND

- Given  $A_h, A_l, B_h, B_l$
- Compute  $Y_h = AB, Y_l = \overline{AB}$
- Pulldown networks are conduction complements



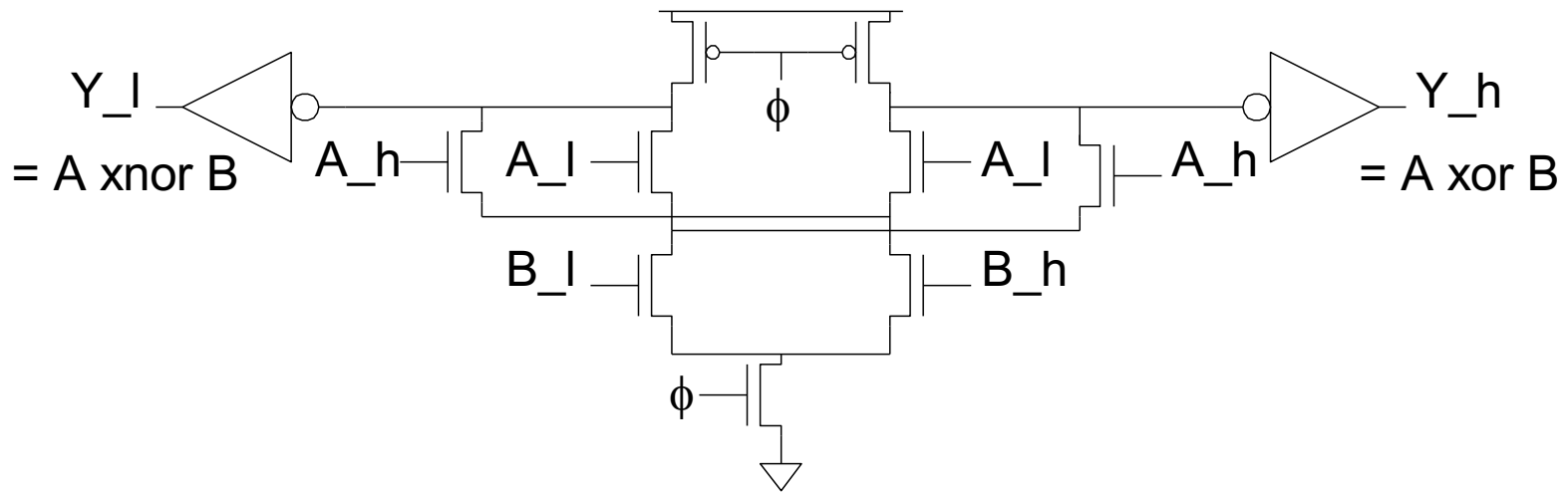
# Example: XOR/XNOR

- Sometimes possible to share transistors




# Differential (Dual Rail) Domino

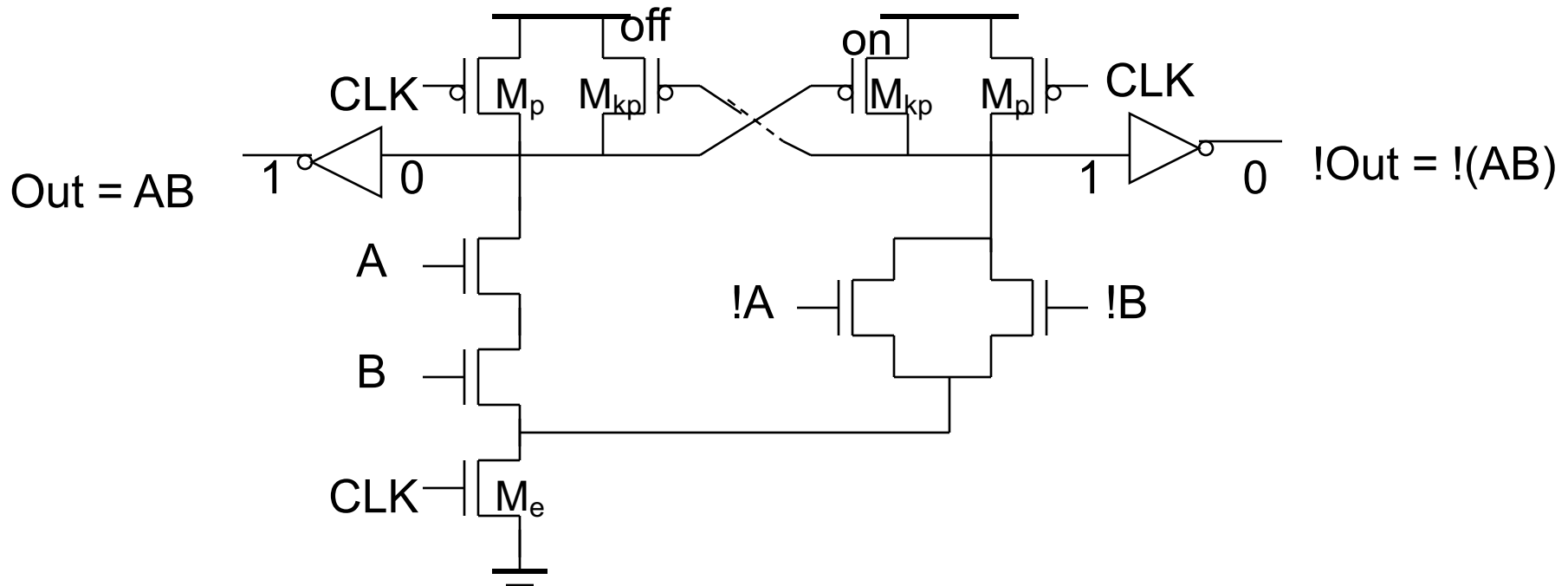

Due to its high-performance, differential domino is very popular and is used in several commercial microprocessors!
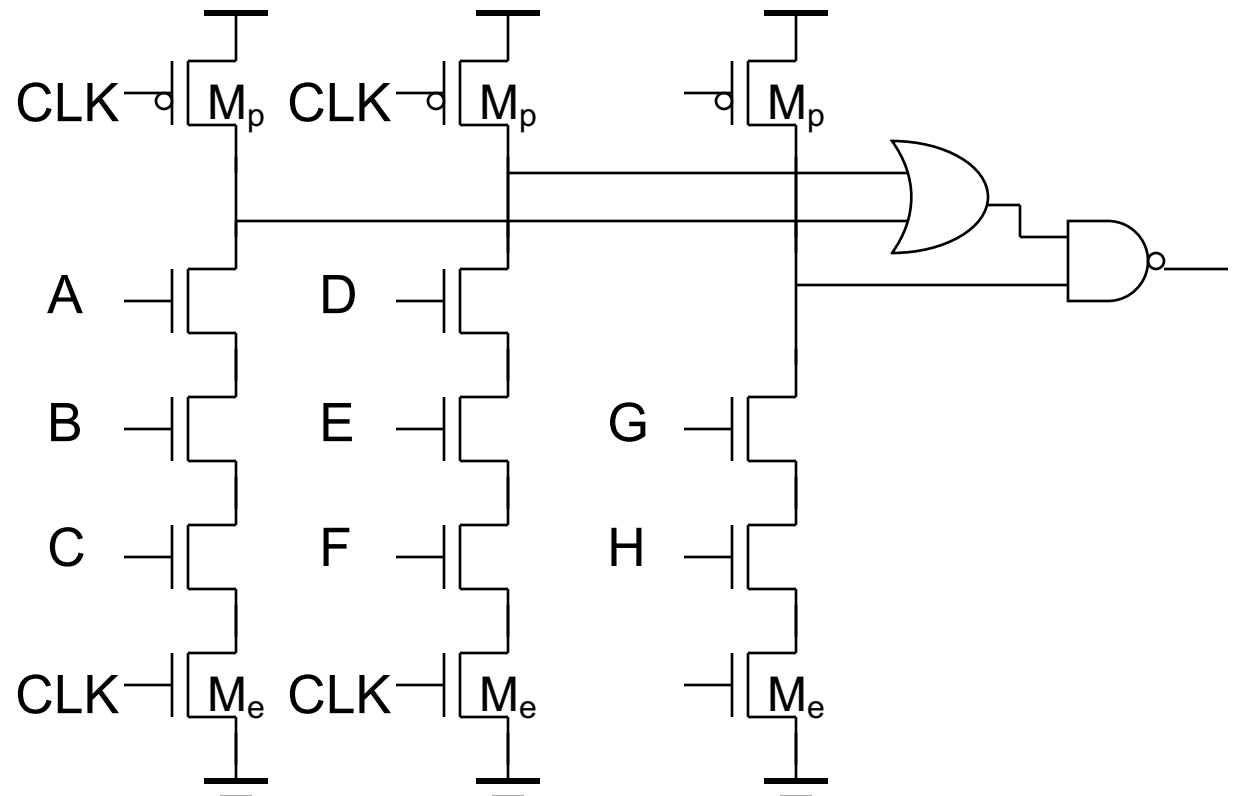
# Other Domino Variations

- Multiple output domino logic – exploits the fact that certain outputs are subsets of other outputs to generate a number of logic functions in a single gate.
- Compound domino




# Domino Summary

---


- Domino logic is attractive for high-speed circuits
  - ◆ 1.3 – 2x faster than static CMOS
  - ◆ But many challenges:
    - Monotonicity, leakage, charge sharing, noise
- Widely used in high-performance microprocessors in 1990s when speed was king
- Largely displaced by static CMOS now that power is the limiter
- Still used in memories for area efficiency
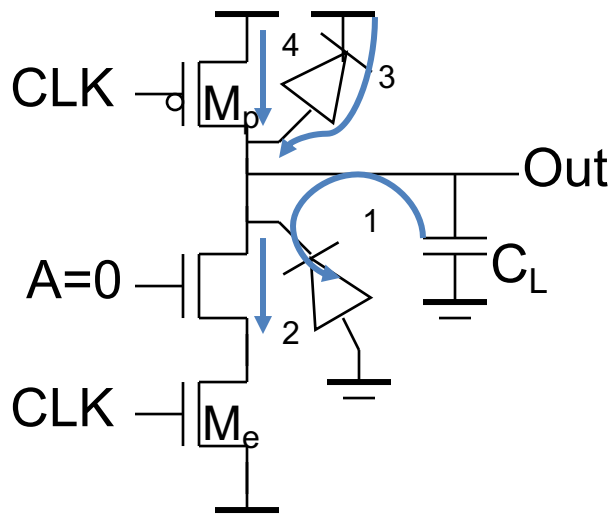
# Impact of Charge Leakage

- Output settles to an intermediate voltage determined by a resistive divider of the pull-up and pull-down networks
- ◆ Once the output drops below the switching threshold of the fan-out logic gate, the output is interpreted as a low voltage.



Leakage sources

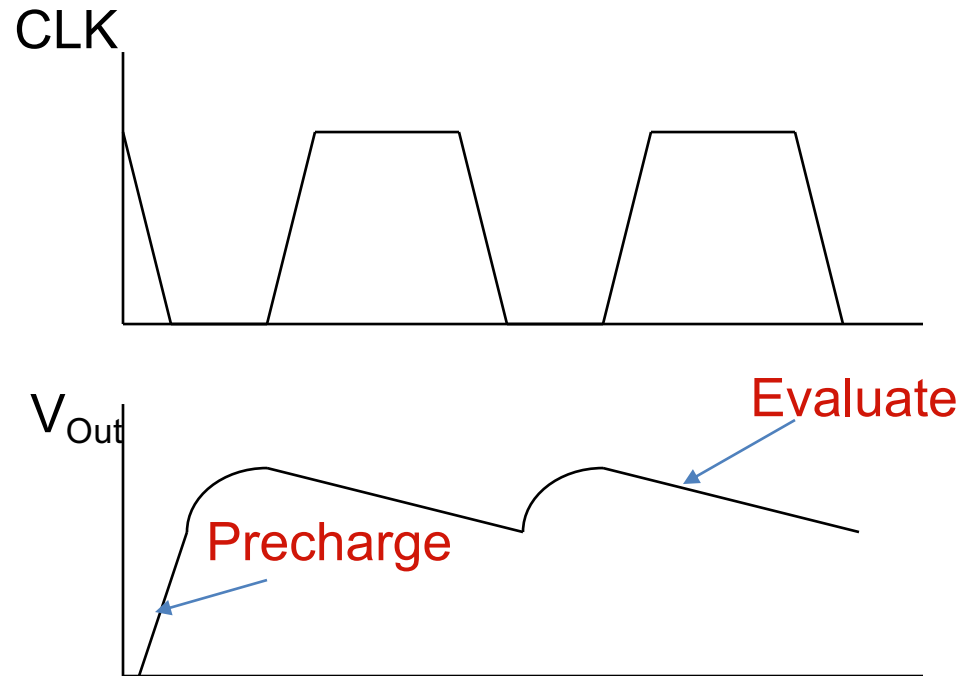


Minimum clock rate!!!


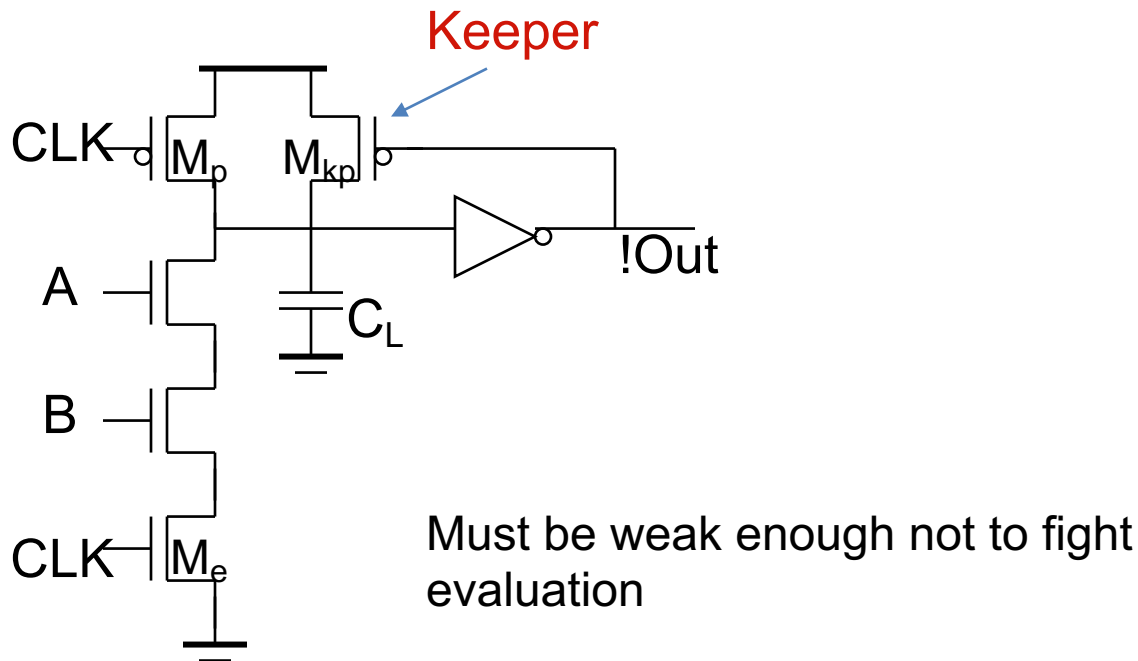
# A Solution to Charge Leakage



- ❑ **Keeper** compensates for the charge lost due to the pull-down leakage paths.



Same approach as level restorer for pass transistor logic

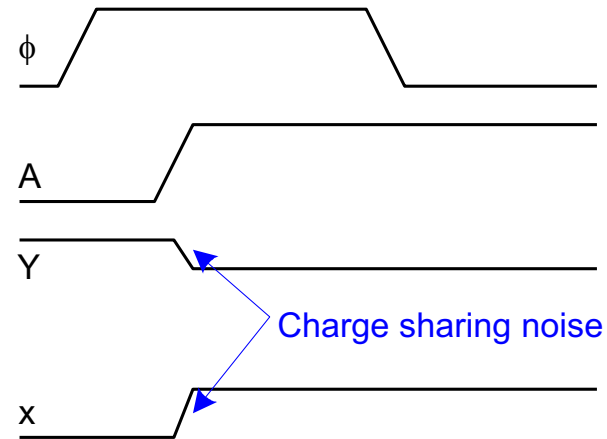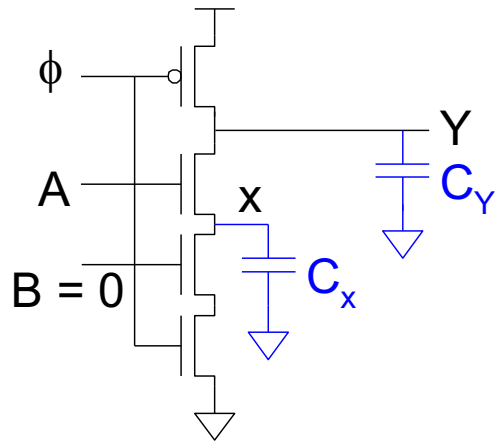
# Charge Sharing

- Dynamic gates suffer from charge sharing



$$V_x = V_Y =$$

# Malfunction of Charge sharing

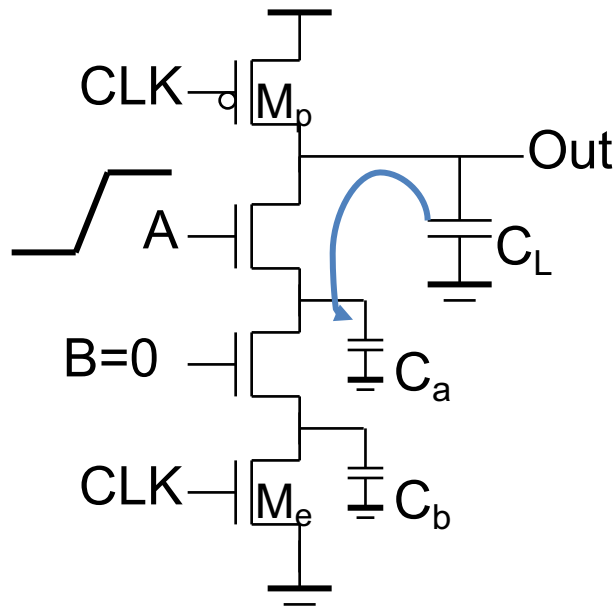


Charge stored originally on  $C_L$  is redistributed (shared) over  $C_L$  and  $C_A$  leading to static power consumption by downstream gates and possible circuit malfunction.

When  $\Delta V_{out} = -V_{DD} (C_a / (C_a + C_L))$  the drop in  $V_{out}$  is large enough to be below the switching threshold of the gate it drives causing a malfunction.
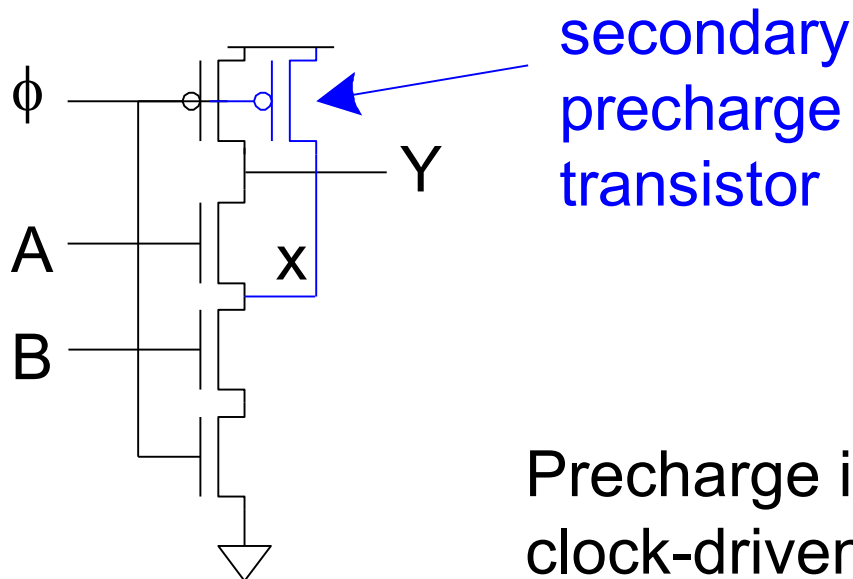
# Solution to Charge Redistribution


- Solution: add secondary precharge transistors
  - ◆ Typically need to precharge every other node
- Big load capacitance  $C_Y$  helps as well



Precharge internal nodes using a clock-driven transistor (at the cost of increased area and power)
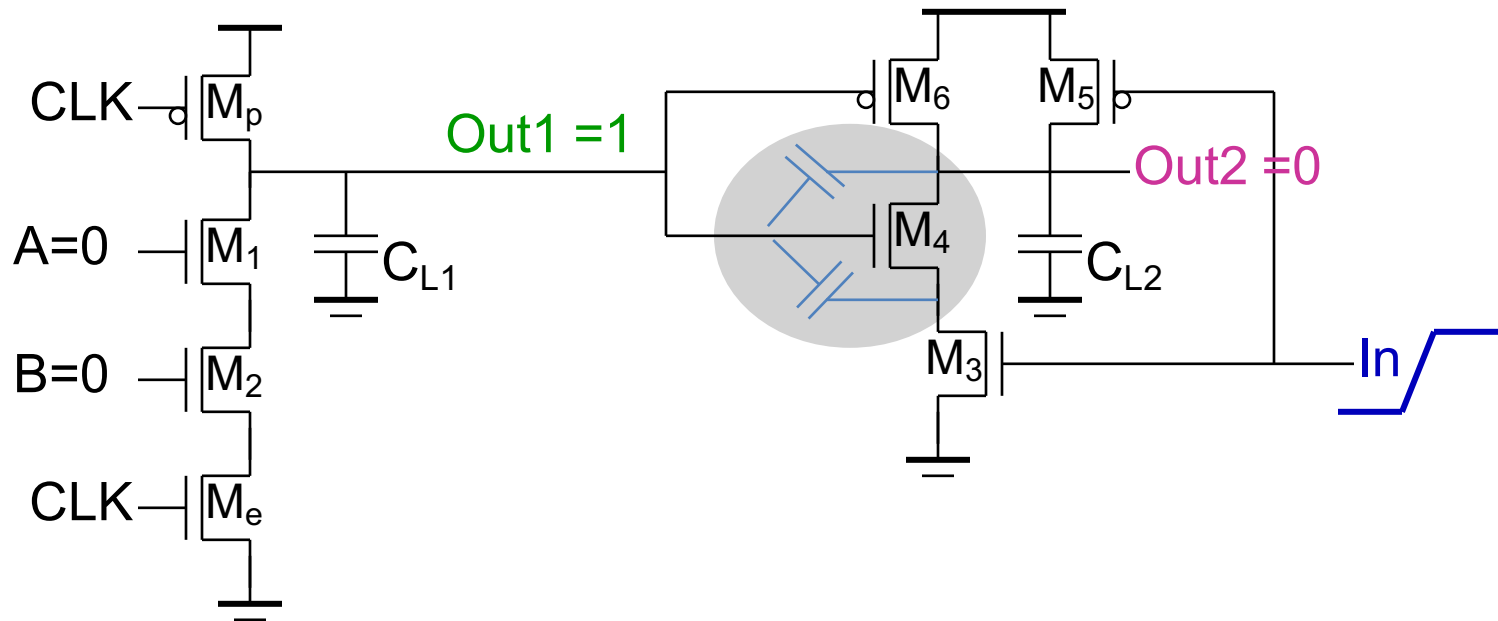
# Backgate Coupling

- Susceptible to crosstalk due to 1) high impedance of the output node and 2) backgate capacitive coupling
- ◆ **Out2** capacitively couples with **Out1** through the gate-source and gate-drain capacitances of M4




Dynamic NAND

Static NAND

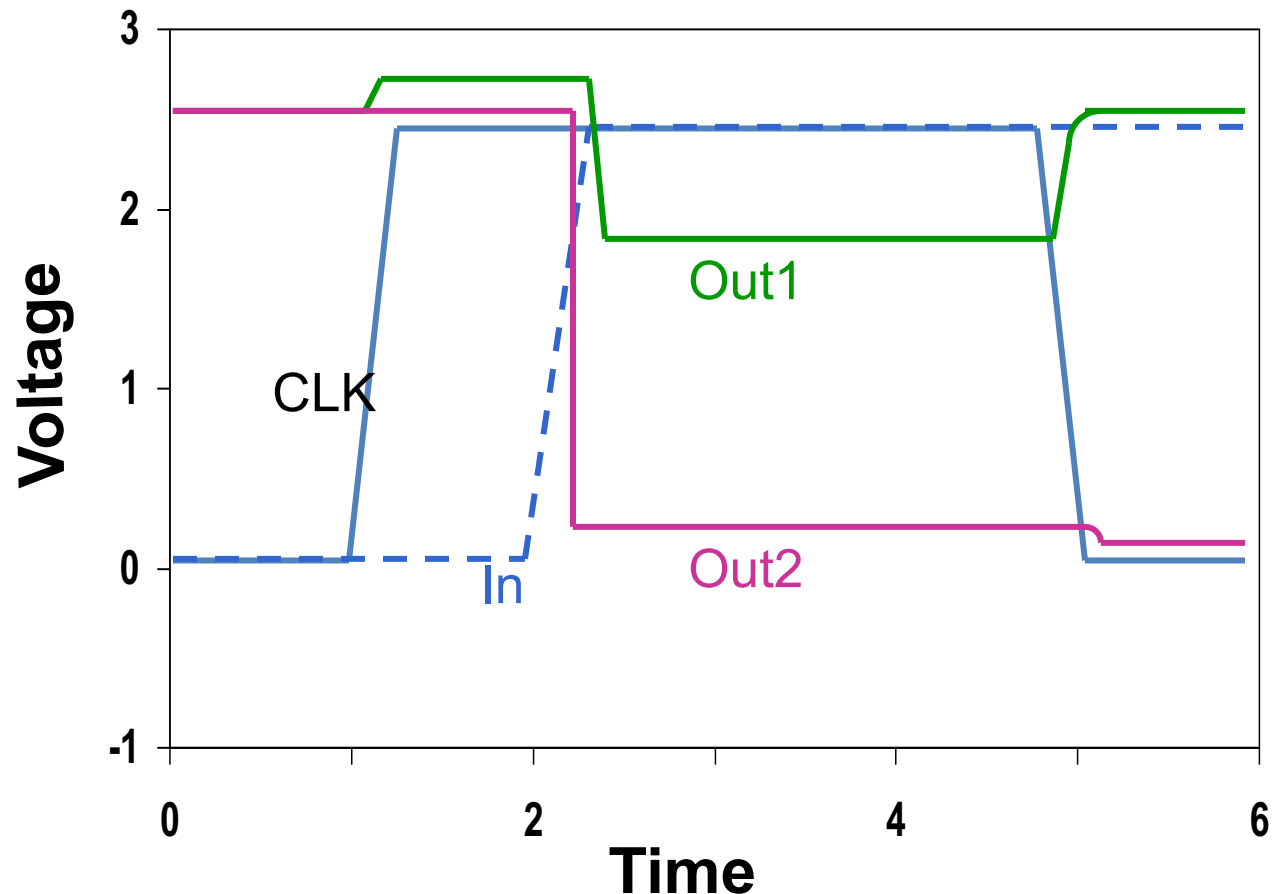
# Backgate Coupling Effect

- Capacitive coupling means Out1 drops significantly so Out2 doesn't go all the way to ground




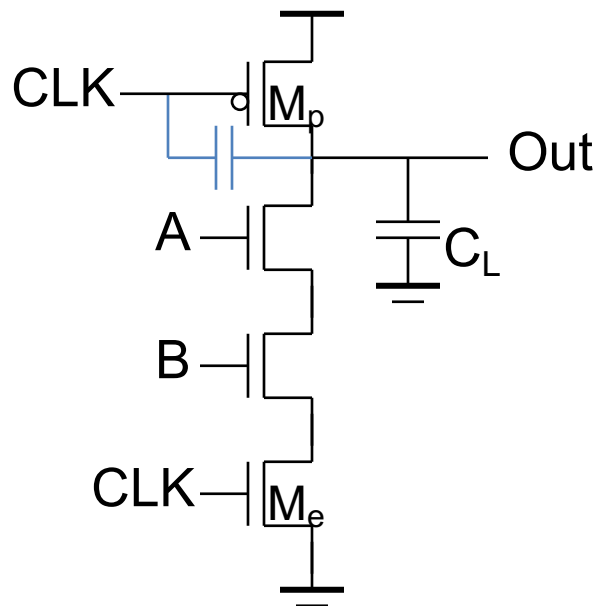
# Clock Feedthrough

- A special case of backgate capacitive coupling between the clock input of the precharge transistor and the dynamic output node




Coupling between Out and CLK input of the precharge device due to the gate-drain capacitance. So voltage of Out can rise above  $V_{DD}$ . The fast rising (and falling edges) of the clock couple to Out.

# Clock Feedthrough

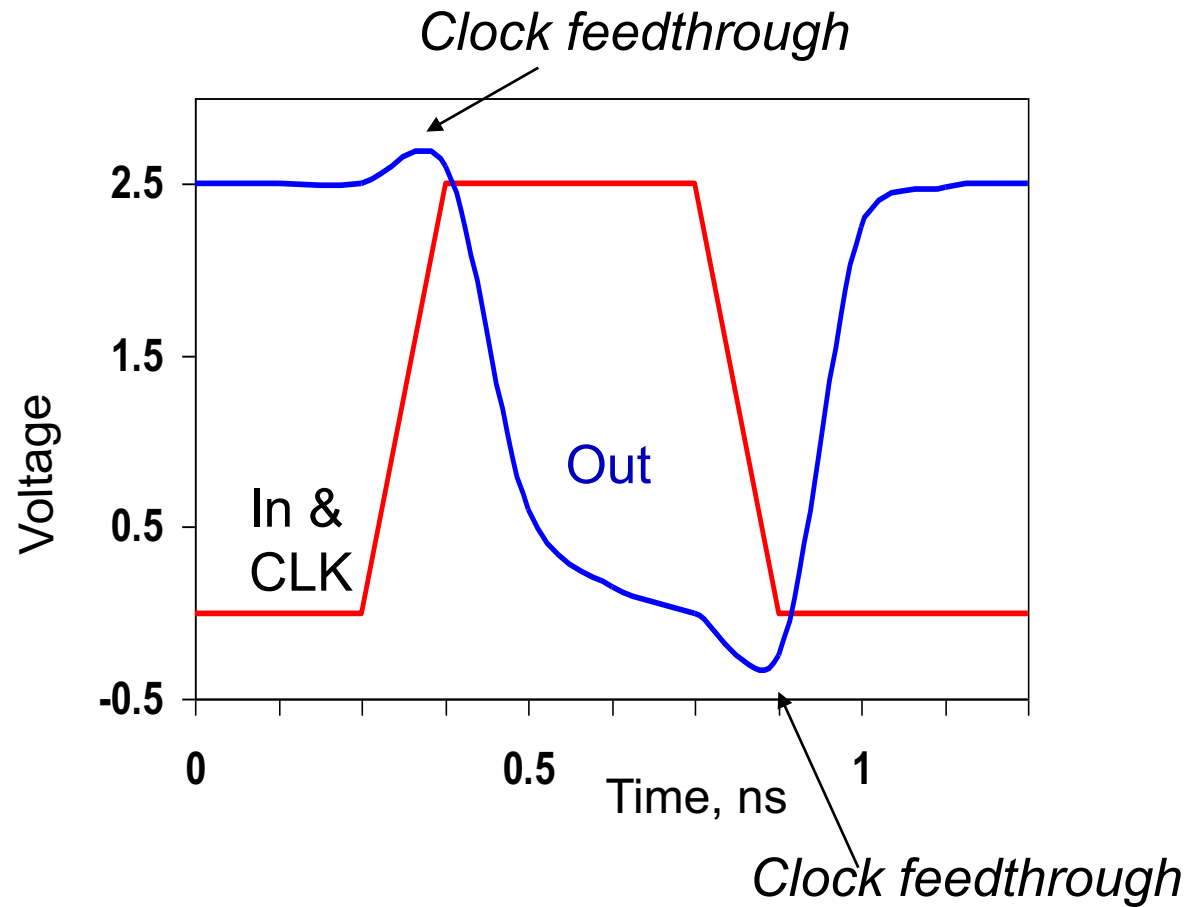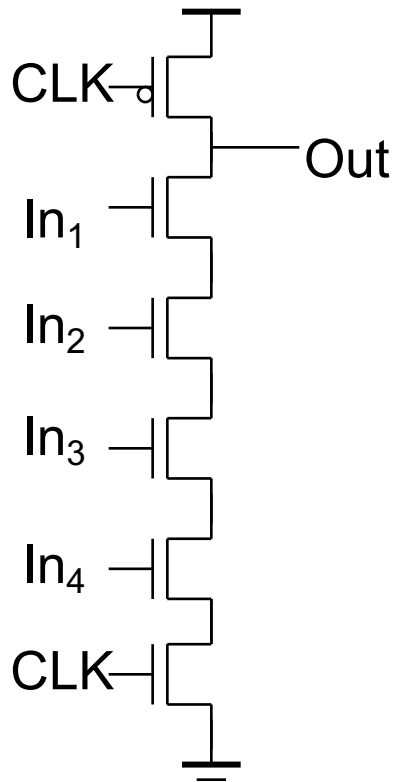



# Power Consumption of Dynamic Gate

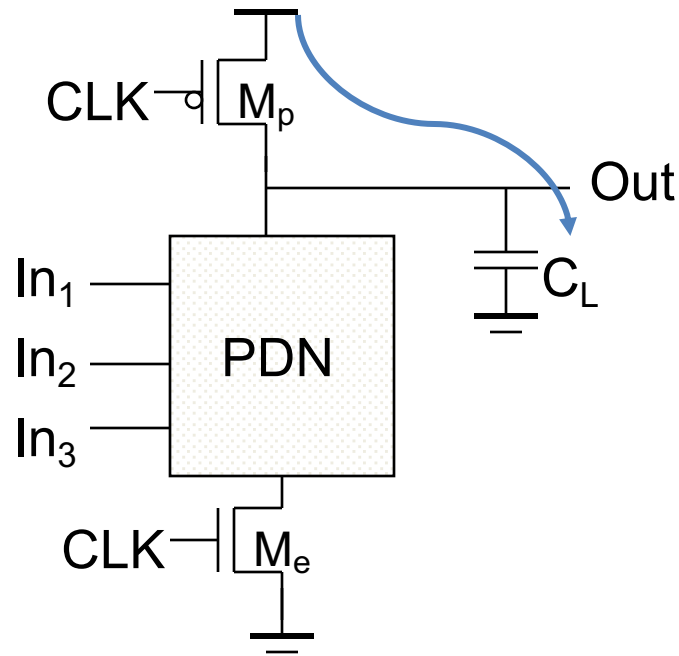

Power only dissipated when previous Out = 0

# Dynamic Power Consumption is Data Dependent

## Dynamic 2-input NOR Gate

A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0

Assume **signal probabilities**

$$P_{A=1} = 1/2$$

$$P_{B=1} = 1/2$$

Then **transition probability**

$$P_{0 \rightarrow 1} = P_{\text{out}=0} \times P_{\text{out}=1}$$

$$= 3/4 \times 1 = 3/4$$

Switching activity can be higher in dynamic gates!

$$P_{0 \rightarrow 1} = P_{\text{out}=0}$$

# Power

---

- Domino gates have high activity factors
  - ◆ Output evaluates and precharges
    - If output probability = 0.5,  $\alpha = 0.5$ 
      - Output rises and falls on half the cycles
  - ◆ Clocked transistors have  $\alpha = 1$
- Leads to very high power consumption

# Noise Sensitivity

---

- Dynamic gates are very sensitive to noise
  - ◆ Inputs:  $V_{IH} \approx V_{tn}$
  - ◆ Outputs: floating output susceptible noise
- Noise sources
  - ◆ Capacitive crosstalk
  - ◆ Charge sharing
  - ◆ Power supply noise
  - ◆ Feedthrough noise
  - ◆ And more!

# Properties of Dynamic Gates

---

- Logic function is implemented by the PDN only
  - ◆ number of transistors is  $N + 2$  (versus  $2N$  for static complementary CMOS)
- Full swing outputs ( $V_{OL} = \text{GND}$  and  $V_{OH} = V_{DD}$ )
- Non-ratioed - sizing of the devices does not affect the logic levels
- Faster switching speeds
  - ◆ reduced load capacitance due to lower input capacitance ( $C_{in}$ )
  - ◆ reduced load capacitance due to smaller output loading ( $C_{out}$ )
  - ◆ no  $I_{sc}$ , so all the current provided by PDN goes into discharging  $C_L$
  - ◆ Ignoring the influence of precharge time on the switching speed of the gate,  $t_{pLH} = 0$  but the presence of the evaluation transistor slows down the  $t_{pHL}$

# Properties of Dynamic Gates

---

- Power dissipation should be better
  - ◆ consumes only dynamic power – no short circuit power consumption since the pull-up path is not on when evaluating
  - ◆ lower  $C_L$ - both  $C_{int}$  (since there are fewer transistors connected to the drain output) and  $C_{ext}$  (since there the output load is one per connected gate, not two)
  - ◆ by construction can have at most one transition per cycle – **no glitching**
- But power dissipation can be significantly **higher** due to
  - ◆ *higher transition probabilities*
  - ◆ *extra load on CLK*
- PDN starts to work as soon as the input signals exceed  $V_{Tn}$ , so set  $V_M$ ,  $V_{IH}$  and  $V_{IL}$  all equal to  $V_{Tn}$ 
  - ◆ low noise margin ( $NM_L$ )
- Needs a precharge clock

# How to Choose a Logic Style

---

- Depends on your area, speed, power and ease of design
- Static CMOS is the most robust to noise
  - ◆ Best general purpose logic style
  - ◆ Complementary CMOS with large fan-in and complex gates
    - high area cost, and lower performance
    - Pseudo NMOS
    - Pass-transistors for MUX and adders
- Dynamic logic is the fastest
  - ◆ Noise sensitive
  - ◆ A lot of design problems
  - ◆ Lower bound on freq. due to charge leakage

# How to Choose a Logic Style

---

- Must consider ease of design, robustness (noise immunity), area, speed, power, system clocking requirements, fan-out, functionality, ease of testing
- Current trend is towards an increased use of complementary static CMOS: design support through DA tools, robust, more amenable to voltage scaling.