

Digital IC Design

Lec 3: MOS/Wire RC for Transient Time


黃柏蒼 Po-Tsang (Bug) Huang
bughuang@nycu.edu.tw

International College of Semiconductor Technology
National Chiao Tung Yang Ming University

國立陽明交通大學


NATIONAL YANG MING CHIAO TUNG UNIVERSITY

Delay Definitions

 


CMOS Inverter : Dynamic

 - Transient, or **dynamic**, response determines the maximum speed at which a device can be operated.



$$t_{pHL} = f(R_n, C_L)$$

Transient Response

 

Inverter Propagation Delay (Designer)


- To see how a **designer** can optimize the delay of a gate have to expand the R_{eq} in the delay equation

$$t_{pHL} = 0.69 R_{eqn} C_L$$

$$= 0.69 (3/4 (C_L V_{DD}) / I_{DSATn})$$

$$\approx 0.52 C_L / (W/L_n k'_n V_{DSATn})$$

Impacts of NMOS/PMOS Ratio

 

$$\beta = (W/L_p)/(W/L_n)$$

β of 2.4 (= 31 k Ω /13 k Ω)
gives symmetrical
response


β of 1.6 to 1.9 gives
optimal performance

Calibrating Delays

- **Step RC delay model is a good first-order approximation**
- **Accuracy can be improved by including:**
 - ◆ Slope effects
 - ◆ Non-linear capacitive loading
 - ◆ Signal arrival times
 - ◆ Wire models

Sources of Capacitance

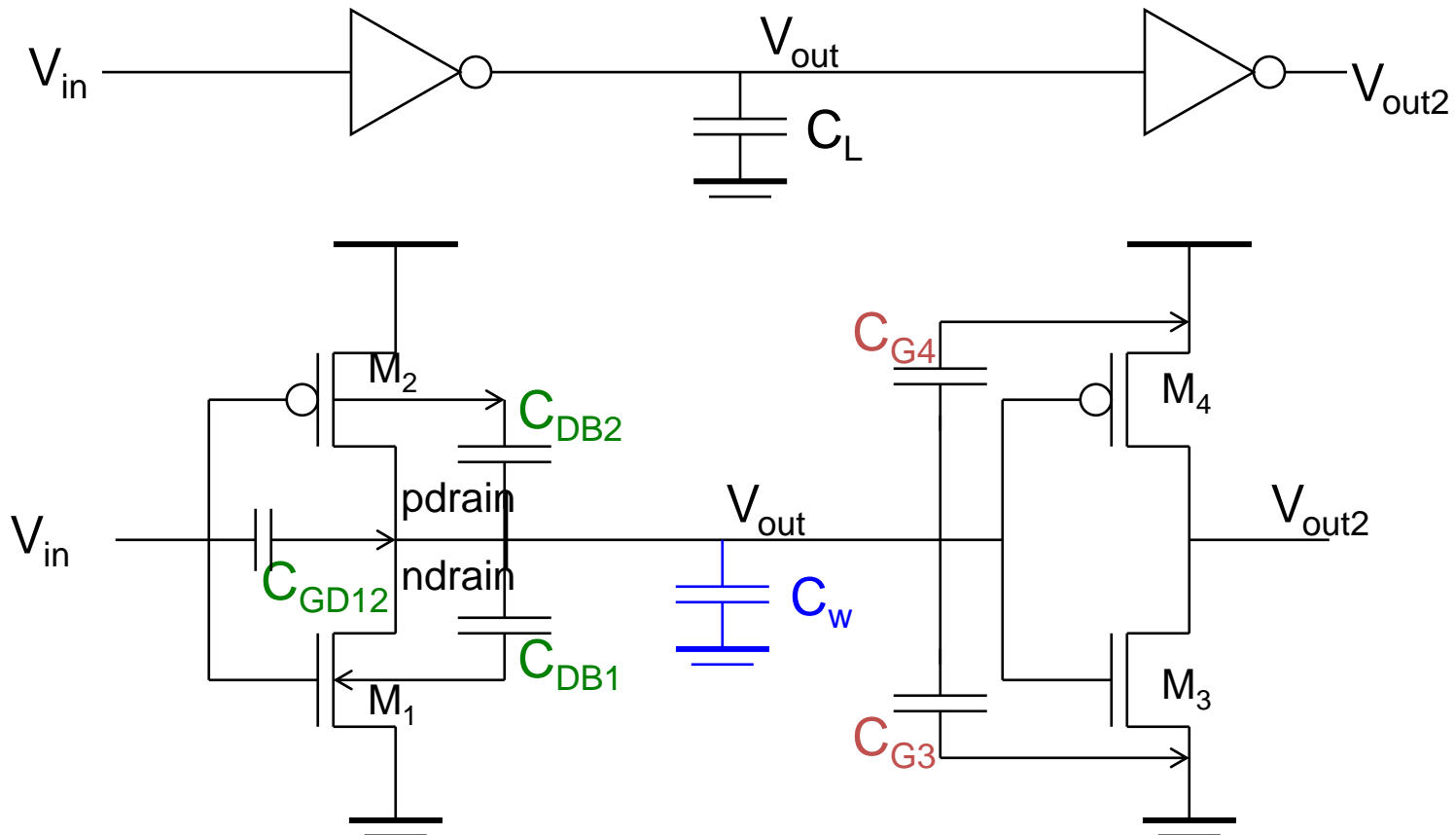- intrinsic MOS transistor capacitances
- extrinsic MOS transistor (fanout) capacitances
- wiring (interconnect) capacitance



MOS Capacitances

■ Gate capacitance

- ◆ Non-linear channel capacitance
- ◆ Linear overlap, fringing capacitances
- ◆ Miller effect on overlap capacitance

■ Non-linear drain diffusion capacitance


- ◆ PN junction

■ Wiring capacitances

- ◆ Linear


Intrinsic MOS Capacitances

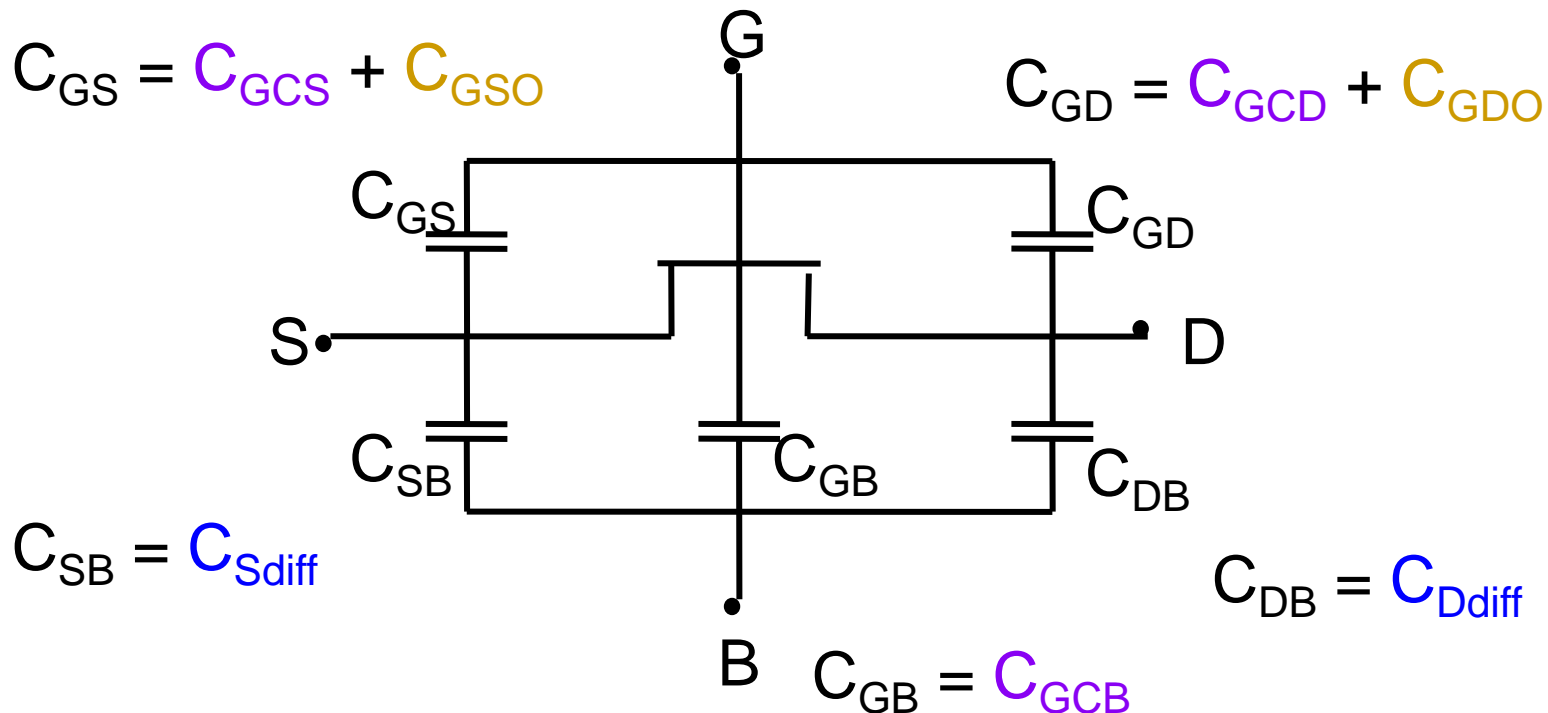- Structure capacitances
- Channel capacitances
- Diffusion capacitances from the depletion regions of the reverse-biased *pn*-junctions




Gate-Drain Capacitance: The Miller Effect

 - M1 and M2 are either in cut-off or in saturation.
- The floating gate-drain capacitor is replaced by a capacitance-to-ground (gate-bulk capacitor).
- Miller Effect: A capacitor experiencing identical but opposite voltage swings at both its terminals can be replaced by a capacitor to ground whose value is two times the original value.



Fan-Out of a Cell (gate)

 - Typically, the output of a logic gate is connected to the input(s) of one or more logic gates
- The fan-out is the number of gates that are connected to the output of the driving gate



- Fanout leads to increased capacitive load on the driving gate, and therefore longer propagation delay
 - ◆ The input capacitances of the driven gates sum, and must be charged through the equivalent resistance of the driver


Extrinsic (Fan-Out) Capacitance

- The extrinsic, or fan-out, capacitance is the total gate capacitance of the loading gates M3 and M4.

$$\begin{aligned} C_{\text{fan-out}} &= C_{\text{gate}} (\text{NMOS}) + C_{\text{gate}} (\text{PMOS}) \\ &= (C_{\text{GSON}} + C_{\text{GDO}_n} + W_n L_n C_{\text{ox}}) + (C_{\text{GSOp}} + C_{\text{GDO}_p} + W_p L_p C_{\text{ox}}) \end{aligned}$$

- Simplification of the actual situation
 - ◆ Assumes all the components of C_{gate} are between V_{out} and GND (or V_{DD})
 - ◆ Assumes the channel capacitances of the loading gates are constant


FO4 Inverter Delay

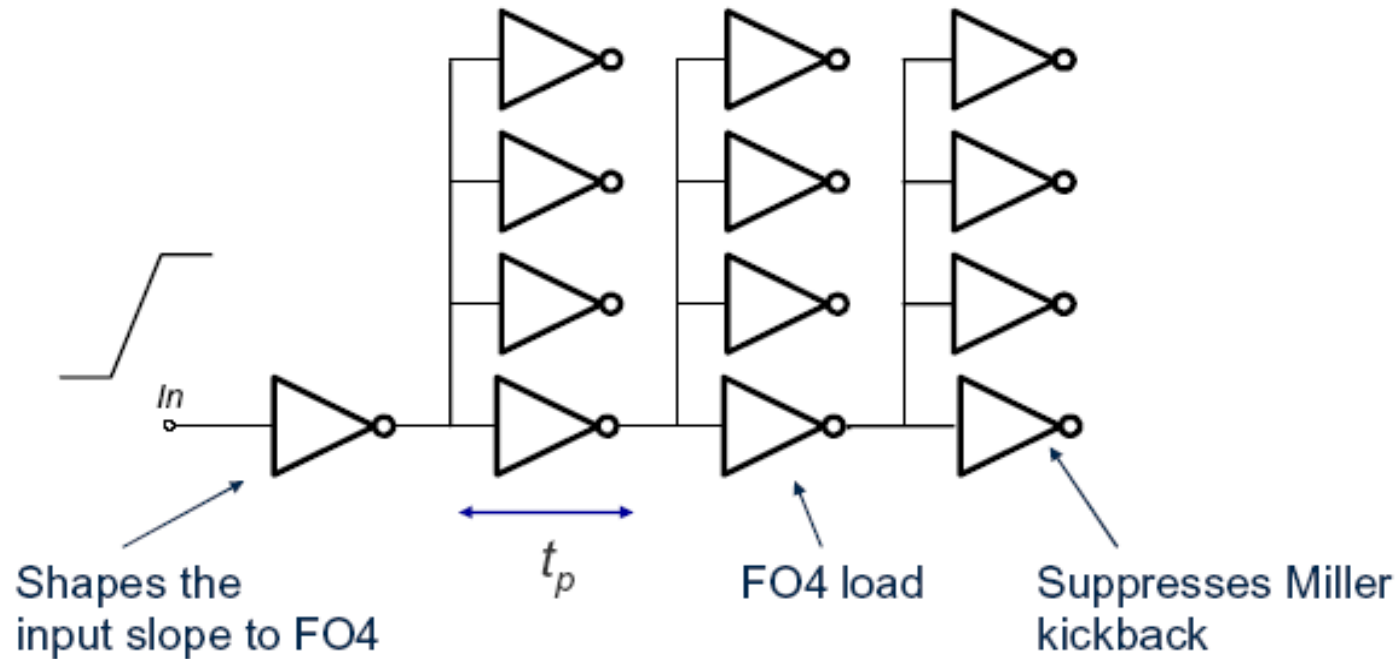

Wiring Capacitance

- The wiring capacitance depends upon the length and width of the connecting wires and is a function of the fan-out from the driving gate and the number of fan-out gates.
- Wiring capacitance is growing in importance with the scaling of technology.

Parallel Plate Wiring Capacitance

 


permittivity
constant
($\text{SiO}_2 = 3.9$)


$$C_{pp} = (\epsilon_{di}/t_{di}) WL$$

Sources of Interwire Capacitance

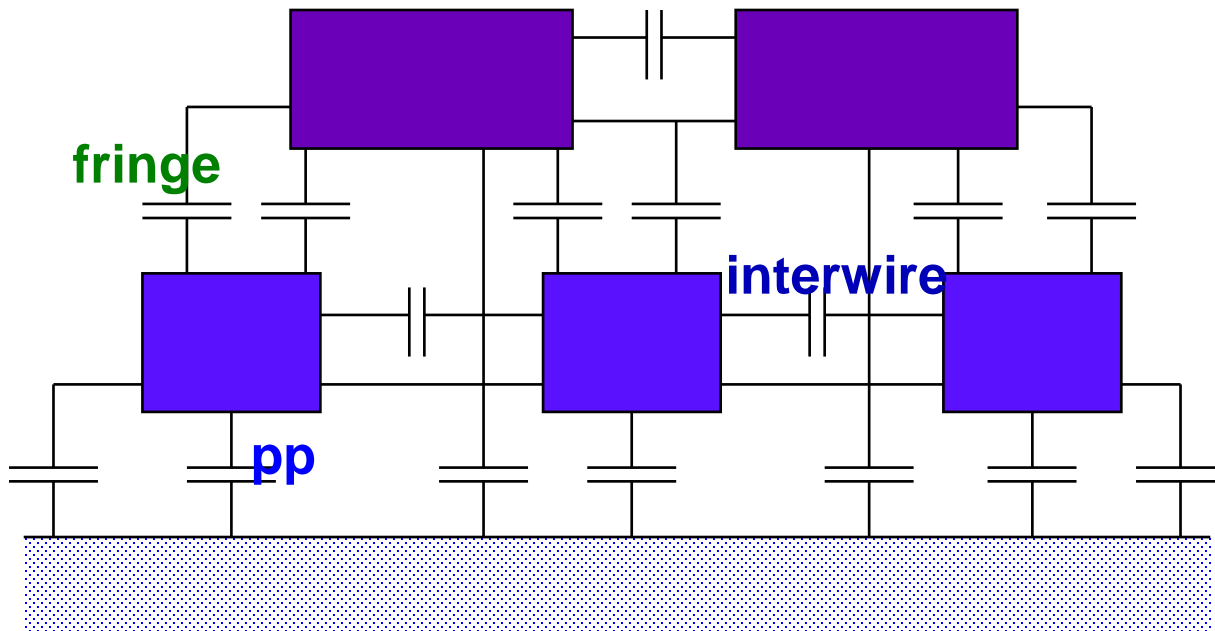
$$\begin{aligned}C_{\text{wire}} &= C_{\text{pp}} + C_{\text{fringe}} + C_{\text{interwire}} \\&= (\epsilon_{\text{di}}/t_{\text{di}})WL \\&\quad + (2\pi\epsilon_{\text{di}})/\log(t_{\text{di}}/H) \\&\quad + (\epsilon_{\text{di}}/t_{\text{di}})HL\end{aligned}$$



Impact of Fringe Capacitance

 

Impact of Interwire Capacitance

 


Wiring Insights

- For $W/H < 1.5$, the fringe component dominates the parallel-plate component. Fringing capacitance can increase the overall capacitance by a factor of 10 or more.
- When $W/H < 1.75$ interwire capacitance starts to dominate
- Interwire capacitance is more pronounced for wires in the higher interconnect layers (further from the substrate)
- Rules of thumb
 - ◆ Never run wires in diffusion
 - ◆ Use poly only for short runs
 - ◆ Shorter wires – lower R and C
 - ◆ Thinner wires – lower C but higher R
- Wire delay nearly proportional to L^2

CMOS Inverter : Dynamic

 
- Transient, or **dynamic**, response determines the maximum speed at which a device can be operated.



$$t_{pHL} = f(R_n, C_L)$$


Sources of Resistance

 - MOS structure resistance - R_{on}
- Source and drain resistance
- Contact (via) resistance
- Wiring resistance



MOS Transistor as a Switch

Discharging a capacitor

 



- Can solve:

$$i_D = i_D(v_{DS})$$


$$i_D = C \frac{dV_{DS}}{dt}$$

- Prefer using equivalent resistances

Equivalent MOS Resistance

  


Traversed path

 


$$R_{eq} = \text{avg}(R_{on}(t)) \Big|_{t=t_1}^{t_2} = \frac{1}{t_2 - t_1} \int_{t_1}^{t_2} R_{on}(t) \cdot dt = \frac{1}{t_2 - t_1} \int_{t_1}^{t_2} \frac{V_{DS}(t)}{I_D(t)} \cdot dt$$

$$R_{eq} \approx \frac{1}{2} \cdot (R_{on}(t_1) + R_{on}(t_2))$$

Equivalent MOS Resistance

 
 
$$R_{eq} = \frac{1}{2} \cdot (R_0 + R_{mid})$$



$$R_{eq} = \frac{1}{2} \cdot \left(\frac{V_{DD}}{I_{DSAT} \cdot (1 + \lambda \cdot V_{DD})} + \frac{V_{DD}/2}{I_{DSAT} \cdot (1 + \lambda \cdot V_{DD}/2)} \right)$$

$$R_{eq} \approx \frac{3}{4} \cdot \frac{V_{DD}}{I_{DSAT}} \left(1 - \frac{5}{6} \cdot \lambda \cdot V_{DD} \right)$$

Approximate MOS Resistance

Solving the integral:

$$R_{eq} = \frac{1}{-V_{DD}/2} \int_{V_{DD}}^{V_{DD}/2} \frac{V}{I_{DSAT}(1 + \lambda V)} dV \approx \frac{3}{4} \frac{V_{DD}}{I_{DSAT}} \left(1 - \frac{7}{9} \lambda V_{DD} \right)$$

$$\text{with } I_{DSAT} = k' \frac{W}{L} \left((V_{DD} - V_T) V_{DSAT} - \frac{V_{DSAT}^2}{2} \right)$$

Averaging resistances:


$$R_{eq} = \frac{1}{2} \left(\frac{V_{DD}}{I_{DSAT}(1 + \lambda V_{DD})} + \frac{V_{DD}/2}{I_{DSAT}(1 + \lambda V_{DD}/2)} \right) \approx \frac{3}{4} \frac{V_{DD}}{I_{DSAT}} \left(1 - \frac{5}{6} \lambda V_{DD} \right)$$

Often just:


$$R_{eq} \approx \frac{3}{4} \cdot \frac{V_{DD}}{I_{DSAT}}$$

CMOS Performance

 Propagation delay: $t_{pHL} = (\ln 2)R_{eqn}C_L$ $t_{pLH} = (\ln 2)R_{eqp}C_L$



(a) schematic

 

(b) trajectory traversed on ID-VDS curve.

$\ln 2 = 0.7$

Short channel

$$R_{eq} \neq f(V_{DD})$$


Long channel

$$R_{eq} \propto \frac{1}{V_{DD}}$$

for $V_{DD} \gg V_T$

MOS Structure Resistance

 
- The simplest model assumes the transistor is a switch with an infinite “off” resistance and a finite “on” resistance R_{on}



- However R_{on} is nonlinear, so use instead the average value of the resistances, R_{eq} , at the end-points of the transition (V_{DD} and $V_{DD}/2$)

$$R_{eq} = \frac{1}{2} (R_{on}(t_1) + R_{on}(t_2))$$
$$R_{eq} = \frac{3}{4} V_{DD} / I_{DSAT} (1 - \frac{5}{6} \lambda V_{DD})$$

Source and Drain Resistance

 

$$R_{S,D} = (L_{S,D}/W)R$$

where $L_{S,D}$ is the length of the source or drain diffusion
 R is the sheet resistance of the source or drain diffusion (20 to 100 Ω/\square)


- More pronounced with scaling since junctions are shallower
- With silicidation R is reduced to the range 1 to 4 Ω/\square

Contact Resistance


- Transitions between routing layers (contacts through via's) add extra resistance to a wire
 - ◆ keep signals wires on a single layer whenever possible
 - ◆ avoid excess contacts
 - ◆ reduce contact resistance by making vias larger (beware of **current crowding** that puts a practical limit on the size of vias) or by using multiple minimum-size vias to make the contact
- Typical contact resistances, R_C , (minimum-size)
 - ◆ 5 to 20 Ω for metal or poly to n+, p+ diffusion and metal to poly
 - ◆ 1 to 5 Ω for metal to metal contacts
- More pronounced with scaling since contact openings are smaller

Contacts Resistance

 - Use many contacts for lower R
 - ◆ Many small contacts for current crowding around periphery



Wire Resistance

 

$$R = \frac{\rho L}{A} = \frac{\rho L}{HW}$$

A pink oval highlights the ρ in the second fraction, with a pink arrow pointing from it towards the text 'Sheet Resistance R'.

Sheet Resistance R

$$R_{1\Box} = R_{2\Box}$$


Below the equation, there are two pink squares. The first is a small square, and the second is a larger square. They are separated by an equals sign, illustrating that sheet resistance is independent of the size of the square.

Material	$\rho(\Omega\text{-m})$
Silver (Ag)	1.6×10^{-8}
Copper (Cu)	1.7×10^{-8}
Gold (Au)	2.2×10^{-8}
Aluminum (Al)	2.7×10^{-8}
Tungsten (W)	5.5×10^{-8}

Material	Sheet Res. (Ω/\square)
n, p well diffusion	1000 to 1500
n+, p+ diffusion	50 to 150
n+, p+ diffusion with silicide	3 to 5
polysilicon	150 to 200
polysilicon with silicide	4 to 5
Aluminum	0.05 to 0.1

Skin Effect

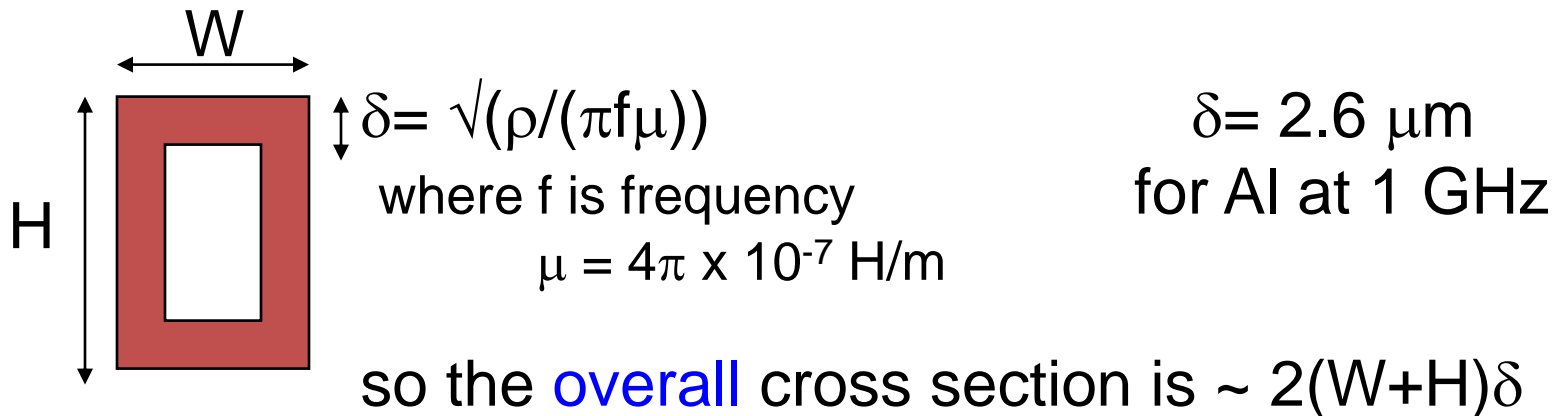- At high frequency, currents tend to flow primarily on the surface of a conductor with the current density falling off exponentially with depth into the wire




- The onset of skin effect is at f_s - where the skin depth is equal to half the largest dimension of the wire.

$$f_s = 4 \rho / (\pi \mu (\max(W, H))^2)$$


- An issue for high frequency, wide (tall) wires (i.e., clocks!)

Skin Effect for Different W's

 

- A 30% increase in resistance is observed for $20 \text{ } \mu\text{m}$ Al wires at 1 GHz (versus only a 1% increase for $1 \text{ } \mu\text{m}$ wires)


The Wire

 

transmitters

receivers


schematic

 


physical

Wire Models

 - Interconnect parasitics (capacitance, resistance, and inductance)
 - ◆ reduce reliability
 - ◆ affect performance and power consumption



All-inclusive (C,R,I) model

 

Capacitance-only

Parasitic Simplifications

- Inductive effects can be ignored
 - ◆ if the resistance of the wire is substantial enough (as is the case for long metal wires with small cross section)
 - ◆ if the rise and fall times of the applied signals are slow enough
- When the wire is short, or the cross-section is large, or the interconnect material has low resistivity, a capacitance only model can be used
- When the separation between neighboring wires is large, or when the wires run together for only a short distance, interwire capacitance can be ignored and all the parasitic capacitance can be modeled as capacitance to ground


Wire Delay Models

■ Ideal wire

- ◆ same voltage is present at every segment of the wire at every point in time - at equi-potential
- ◆ only holds for *very short* wires, i.e., interconnects between *very* nearest neighbor gates

■ Lumped C model

 - ◆ when only a single parasitic component (C, R, or L) is dominant the different fractions are lumped into a single circuit element
 - When the resistive component is small and the switching frequency is low to medium, can consider only C; the wire itself does not introduce any delay; the only impact on performance comes from wire capacitance



- good for short wires; pessimistic and inaccurate for long wires


Lumped/Distributed Delay Models

■ Lumped RC model

- ◆ total wire resistance is lumped into a single R and total capacitance into a single C
- ◆ good for short wires; pessimistic and inaccurate for long wires

■ Distributed RC model

 - ◆ circuit parasitics are **distributed** along the length, L , of the wire
 - c and r are the capacitance and resistance per unit length



- Delay is determined using the **Elmore delay** equation

$$\tau_{Di} = \sum_{k=1}^N C_k r_{ik}$$

RC Tree Definitions

RC tree characteristics

- A unique resistive path exists between the source node and any node of the network

- ◆ Single input (source) node, s
- ◆ All capacitors are between a node and GND
- ◆ No resistive loops

- Path resistance** (sum of the resistances on the path from the input node to node i)


$$r_{ii} = \sum_{j=1}^i r_j \Rightarrow (r_j \in [\text{path}(s \rightarrow i)])$$

- Shared path** resistance (resistance shared along the paths from the input node to nodes i and k)

$$r_{ik} = \sum_{j=1}^N r_j \Rightarrow (r_j \in [\text{path}(s \rightarrow i) \cap \text{path}(s \rightarrow k)])$$


- A typical wire is a **chain** network with (simplified) Elmore delay of

$$\tau_{DN} = \sum_{i=1}^N c_i r_{ii}$$

 

Chain Network Elmore Delay
 
$$\tau_{D1} = c_1 r_1 \quad \tau_{D2} = c_1 r_1 + c_2 (r_1 + r_2)$$



$$\tau_{Di} = c_1 r_1 + c_2 (r_1 + r_2) + \dots + c_i (r_1 + r_2 + \dots + r_i)$$

Elmore delay equation $\tau_{DN} = \sum c_i r_{ii} = \sum_{i=1}^N c_i \sum_{j=1}^i r_j$

$$\tau_{Di} = c_1 r_{eq} + 2c_2 r_{eq} + 3c_3 r_{eq} + \dots + i c_i r_{eq}$$

Distributed RC Model for Simple Wires

- A length L RC wire can be modeled by N segments of length L/N
 - ◆ The resistance and capacitance of each segment are given by $r L/N$ and $c L/N$

$$\tau_{DN} = (L/N)^2(cr + 2cr + \dots + Ncr) = (crL^2) (N(N+1))/(2N^2) = CR((N+1)/(2N))$$

where $R (= rL)$ and $C (= cL)$ are the total lumped resistance and capacitance of the wire

- For large N

$$\tau_{DN} = RC/2 = rcL^2/2$$

- Delay of a wire is a **quadratic** function of its length, L
- The delay is **1/2** of that predicted (by the lumped model)


Step Response Points

Voltage Range	Lumped RC	Distributed RC
$0 \rightarrow 50\% (t_p)$	0.69 RC	0.38 RC
$0 \rightarrow 63\% (\tau)$	RC	0.5 RC
$10\% \rightarrow 90\% (t_r)$	2.2 RC	0.9 RC
$0 \rightarrow 90\%$	2.3 RC	1.0 RC


Time to reach the 50% point is $t = \ln(2)\tau = 0.69\tau$

Time to reach the 90% point is $t = \ln(9)\tau = 2.2\tau$

Nature of Interconnect

 


Wire Spacing

 


Inductance of Wires

 - When the rise and fall times of the signal become comparable to the time of flight of the signal waveform across the line, then the **inductance** of the wire starts to dominate the delay behavior



- Must consider wire **transmission line** effects
 - ◆ Signal propagates over the wire as a **wave** (rather than **diffusing** as in rc only models)
 - Signal propagates by alternately transferring energy from capacitive to inductive modes

Delay of MOS + Wire

 

- Total propagation delay consider driver and wire

$$\tau_D = R_{Driver} C_w + (R_w C_w)/2 = R_{Driver} C_w + 0.5 r_w c_w L^2$$

$$\text{and } t_p = 0.69 R_{Driver} C_w + 0.38 R_w C_w$$

where $R_w = r_w L$ and $C_w = c_w L$

- The delay introduced by wire resistance becomes dominant when

$$(R_w C_w)/2 \geq R_{Driver} C_w \quad (\text{when } L \geq 2R_{Driver}/r_w)$$


- For an $R_{Driver} = 1 \text{ k}\Omega$ driving an $1 \text{ }\mu\text{m}$ wide Al1 wire, L_{crit} is 2.67 cm

Crosstalk

- A capacitor does not like to change its voltage instantaneously.
- A wire has high capacitance to its neighbor.
 - ◆ When the neighbor switches from 1- \rightarrow 0 or 0- \rightarrow 1, the wire tends to switch too.
 - ◆ Called capacitive *coupling* or *crosstalk*.
- Crosstalk effects
 - ◆ Noise on nonswitching wires
 - ◆ Increased delay on switching wires

Crosstalk Delay

 - Assume layers above and below on average are quiet
 - ◆ Second terminal of capacitor can be ignored
 - ◆ Model as $C_{\text{gnd}} = C_{\text{top}} + C_{\text{bot}}$
- Effective C_{adj} depends on behavior of neighbors
 - ◆ *Miller effect*




B	ΔV	$C_{\text{eff(A)}}$	MCF
Constant	V_{DD}	$C_{\text{gnd}} + C_{\text{adj}}$	1
Switching with A	0	C_{gnd}	0
Switching opposite A	$2V_{\text{DD}}$	$C_{\text{gnd}} + 2 C_{\text{adj}}$	2

Crosstalk Noise


- Crosstalk causes noise on nonswitching wires
- If victim is floating:
 - ◆ model as capacitive voltage divider
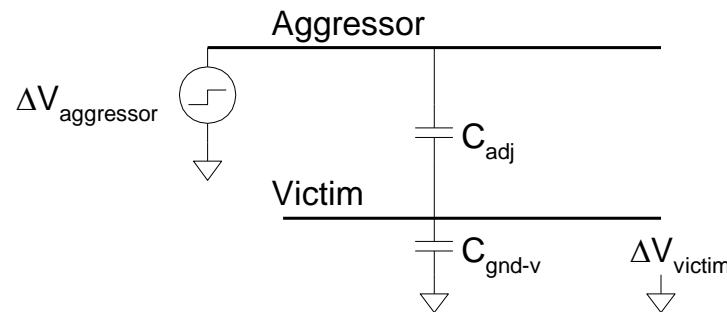
$$\Delta V_{victim} = \frac{C_{adj}}{C_{gnd-v} + C_{adj}} \Delta V_{aggressor}$$



Coupling Waveforms

 - Simulated coupling for $C_{\text{adj}} = C_{\text{victim}}$




Noise Implications

- *So what* if we have noise?
- If the noise is less than the noise margin, nothing happens
- Static CMOS logic will eventually settle to correct output even if disturbed by large noise spikes
 - ◆ But glitches cause extra delay
 - ◆ Also cause extra power from false transitions
- Dynamic logic never recovers from glitches
- Memories and other sensitive circuits also can produce the wrong answer

Wire Engineering

 - Goal: achieve delay, area, power goals with acceptable noise
- Degrees of freedom:
 - ◆ Width
 - ◆ Spacing
 - ◆ Layer
 - ◆ Shielding



Repeaters

- R and C are proportional to l
- RC delay is proportional to l^2
 - ◆ Unacceptably great for long wires
- Break long wires into N shorter segments
 - ◆ Drive each one with an inverter or buffer

