

# Digital IC Design

## Lecture 8: Embedded Memory


黃柏蒼 Po-Tsang (Bug) Huang  
bughuang@nycu.edu.tw

International College of Semiconductor Technology  
National Chiao Tung Yang Ming University

國立陽明交通大學



NATIONAL YANG MING CHIAO TUNG UNIVERSITY

# Memory Arrays

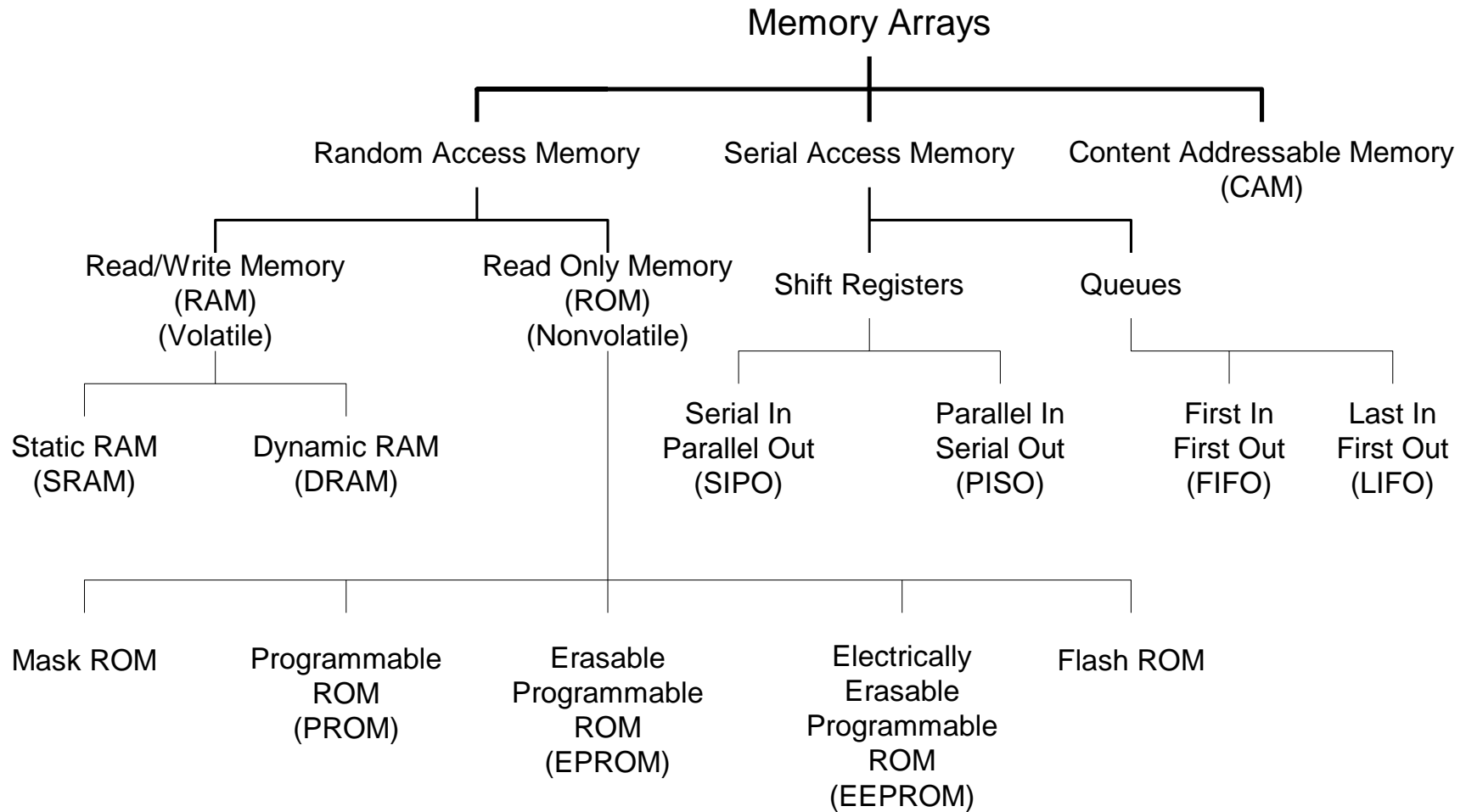

  
# Memory Array

- Decode address to access the corresponding data




 
# Memory Array Architecture

- $2^n$  words of  $2^m$  bits each
- If  $n \gg m$ , fold by  $2^k$  into fewer rows of more columns
- Good regularity – easy to design
- Very high density if good cells are used




# Basic Memory Subsystem Block Diagram

  

**Construct large memory through modular design**
 
# Memory Structure

- Memory array
- Interconnection architecture (memory bus)



# Memory Array Architecture

---

## ■ Address decoder

- ◆ 1-D address
- ◆ 2-D address
  - Separated into row/column

## ■ Memory cell array

- ◆ Static: SRAM
- ◆ embedded DRAM
- ◆ embedded Nonvolatile memory
  - eflash, ReRAM, MRAM


## ■ Read out

- ◆ Sense amplifier

# Operation of Memory
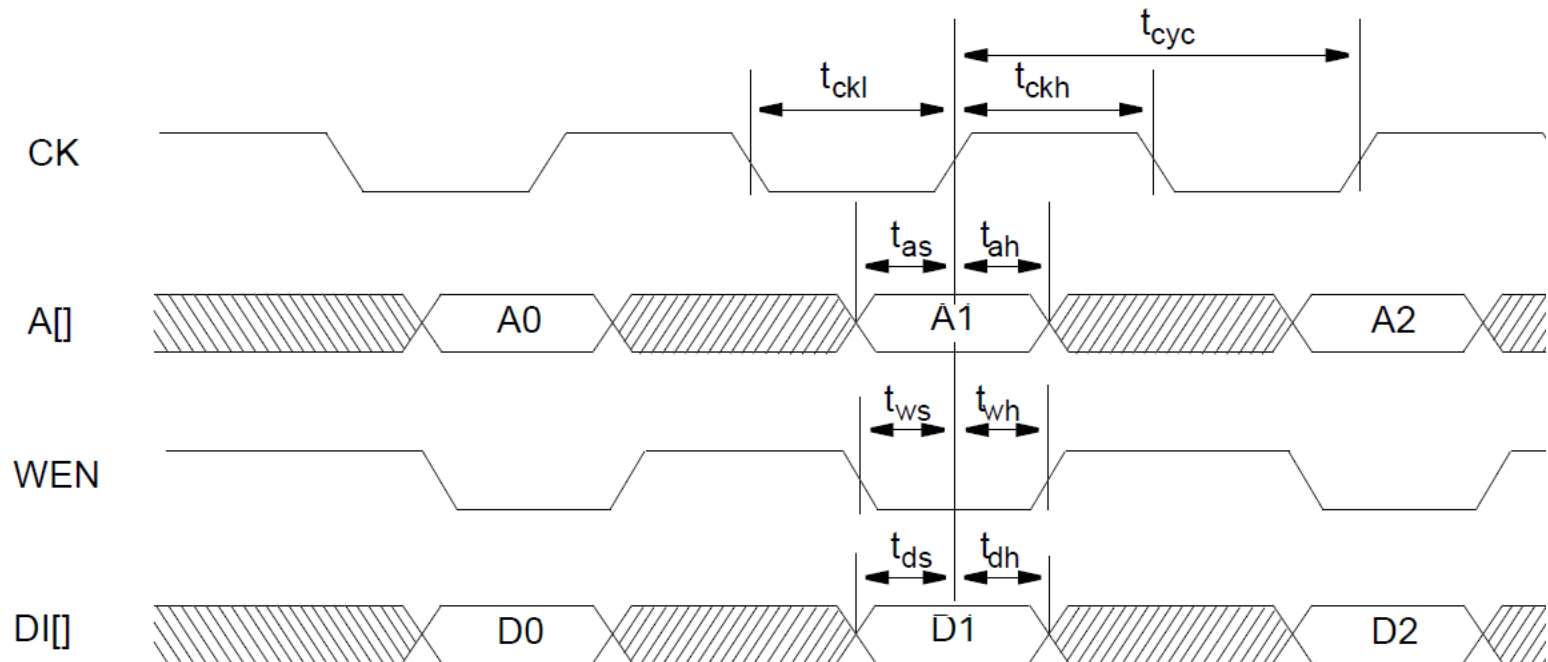
## ■ Write

- ◆ Send address, read/write control, *data to write*






# Operation of Memory
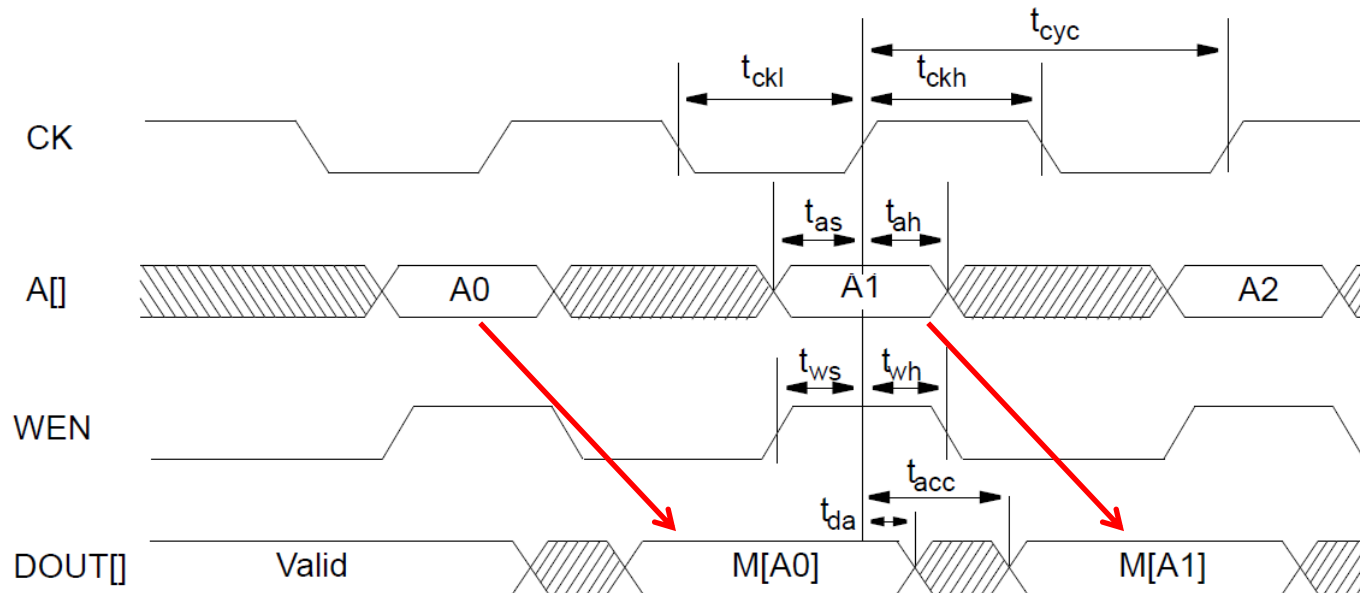
## ■ Read


- ◆ Send address, read/write control
- ◆ Output data



# Basic Blocks of Memory


 
## ■ SRAM basic structure

- ◆ SRAM Array
- ◆ Sense amplifier
- ◆ Write Driver
- ◆ Row decoder
- ◆ Column decoder
- ◆ Timing unit
- ◆ Address Latch
- ◆ Input latch
- ◆ Output latch


 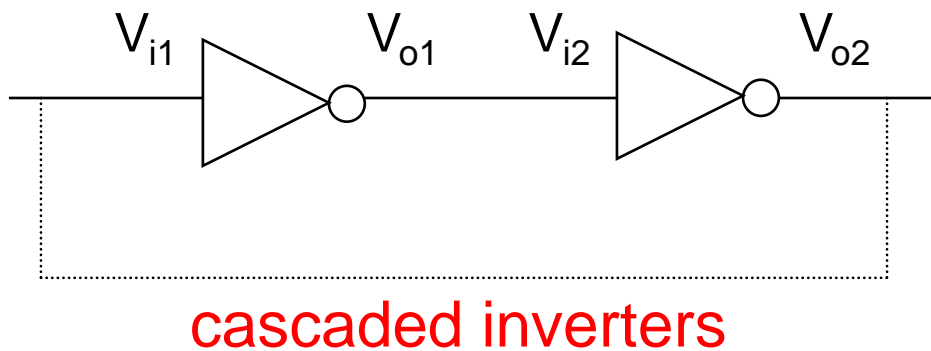
# Regenerative Property of Bistable Circuits

- The cross-coupling of two inverters results in a **bistable circuit** (a circuit with two stable states)
- If the gain in the transient region is larger than 1, only A and B are stable operation points. C is a **metastable** operation point.




# How to write(flip) a Bistable Memory

---

- Have to be able to **change** the stored value by making A (or B) temporarily unstable by increasing the loop gain to a value larger than 1
  - done by applying a trigger pulse at  $V_{i1}$  or  $V_{i2}$
  - the width of the trigger pulse need be only a little larger than the total propagation delay around the loop circuit (twice the delay of an inverter)
- Two approaches for flipping data
  - ◆ cutting the feedback loop (latch/flip-flop)
  - ◆ overpowering the feedback loop (as used in SRAMs)
 
# 6T SRAM Cell


- Cross-coupled inverter to latch/store data
- Bi-directional access transistor


 
# 6T SRAM Cell



---

- Cell size accounts for most of array size
  - ◆ Reduce cell size at expense of complexity
- 6T SRAM Cell
  - ◆ Used in most commercial chips
  - ◆ Data stored in cross-coupled inverters
- Read:
  - ◆ Precharge bit, bit\_b
  - ◆ Raise wordline
- Write:
  - ◆ Drive data onto bit, bit\_b
  - ◆ Raise wordline






# Standby Mode

Standby Cycle:

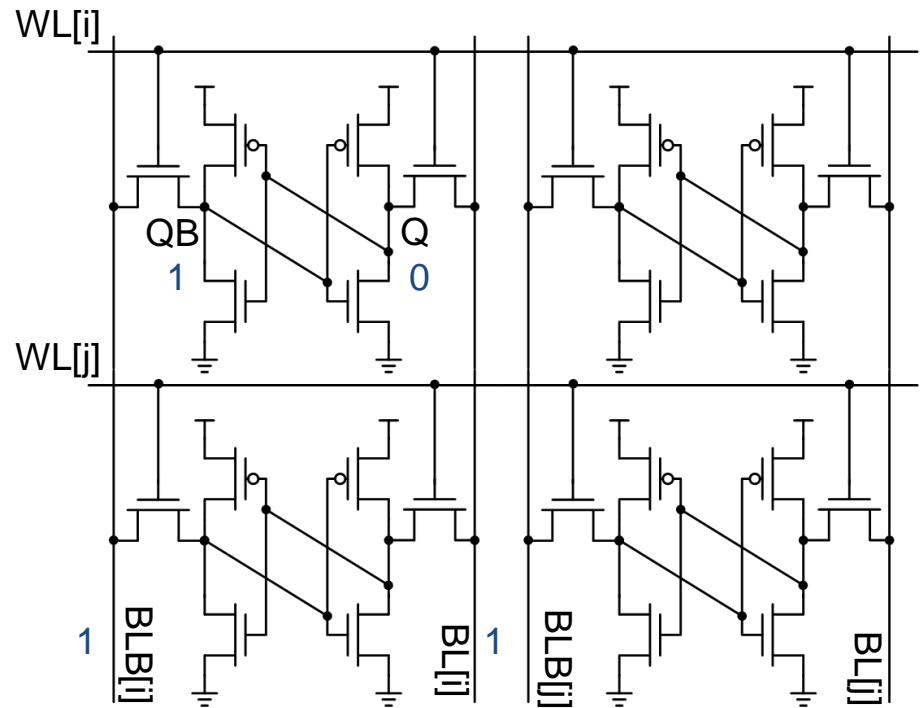 

# Write Operation in Local Circuits

Write Cycle:

 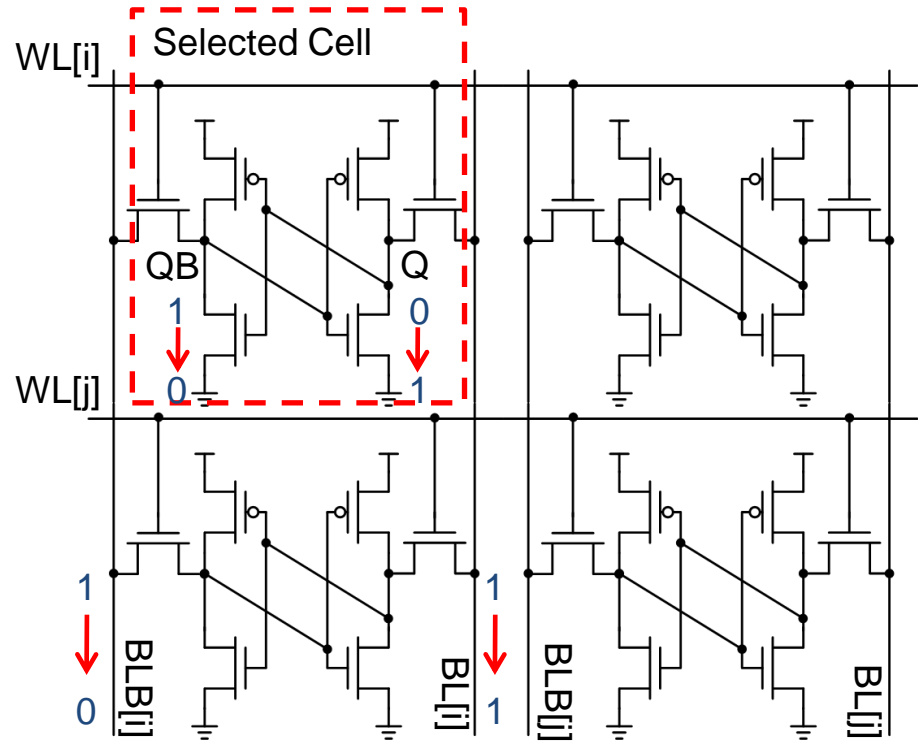 




# Write Operation in Global Circuits

## ■ Data input path

- ◆ Input Latch
- ◆ Write Driver
- ◆ SRAM Array (Selected BL pairs)
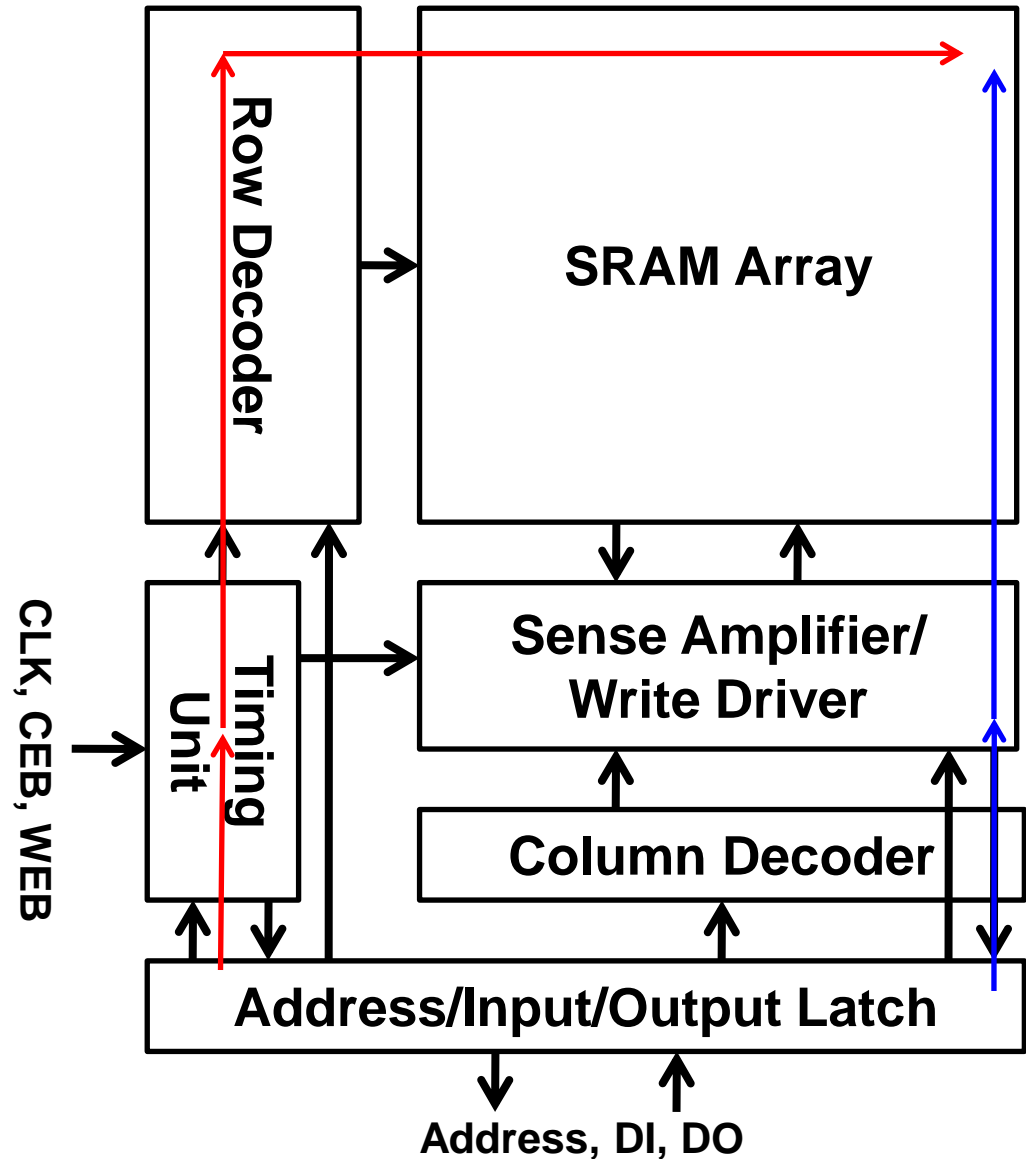
## ■ Control path


- ◆ Address latch
- ◆ Timing Unit
- ◆ Row Decoder
- ◆ SRAM Array (Selected WL)



# Read Operation in Global Circuits

 
## ■ Read critical path

- ◆ Address latch
- ◆ Timing Unit
- ◆ Row Decoder (WL driver)
- ◆ SRAM Array
  - Selected WL
  - Selected BL pairs
- ◆ Sense Amplifier
- ◆ Output latch



 
# Bitline Conditioning (Precharge)

- Two purposes
- Precharge bitlines high before reads



 - Equalize bitlines to minimize voltage difference when using sense amplifiers




# SRAM Read Performance

- In general, the latency of SRAM Read operation is longer than Write operation

$$T_{BL} = \frac{C_{BL} \Delta V}{I_{Cell}}$$

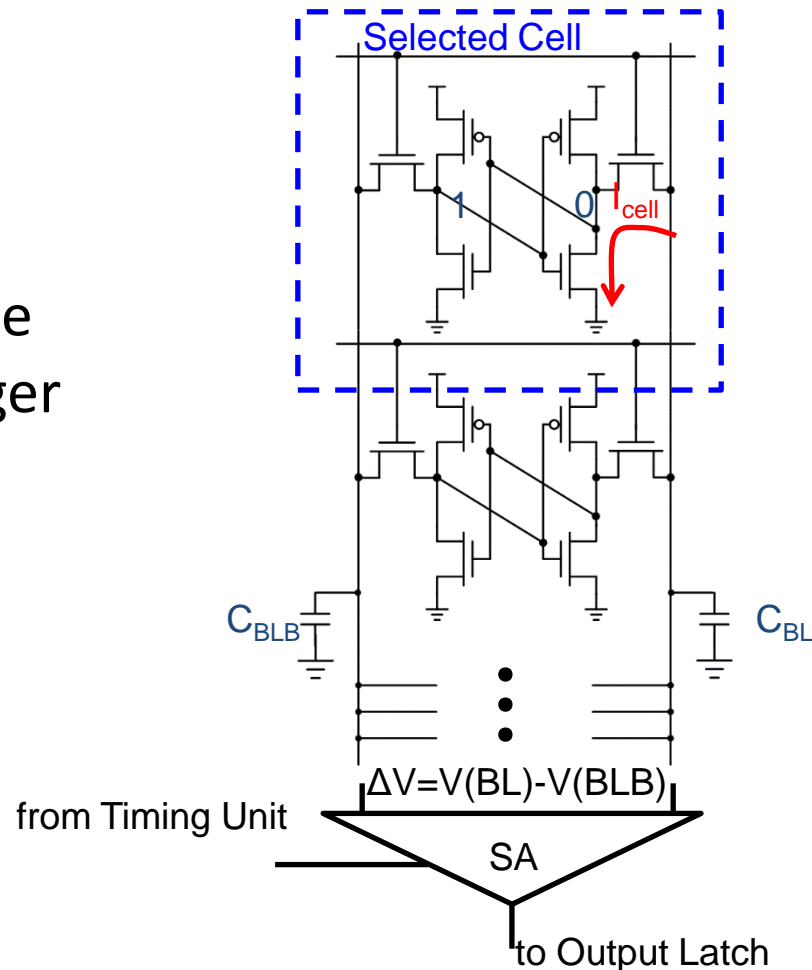- $\Delta V$ : The difference voltage between BL and BLB, larger than the offset voltage ( $V_{offset}$ ) of SA
- $I_{cell}$ : Cell Read current



# SRAM Cell

---

- What we care
  - ◆ Read/write operation
  - ◆ Stability of hold/read/write
  - ◆ Cell size


# Conflicting Read/Write Requirements

- To facilitate Read and minimize Read-disturb ( $V_{\text{READ}}$ )
  - ◆ Strong PD NMOS and weak AX NMOS (small  $\beta_2$ )
- To improve Write-ability (Write margin)
  - ◆ Strong AX NMOS and weak PUP PMOS (large  $\beta_3$ )

$$\frac{I_{\text{PUP}}}{I_{\text{HD}}} \sim \beta_1 = \frac{\mu_p (W/L)_{\text{PUP}}}{\mu_n (W/L)_{\text{HD}}} \Rightarrow V_{\text{TRIP}}$$


$$\frac{I_{\text{AX}}}{I_{\text{HD}}} \sim \beta_2 = \frac{\mu_n (W/L)_{\text{AX}}}{\mu_n (W/L)_{\text{HD}}} \Rightarrow V_{\text{READ}}$$
 
$$\frac{I_{\text{AX}}}{I_{\text{PUP}}} \sim \beta_3 = \frac{\mu_n (W/L)_{\text{AX}}}{\mu_p (W/L)_{\text{PUP}}} \Rightarrow T_{\text{WRITE}}$$





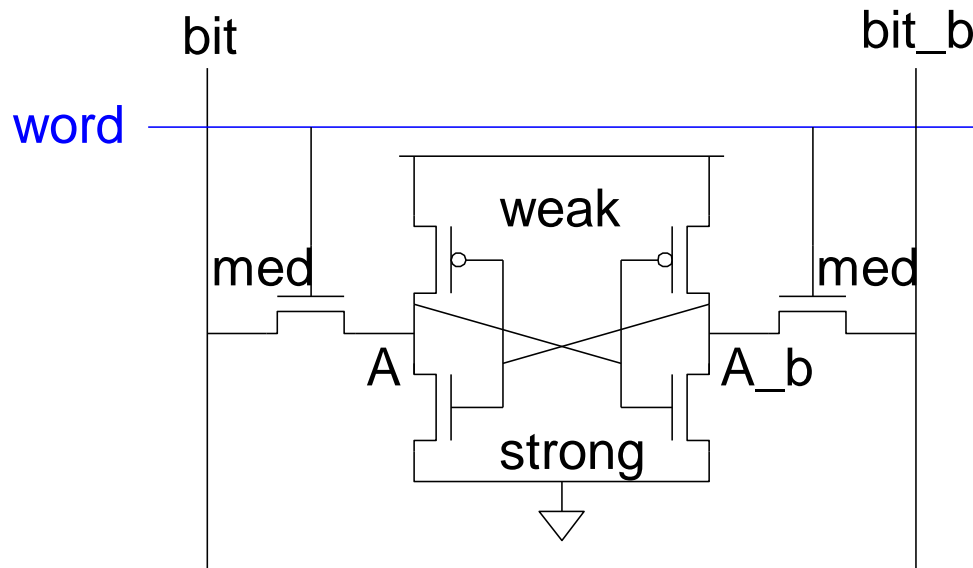
# SRAM Sizing

- High bitlines must not overpower inverters during reads
- But low bitlines must write new value into cell


 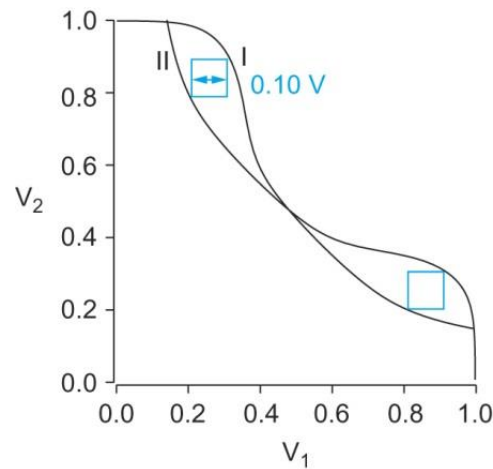 
# Cell Stability




- Hold margin
- Read margin
- Write margin





   
# SRAM Layout

- Tile cells sharing  $V_{DD}$ , GND, bitline contacts


 
# Thin Cell

- In nanometer CMOS
  - ◆ Avoid bends in polysilicon and diffusion
  - ◆ Orient all transistors in one direction
- *Lithographically friendly or thin cell* layout fixes this
  - ◆ Also reduces length and capacitance of bitlines
    - Diffusion run vertically, poly run horizontally




# Commercial SRAMs


- Five generations of Intel SRAM cell micrographs
- ◆ Transition to thin cell at 65 nm
- ◆ Steady scaling of cell area




130 nm [Tyagi00]

 


90 nm [Thompson02]

 

65 nm [Bai04]

 


45 nm [Mistry07]

 


32 nm [Natarajan08]

1  $\mu\text{m}$

 

 
# FinFET SRAM


- In FinFET, the width which is given by  $W = (T_{\text{FIN}} + 2H_{\text{FIN}}) \times N_{\text{FIN}}$  is quantized.
- For a high-density FinFET 6T-SRAM cell and a high-performance FinFET 6T-SRAM cell, the width ratio of Pull-Up PMOS, pass-gate NMOS and Pull-down NMOS are 1:1:1 and 1:2:2, respectively



# Memory Architecture: Decoders

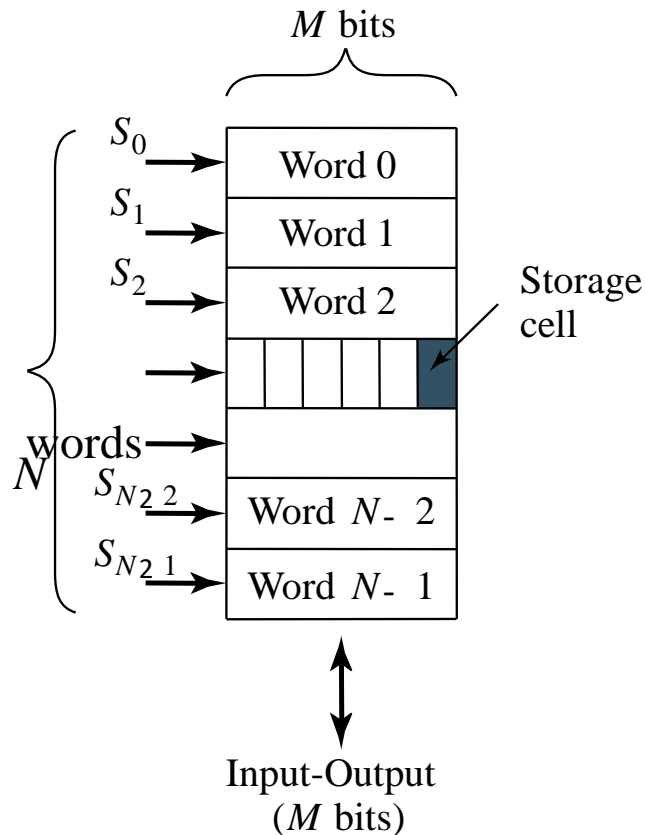

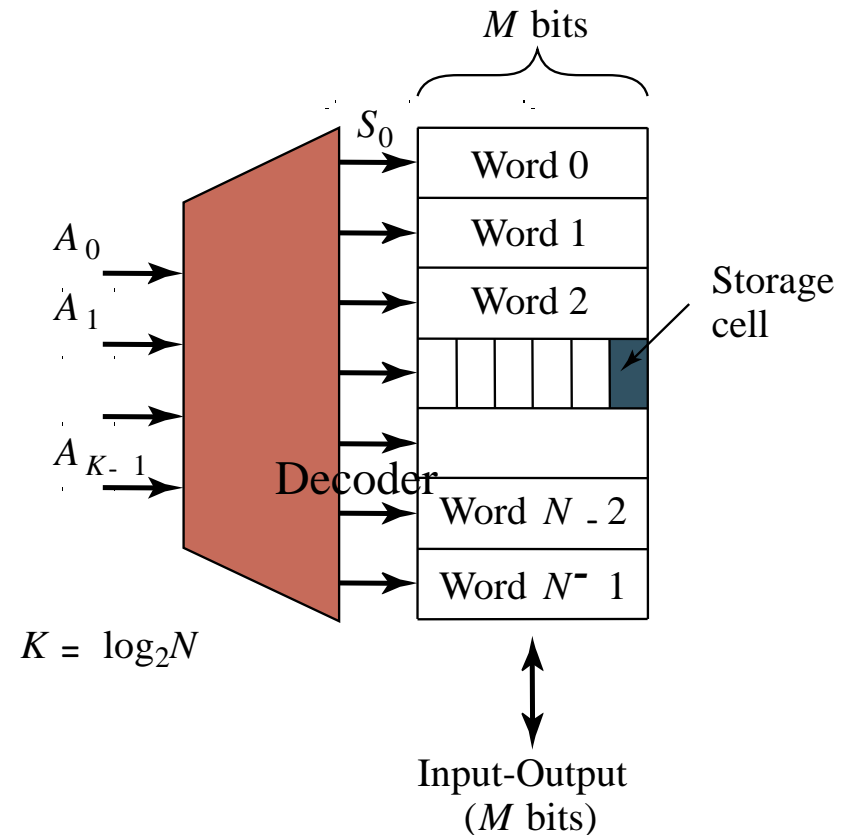
Intuitive architecture for  $N \times M$  memory  
 Too many select signals:  
 $N$  words ==  $N$  select signals



Decoder reduces the number of select signals  
 $K = \log_2 N$

 
# Decoder Layout

- Decoders must be *pitch-matched* to SRAM cell
- ◆ Requires very skinny gates



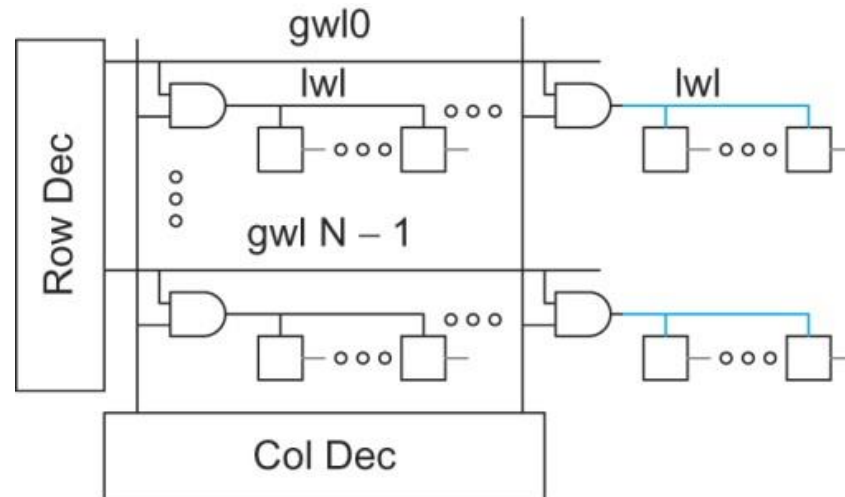
# Address Decoders

- What we care
  - ◆ Layout match with SRAM cells
  - ◆ How to handle large address
    - Predecoding
    - Row/Column address
      - See large SRAM
    - Hierarchical word lines


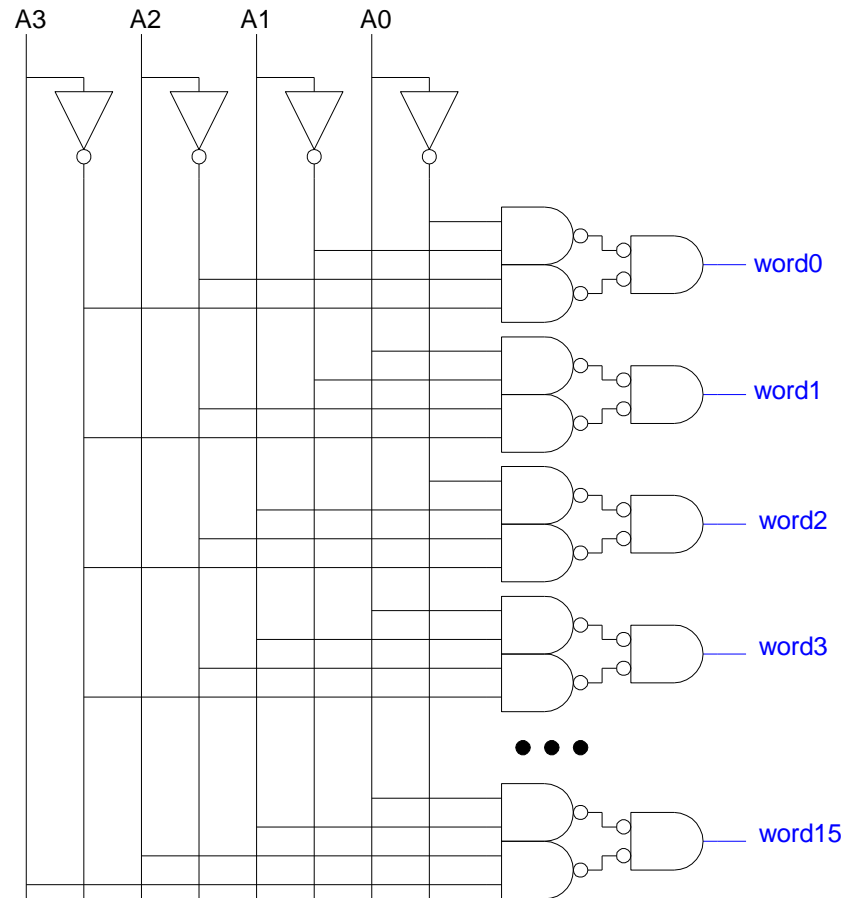
# Large Decoders

- For  $n > 4$ , NAND gates become slow
- ◆ Break large gates into multiple smaller gates






# Predecoding

■ Many of these gates are redundant

◆ Factor out common gates into predecoder


◆ Saves area

◆ Same path effort

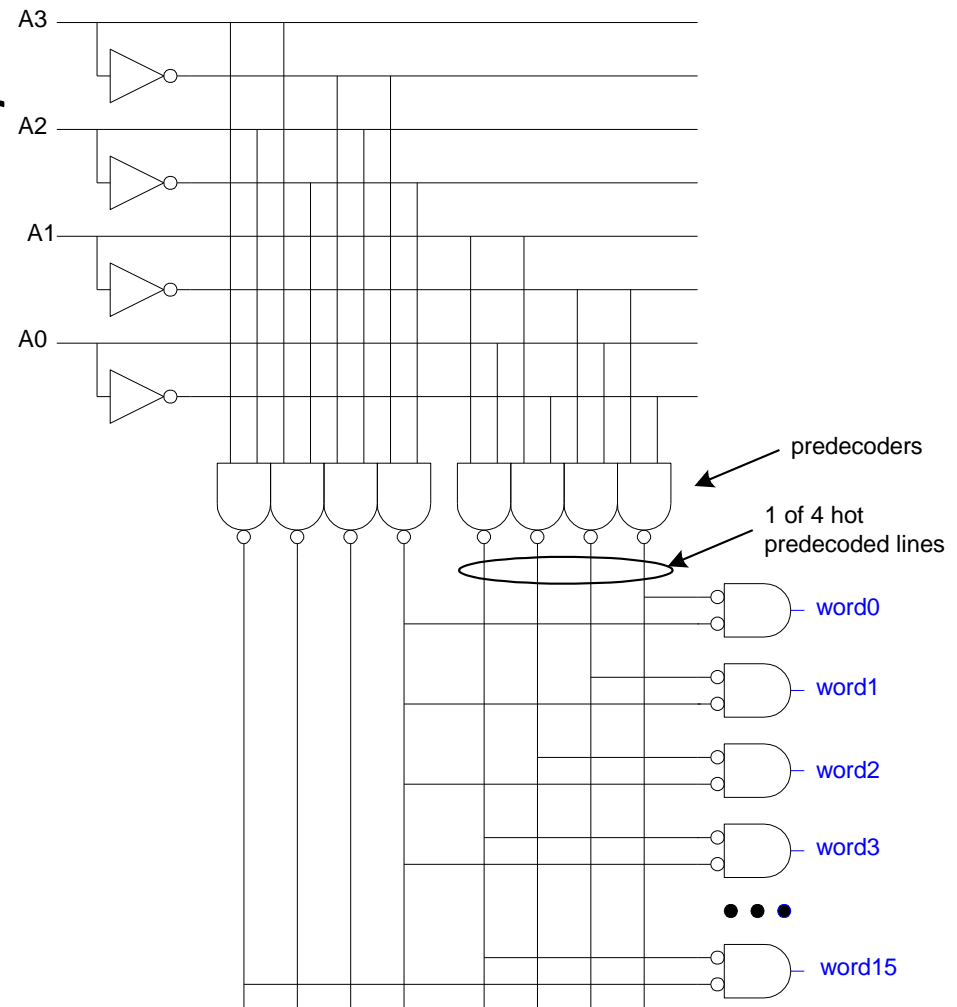
 
# Column Circuitry

- Some circuitry is required for each column
  - ◆ Bitline conditioning
  - ◆ Sense amplifiers
  - ◆ Column multiplexing



# Sense Amplifiers


$$t_p = \frac{C \times \Delta V}{I_{av}}$$

make  $\Delta V$  as small as possible

large

small

Idea: Use Sense Amplifier

 

# Sense Amplifiers

---

- Bitlines have many cells attached
  - ◆ Ex: 32-kbit SRAM has 128 rows x 256 cols
  - ◆ 128 cells on each bitline
- $t_{pd} \propto (C/I) \Delta V$ 
  - ◆ Even with shared diffusion contacts, 64C of diffusion capacitance (big C)
  - ◆ Discharged slowly through small transistors (small I)
- *Sense amplifiers* are triggered on **small voltage swing** (reduce  $\Delta V$ )


# Column Multiplexing

---

- Recall that array may be folded for good aspect ratio
- Ex: 2 kword x 16 folded into 256 rows x 128 columns
  - ◆ Must select 16 output bits from the 128 columns
  - ◆ Requires 16 8:1 column multiplexers

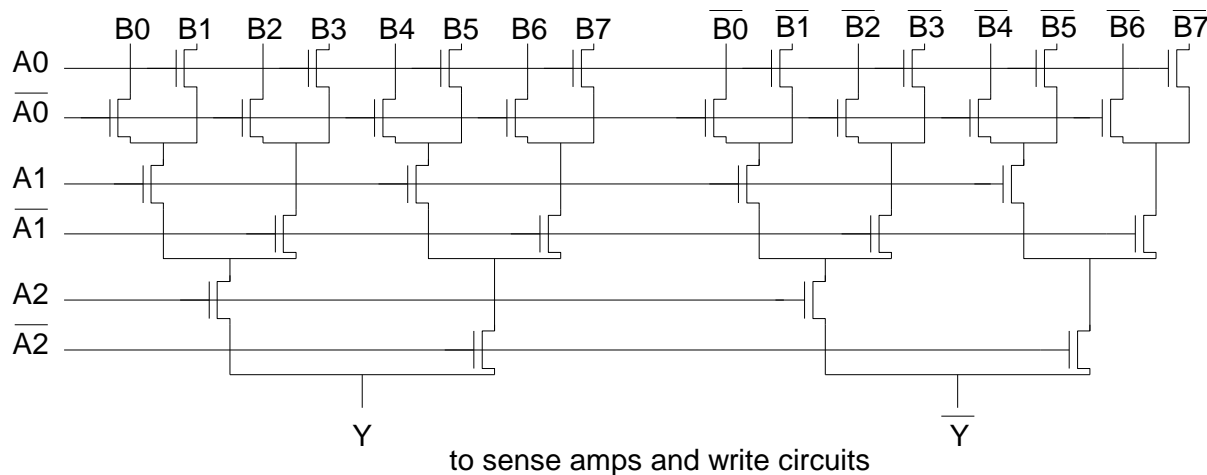
# Tree Decoder Mux

- Column mux can use pass transistors
  - ◆ Use nMOS only, precharge outputs
- One design is to use k series transistors for  $2^k:1$  mux
  - ◆ No external decoder logic needed



 
# Single Pass-Gate Mux

- Or eliminate series transistors with separate decoder



## Ex: 2-way Muxed SRAM

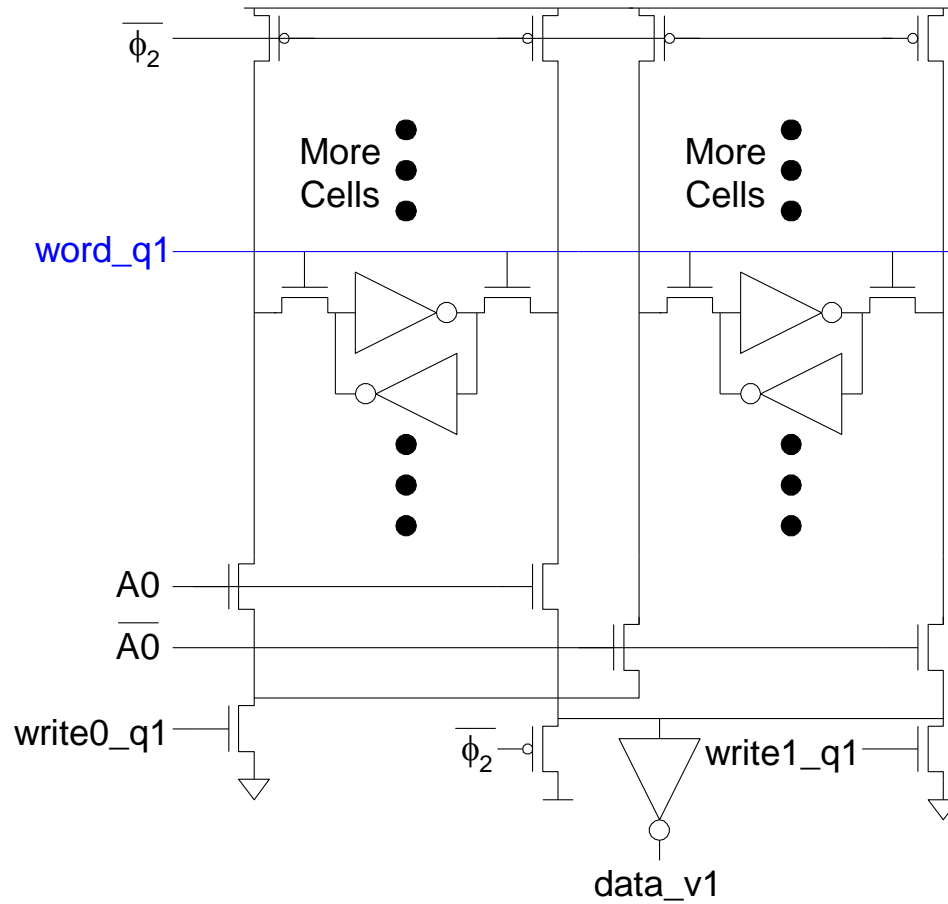



# Multiple Ports

---


- We have considered single-ported SRAM
  - ◆ One read or one write on each cycle
- *Multiported* SRAM are needed for **register files**
- Examples:
  - ◆ Multicycle MIPS must read two sources or write a result on some cycles
  - ◆ Pipelined MIPS must read two sources and write a third result each cycle
  - ◆ Superscalar MIPS must read and write many sources and results each cycle

# Dual-Ported SRAM

---
 
## ■ Simple dual-ported SRAM

- ◆ Two independent single-ended reads
- ◆ Or one differential write




## ■ Do two reads and one write by time multiplexing

- ◆ Read during ph1, write during ph2

 
# Multi-Ported SRAM (Register File)

- Adding more access transistors hurts read stability
- Multiported SRAM isolates reads from state node
- Single-ended bitlines save area






# Array-Structured Memory Architecture

 Problem: ASPECT RATIO or HEIGHT  $\gg$  WIDTH




# Embedded DRAM

- Logic process
- 3T or 4T cells

   


## Read-Only Memory (ROM)

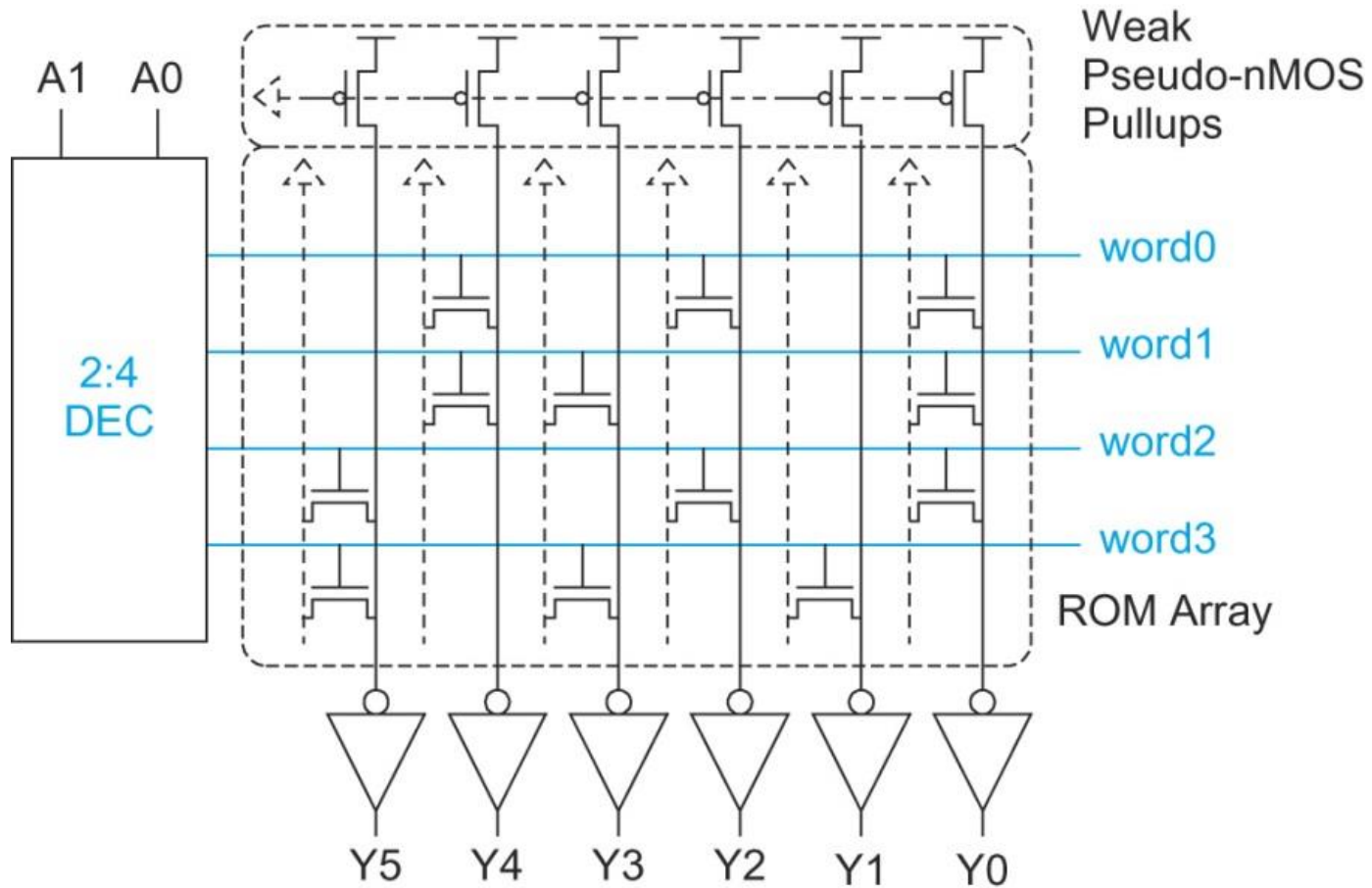


# Non-Volatile Memories

## Flash - floating-gate transistor

 


Device cross-section

 


Schematic symbol


# Floating-Gate Transistor Programming

 

Avalanche injection

 

 Removing programming voltage leaves charge trapped



Programming results in higher  $V_T$ .



# Serial Access Memories


---

- Serial access memories do not use an address
  - ◆ Shift Registers
  - ◆ Tapped Delay Lines
  - ◆ Serial In Parallel Out (SIPO)
  - ◆ Parallel In Serial Out (PISO)
  - ◆ Queues (FIFO, LIFO)
 
# Queues

---


- Queues allow data to be read and written at different rates.
- Read and write each use their own clock, data
- Queue indicates whether it is full or empty
- Synchronous, semi-synchronous, asynchronous


 
# Shift Register


---

- *Shift registers* store and delay data
- Simple design: cascade of registers
- ◆ Watch your hold times!



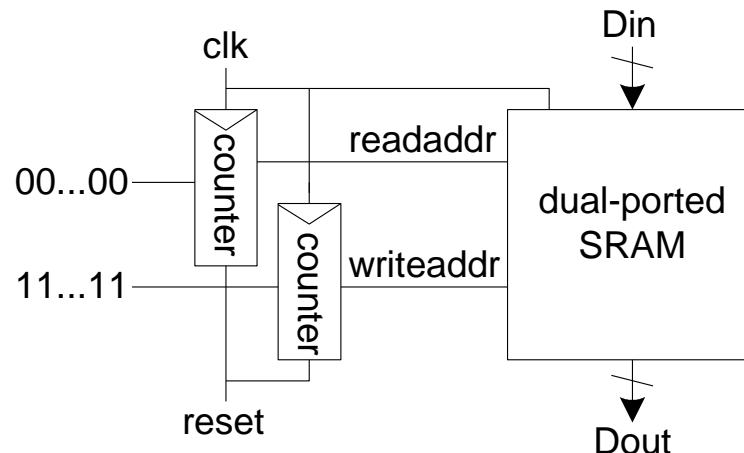
# Denser Shift Registers

- Flip-flops aren't very area-efficient
- For large shift registers, keep data in SRAM instead
- Move read/write pointers to RAM rather than data
  - ◆ Initialize read address to first entry, write to last
  - ◆ Increment address on each cycle


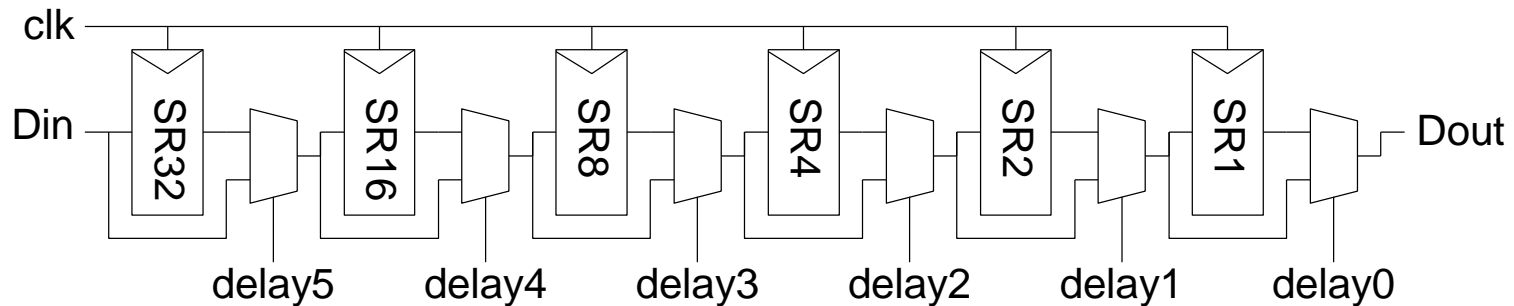
# Tapped Delay Line


- A *tapped delay line* is a shift register with a programmable number of stages
- Set number of stages with delay controls to mux
- ◆ Ex: 0 – 63 stages of delay


 
# Serial In Parallel Out


---

- 1-bit shift register reads in serial data
- ◆ After N steps, presents N-bit parallel output


 
# Parallel In Serial Out


- Load all N bits in parallel when shift = 0
- ◆ Then shift one bit out per cycle


 
# Queues

---

- *Queues* allow data to be read and written at different rates.
- Read and write each use their own clock, data
- Queue indicates whether it is full or empty
- Build with SRAM and read/write counters (pointers)





# FIFO, LIFO Queues

---

## ■ *First In First Out (FIFO)*


- ◆ Initialize read and write pointers to first element
- ◆ Queue is EMPTY
- ◆ On write, increment write pointer
- ◆ If write almost catches read, Queue is FULL
- ◆ On read, increment read pointer

## ■ *Last In First Out (LIFO)*


- ◆ Also called a *stack*
- ◆ Use a single *stack pointer* for read and write
 
# Implementation for Short-Depth Queues

- Register-based FIFO for short-depth queues
  - ◆ Shift-in shift-out FIFO




- ◆ Bus-in shift-out FIFO

 

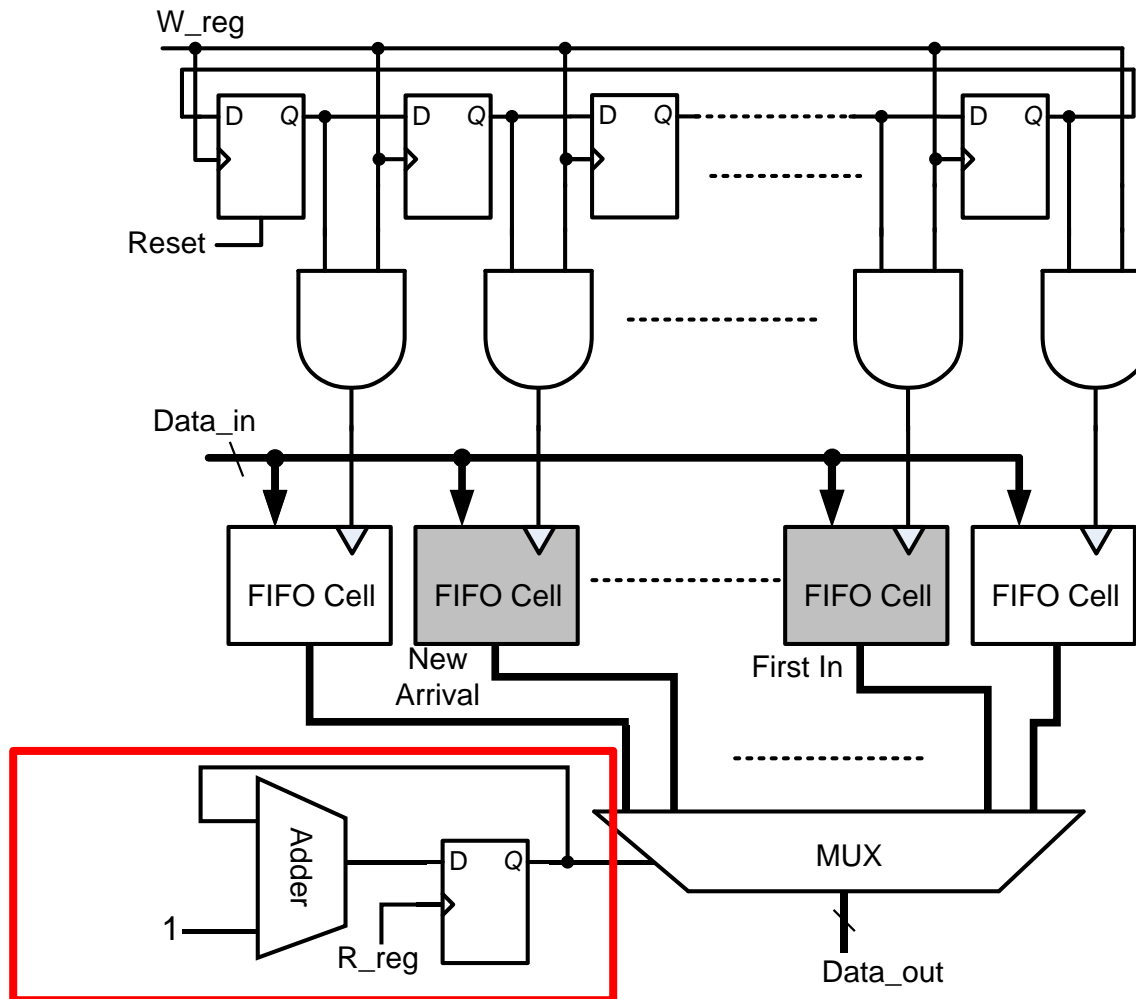
# Bus-In Mux-Out Register-Based FIFO

- Read pointer for read token
- Complex wire routing



 
# Bus-In Bus-Out Register-Based FIFO

- Registers for Read/write tokens
- Large capacitance on I/Os




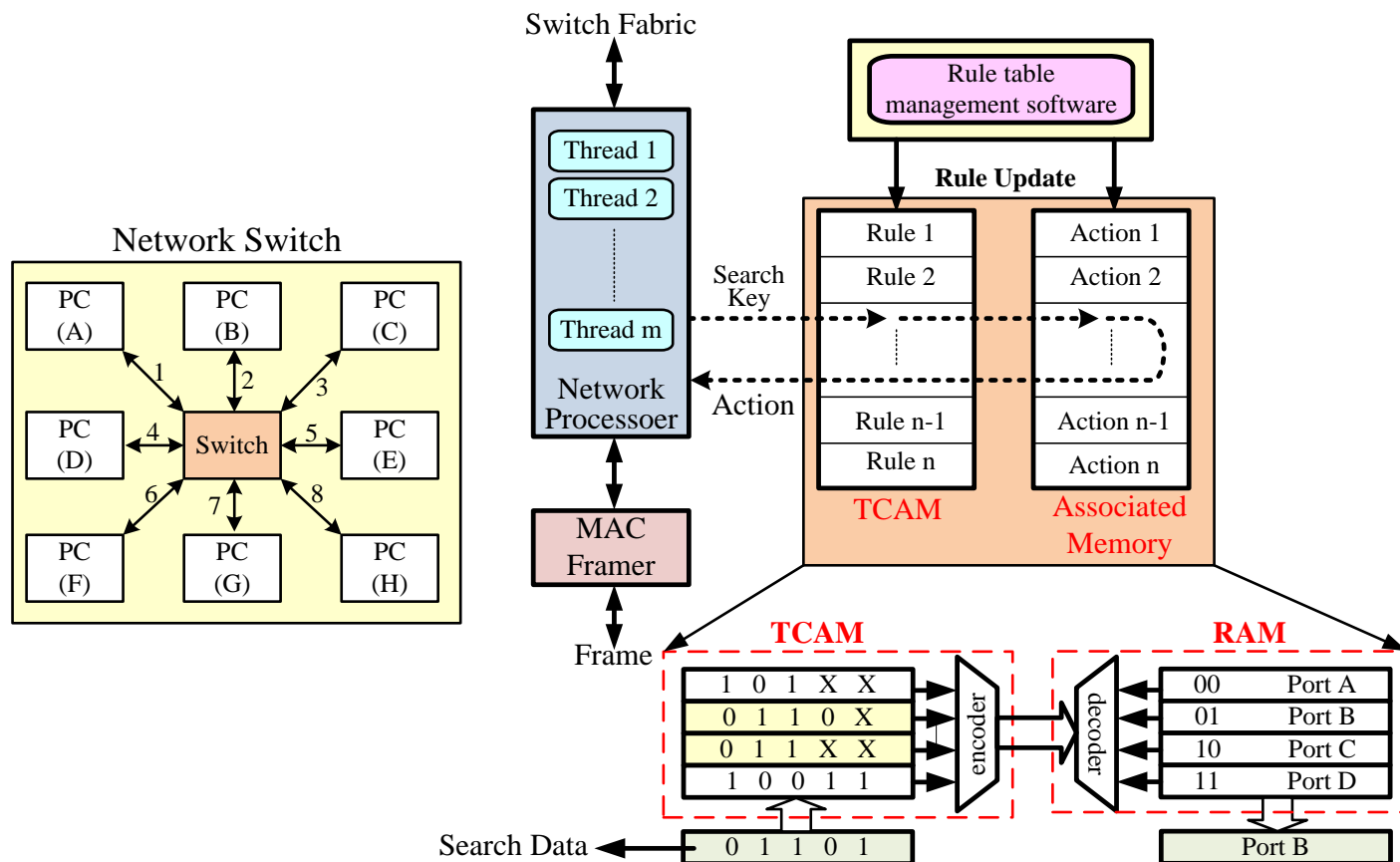
# Introduction to CAM/TCAM

- Applications: lookup table
  - ◆ Great amounts of XORs
- Binary CAM and Ternary CAM (TCAM)


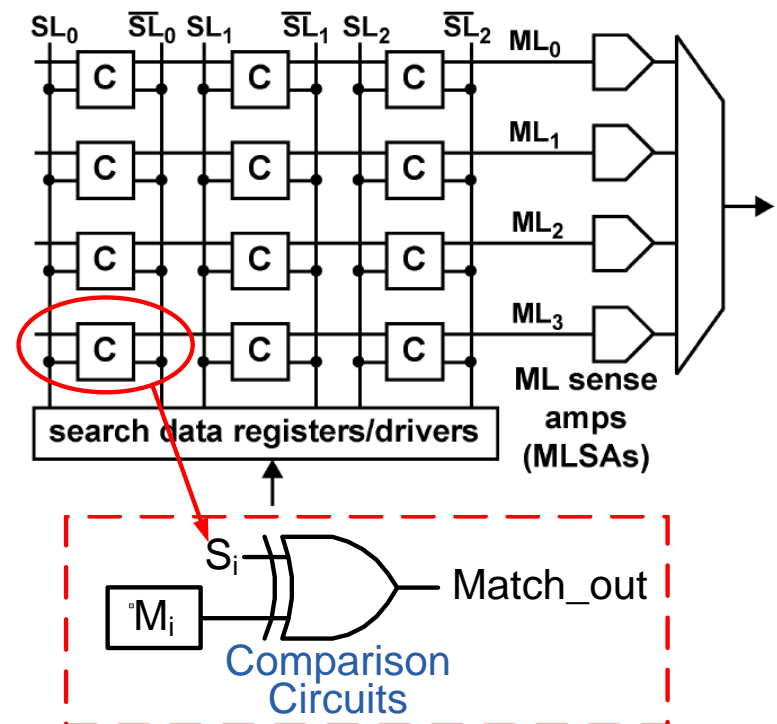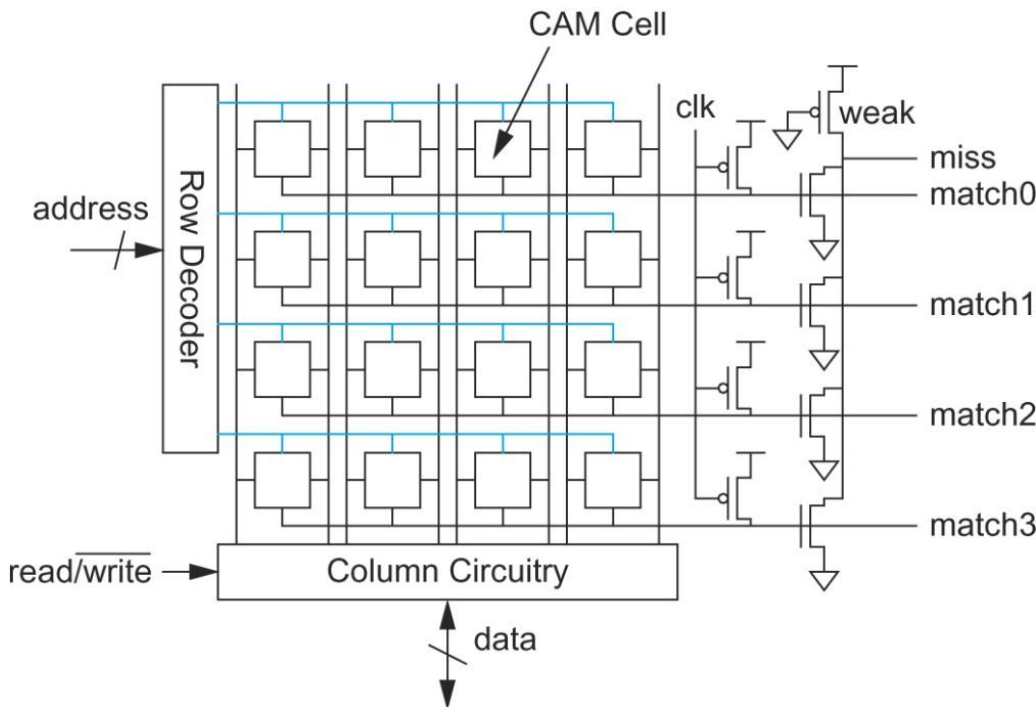
# CAM Array


- Vertical lines: search-lines, bit-lines
- Horizontal lines: word-lines, match-lines
- Operation: Write, read, **search**




# Match-line schemes for CAM

## ■ Match-line: match/mismatch collection

### NOR-type match-line scheme

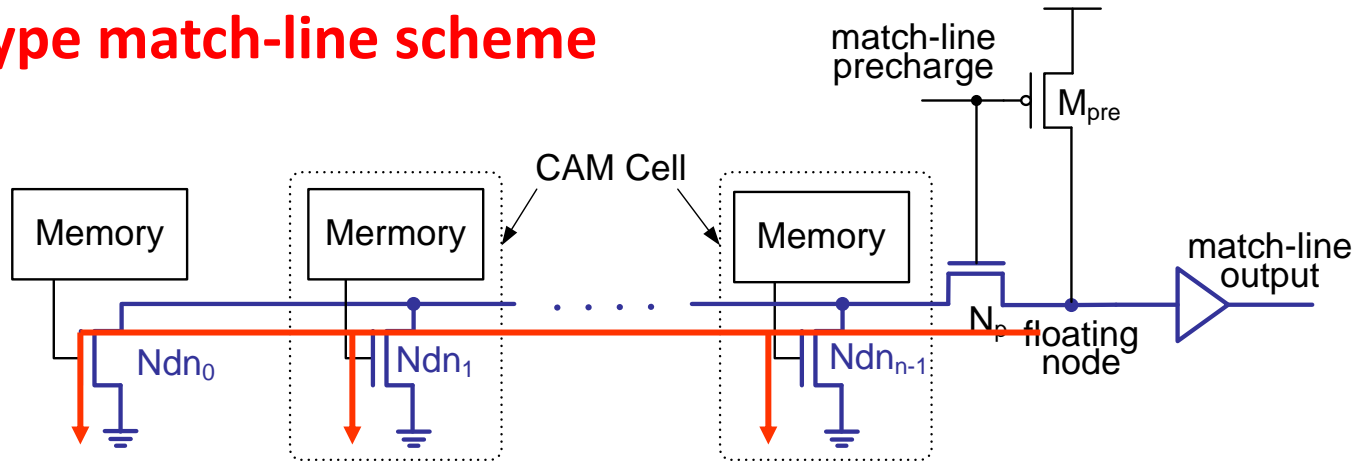


### AND-type match-line scheme

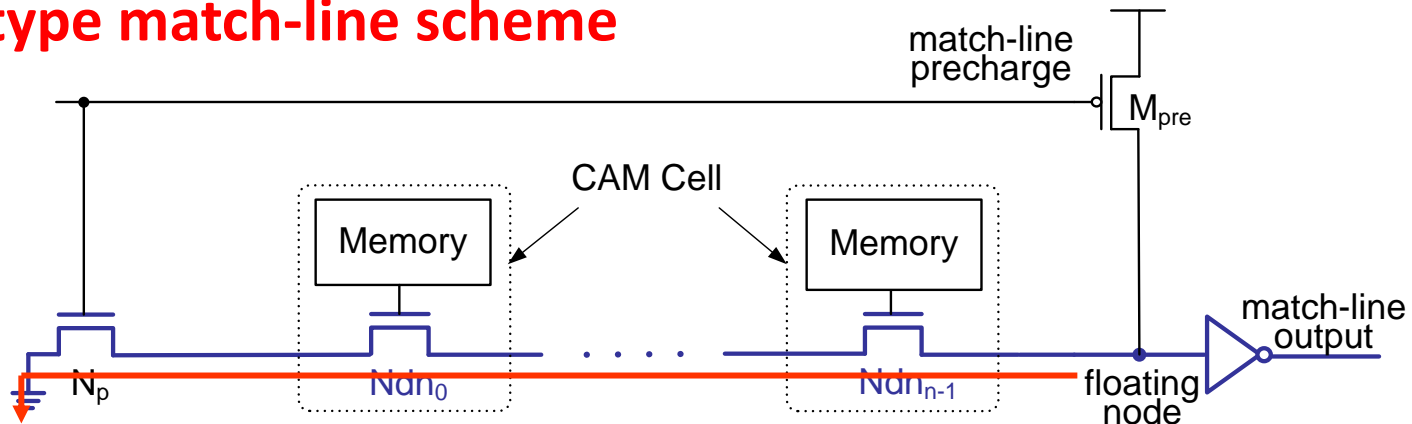


# Operation of Binary CAM cell

## ◆ NOR-type CAM

| State    | $Q_i$ | SL | ML       |
|----------|-------|----|----------|
| Zero (0) | 0     | 0  | floating |
|          | 0     | 1  | 0        |
| One (1)  | 1     | 0  | 0        |
|          | 1     | 1  | floating |

 


9T NOR

 


10T NOR

## ◆ AND-type CAM

| State    | $Q_i$ | SL | ML       |
|----------|-------|----|----------|
| Zero (0) | 0     | 0  | 0        |
|          | 0     | 1  | floating |
| One (1)  | 1     | 0  | floating |
|          | 1     | 1  | 0        |

 

9T NAND

 


10T NAND



# Operations of Binary CAM cell

## ◆ NOR-type TCAM

| State          | $Q_i$ | $Q_j$ | SL | ML       |
|----------------|-------|-------|----|----------|
| Zero (0)       | 0     | 1     | 0  | floating |
|                | 0     | 1     | 1  | 0        |
| One (1)        | 1     | 0     | 0  | 0        |
|                | 1     | 0     | 1  | floating |
| Don't Care (X) | 0     | 0     | 0  | floating |
|                | 0     | 0     | 1  | floating |
| Not Allowed    | 1     | 1     | 0  | —        |
|                | 1     | 1     | 1  | —        |

 

## ◆ AND-type TCAM

| State          | $Q_i$ | $Q_j$ | SL | ML       |
|----------------|-------|-------|----|----------|
| Zero (0)       | 0     | 0     | 0  | 0        |
|                | 0     | 0     | 1  | floating |
| One (1)        | 1     | 0     | 0  | floating |
|                | 1     | 0     | 1  | 0        |
| Don't Care (X) | 0     | 1     | 0  | 0        |
|                | 0     | 1     | 1  | 0        |
|                | 1     | 1     | 0  | 0        |
|                | 1     | 1     | 1  | 0        |

