

Digital IC Design

Lecture 5:

Sequential Circuits

黃柏蒼 Po-Tsang (Bug) Huang

bughuang@nycu.edu.tw

International College of Semiconductor Technology
National Chiao Tung Yang Ming University

國立陽明交通大學

NATIONAL YANG MING CHIAO TUNG UNIVERSITY


Sequencing

■ *Combinational logic*

- ◆ output depends on **current (present) inputs**

■ *Sequential logic*

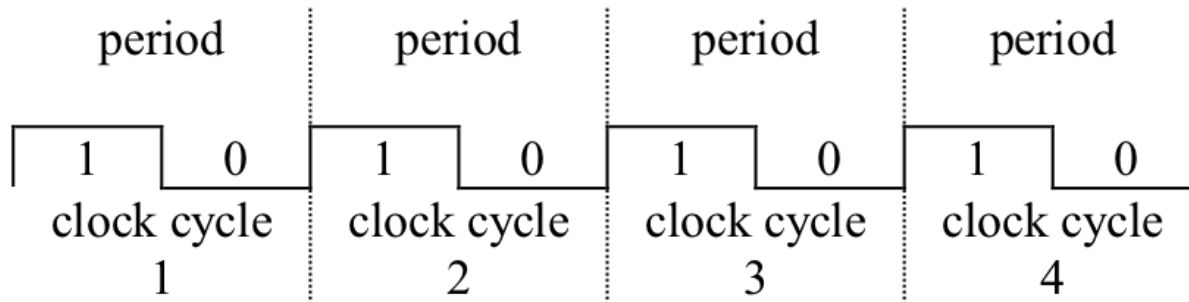- ◆ *output depends on* **current** and **previous inputs**
- ◆ Requires separating previous, current, future
- ◆ Called state or tokens
- ◆ Circuit “**remembers**” previous history using
 - **Flip-Flop (F/F) or latch related with a reference clock signal**




Synchronous circuits


Sequential Logic

■ Sequential finite state machine(FSM)

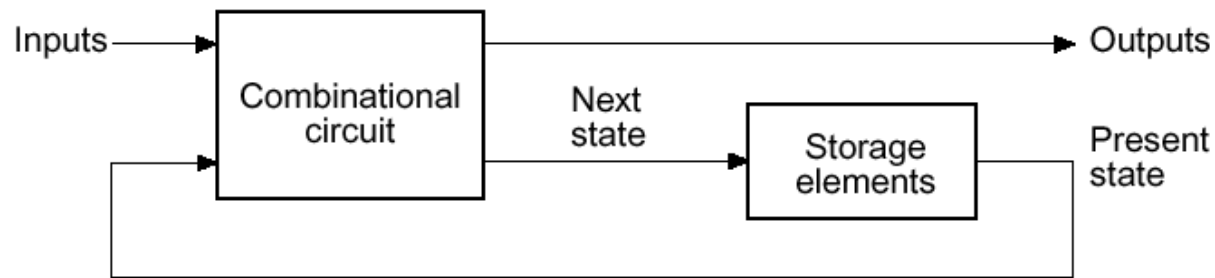- ◆ Output depends not only on current input but also on past input values, e.g., design a counter
- ◆ Need some type of memory to remember the past input values



■ Sequential pipeline

 


Finite State Machine

Pipeline


Sequential Logic: Concept

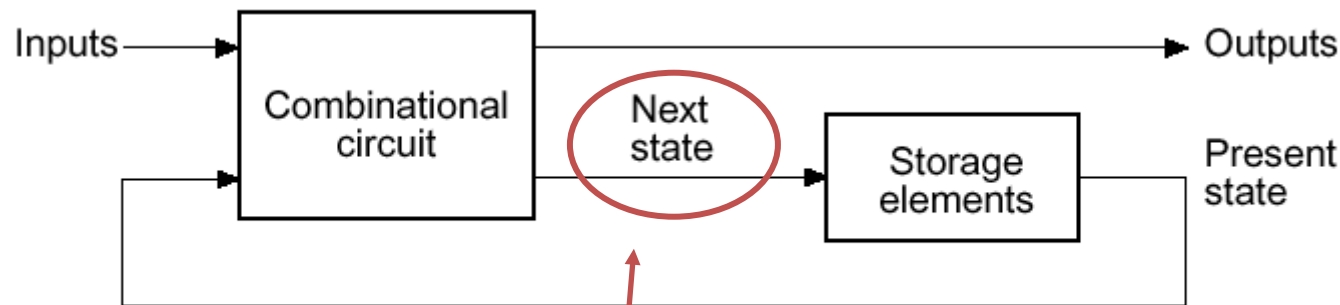- Sequential Logic circuits remember past inputs and past circuit state.
- Outputs from the system are “feedback” as new inputs
 - ◆ With gate delay and wire delay
- The storage elements are circuits that are capable of storing binary information: memory.



Timed "States"

Performance of Combinational Circuits

 


For combinational logic:

$$L = t_{PD},$$

$$T = 1/t_{PD}.$$

 
We can't get the answer faster, but are we making effective use of our hardware at all times?



F & G are "idle", just holding their outputs stable while H performs its computation

Pipeline diagrams

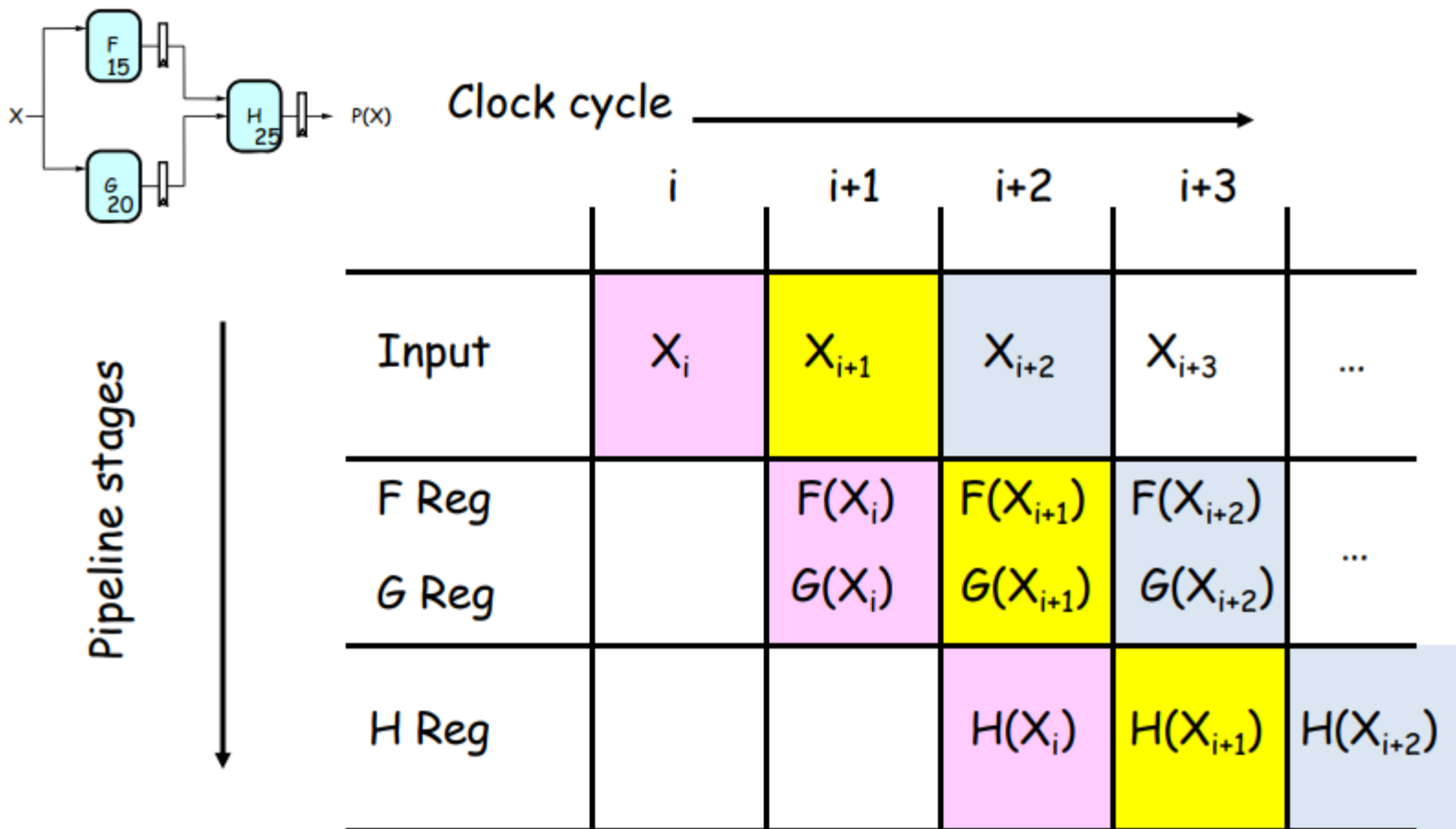- The results associated with a particular set of input data moves diagonally through the diagram, progressing through one pipeline stage each clock cycle




Pipeline Conventions

■ DEFINITION:

- ◆ a K-Stage Pipeline (“K-pipeline”) is an acyclic circuit having exactly K registers on every path from an input to an output.
- ◆ a COMBINATIONAL CIRCUIT is thus an 0-stage pipeline.

Synchronous & Asynchronous

SYNCHRONOUS

 

ASYNCHRONOUS



BRYAN CHRISTIE DESIGN

Synchronous vs. Asynchronous

■ Synchronous Circuit


1. Use an external global **clock** to separate consecutive system states from each other
2. *Time Domain* : Assert signals at a specific time, and for a specific duration

■ Asynchronous Circuit

 
1. Define system states in terms of internal and external **events** (signal transitions)
2. Sequence Domain: Assert a signal after some event and holds the value until some other event
3. Use **handshakes** between system components to ensure correct sequencing of events (instead of a global clock signal)

Sequencing Elements

- **Latch:** Level sensitive (Transparent)
 - ◆ a.k.a. transparent latch, D latch
- **Flip-flop:** edge-triggered
 - ◆ master-slave flip-flop, D flip-flop, pulsed latch




Timing of Sequencing Elements

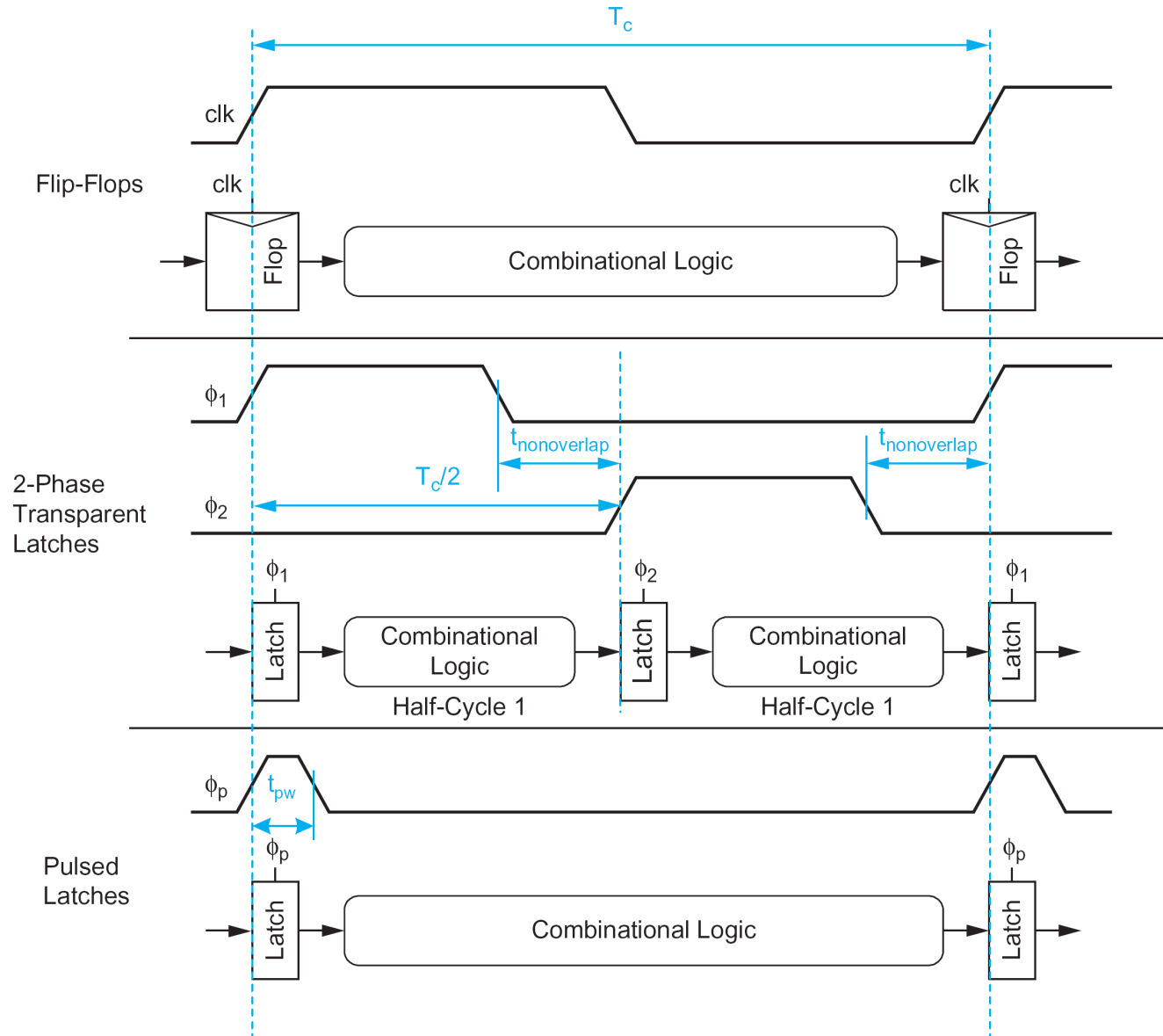

Relation between Latch & F/F

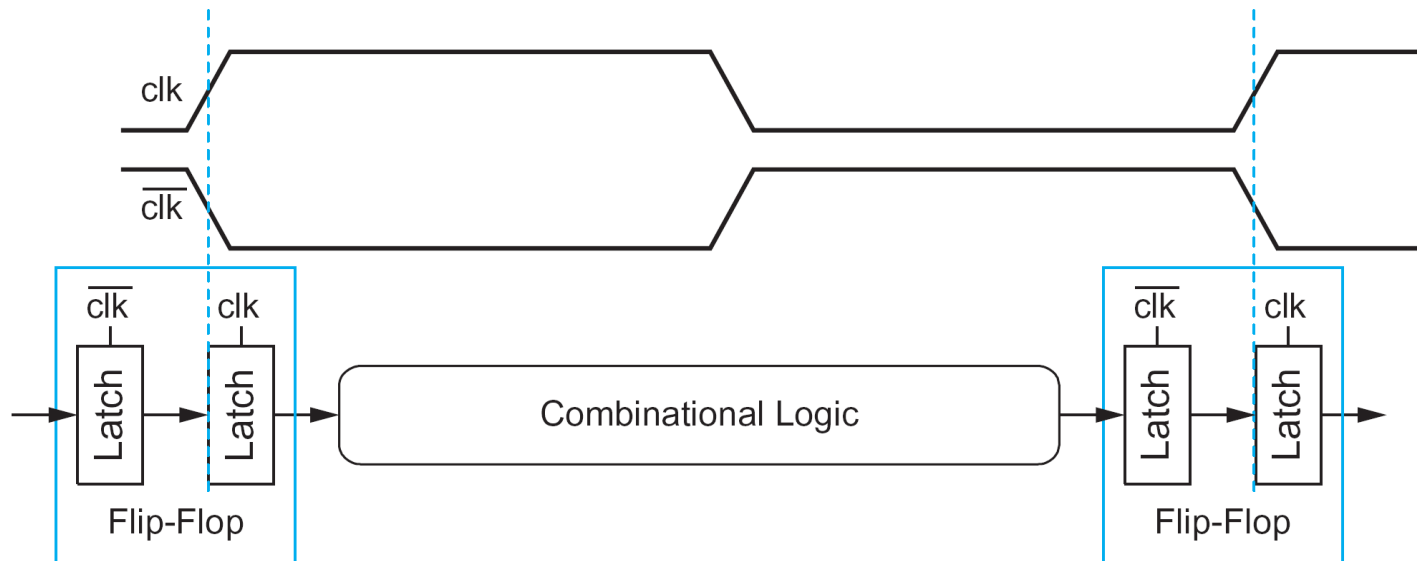- 2 level sensitive latches = 1 edge-triggered FF









- Pulsed latch is similar to a F/F
 - ◆ Duty cycle is approached to 0% or 100%







Definition of Timing issues in Sequencing

Contamination and Propagation Delays

t_{pd}	Logic Prop. Delay
t_{cd}	Logic Cont. Delay
t_{pcq}	Latch/Flop Clk->Q Prop. Delay
t_{ccq}	Latch/Flop Clk->Q Cont. Delay
t_{pdq}	Latch D->Q Prop. Delay
t_{cdq}	Latch D->Q Cont. Delay
t_{setup}	Latch/Flop Setup Time
t_{hold}	Latch/Flop Hold Time

      


      Definition of Timing issues in Sequencing



Sequencing Elements

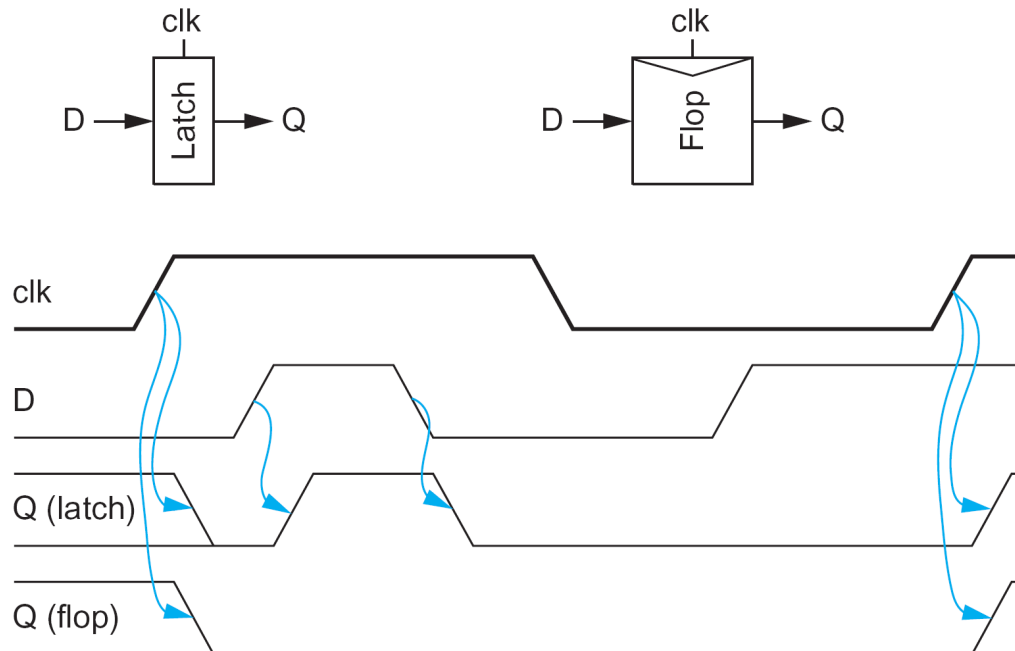- **Latch:** Level sensitive (Transparent)
 - ◆ a.k.a. transparent latch, D latch
- **Flip-flop:** edge-triggered
 - ◆ master-slave flip-flop, D flip-flop, pulsed latch



Static vs Dynamic Storage

■ Static storage

- ◆ preserve state as long as the power is on
- ◆ have positive feedback (**regeneration**) with an internal connection between the output and the input
- ◆ useful when updates are infrequent (clock gating)


■ Dynamic storage

- ◆ store state on parasitic capacitors
- ◆ only hold state for short periods of time (milliseconds)
- ◆ require periodic refresh
- ◆ usually simpler, so higher speed and lower power

Feedback of Odd and Even Inverters

- Timing in feedback network

One inversion (oscillatory)

 


(a) Inverter with feedback




(b) Oscillation at inverter output

Two inversions (stable)




 


(a)

 


(b)

Positive and Negative Latches

    

MUX Based Latches

 
- Change the stored value by cutting the feedback loop



Negative Latch

$$Q = \text{clk} \& Q \mid !\text{clk} \& D$$

transparent when the
clock is low

 

Positive Latch

$$Q = !\text{clk} \& Q \mid \text{clk} \& D$$

transparent when the
clock is high

Latch Design - Pass Transistor



■ Pass Transistor Latch

■ Pros

- ◆ Tiny
- ◆ Low clock load

■ Cons

  - ◆ V_t drop
- ◆ nonrestoring
- ◆ backdriving
- ◆ output noise sensitivity
- ◆ dynamic
- ◆ diffusion input





Requires inverted clock

Latch Design - Inverting buffer


■ Inverting buffer

  - + Restoring
- + No backdriving
- + Fixes either
 - Output noise sensitivity
 - Or diffusion input
- ◆ Inverted output




Latch Design - Tristate feedback

 - Tristate feedback + Static
 - ◆ Backdriving risk
- Static latches are now essential because of leakage




Latch Design - Buffered input

 - Buffered input
 - + Fixes diffusion input
 - + Noninverting





Latch Design - Buffered Output

 - Buffered output
 - + No backdriving
- Widely used in standard cells
 - + Very robust (most important)
 - Rather large
 - Rather slow (1.5 – 2 FO4 delays)
 - High clock loading






D Latch Design


- Multiplexer chooses D or old Q

  

D Latch Operation

  
 


SR Latch

 

S	R	Q	!Q	
0	0	Q	!Q	memory
1	0	1	0	set
0	1	0	1	reset
1	1	0	0	disallowed


Latch Race Problem

  

Which value of B is stored ?



D Flip-Flop

 - When CLK rises, D is copied to Q
- At all other times, Q holds its value
- a.k.a. *positive edge-triggered flip-flop, master-slave flip-flop*




D Flip-Flop Design

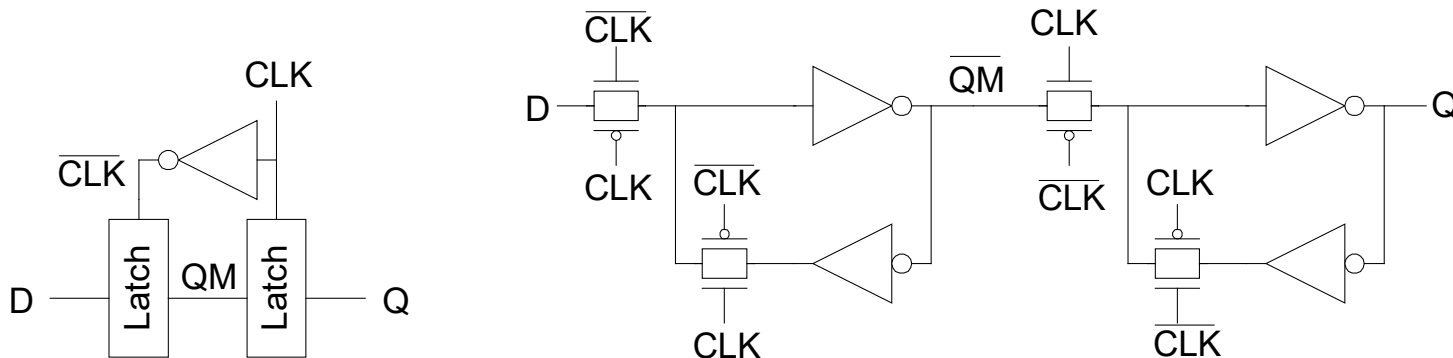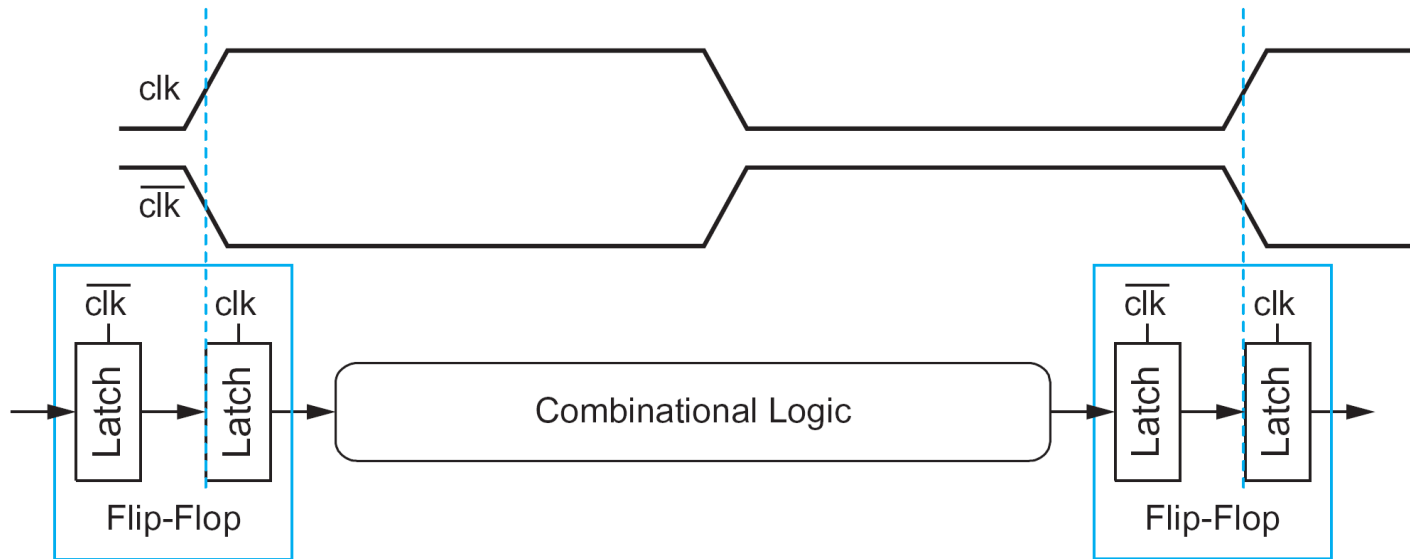- Flip-flop is built as pair of back-to-back latches
- Built from master and slave D latches



Master-Slave Edge-Triggered Flip-Flop

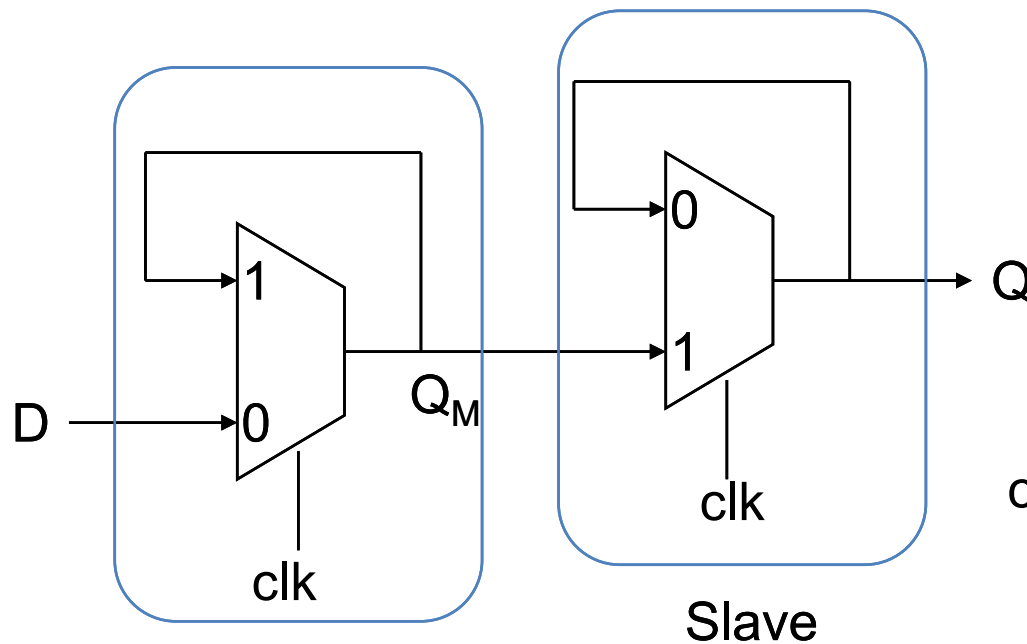

Master



Slave

clk = 0 transparent




hold

clk = 0 → 1 hold

transparent

  


D Flip-flop Operation

   

Timing Analysis-Timing of D Flip-Flop

- **Setup time (T_{setup}):** the time that the input signal must be stabilized before the clock edge.
- **Hold time (T_{hold}):** the time that the input signal must be stabilized after the clock edge.
- **Clk-to-Q contamination delay (T_{ccq}):** the contamination time that Q is first changed after the clock edge.
- **Clk-to-Q propagation delay (T_{pcq}):** the propagation time that Q reaches steady state after the clock edge.

 


Timing Analysis-Timing of D Flip-Flop

■ Static flip-flop

- ◆ **tsetup**: D -> inv1 -> inv2 -> inv3
- ◆ **thold**: TR1 (ON->OFF)
- ◆ **tpcq**: D_temp -> TR2 (OFF->ON) -> inv4 -> inv5 -> Q

Latch 1


Latch 2

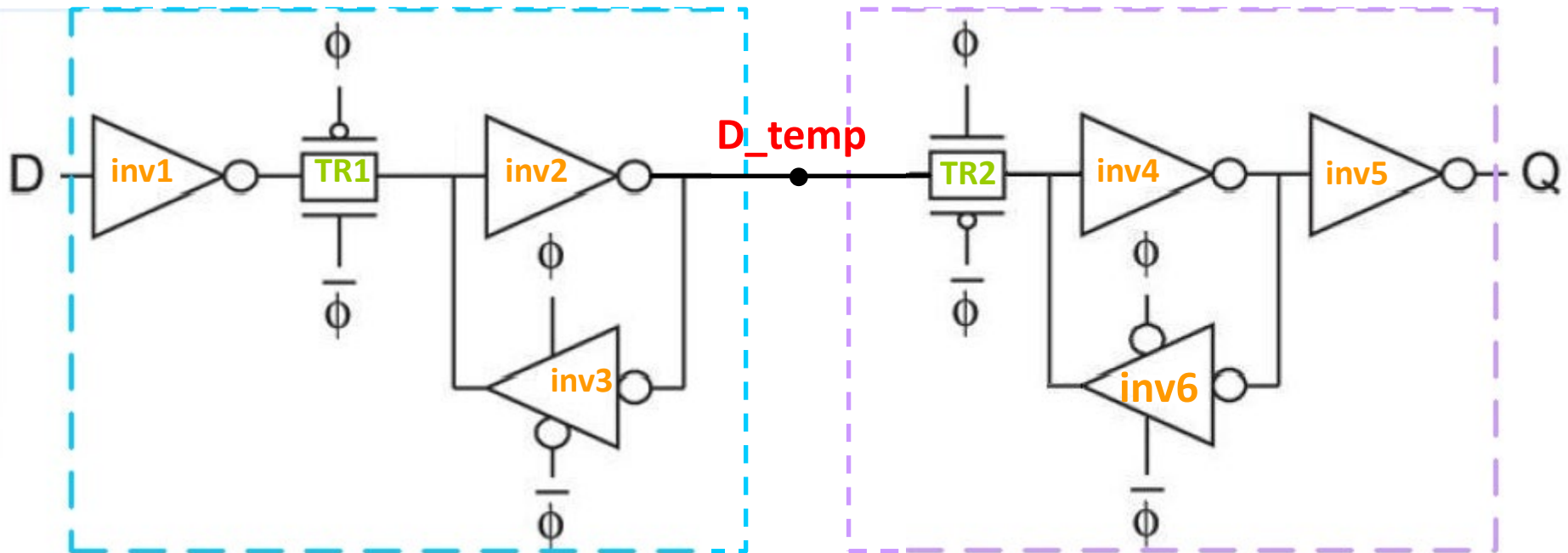



Determine the CLK-to-Q Delay

Race Condition

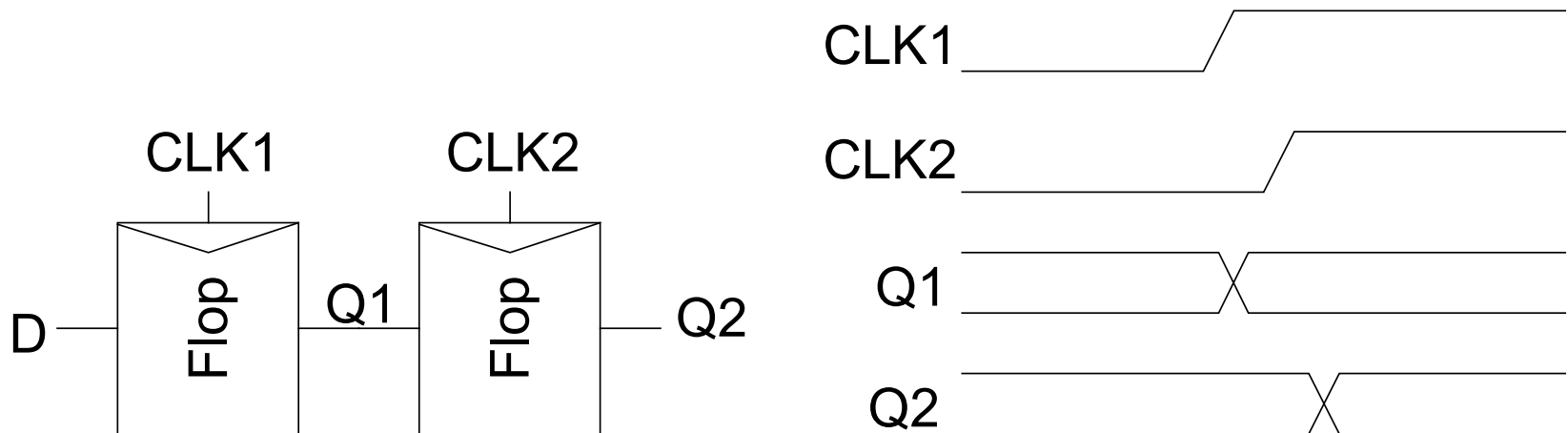- Back-to-back flops can malfunction from clock skew
 - ◆ Second flip-flop fires late
 - ◆ Sees first flip-flop change and captures its result
 - ◆ Called *hold-time failure* or *race condition*



Race Conditions in Dynamic FF

  

0-0 overlap race condition



$$t_{\text{overlap}0-0} < t_{T1} + t_{I1} + t_{T2}$$

1-1 overlap race condition

$$t_{\text{overlap1-1}} < t_{\text{hold}}$$


NORA Dynamic FF

- NORA – no racing


 
 


Nonoverlapping Clocks

 - Nonoverlapping clocks can prevent races
 - ◆ As long as nonoverlap exceeds clock skew
- We will use them in this class for safe design
 - ◆ Industry manages skew more carefully instead




Pulse Generator + Latch (Pulsed Latch)

  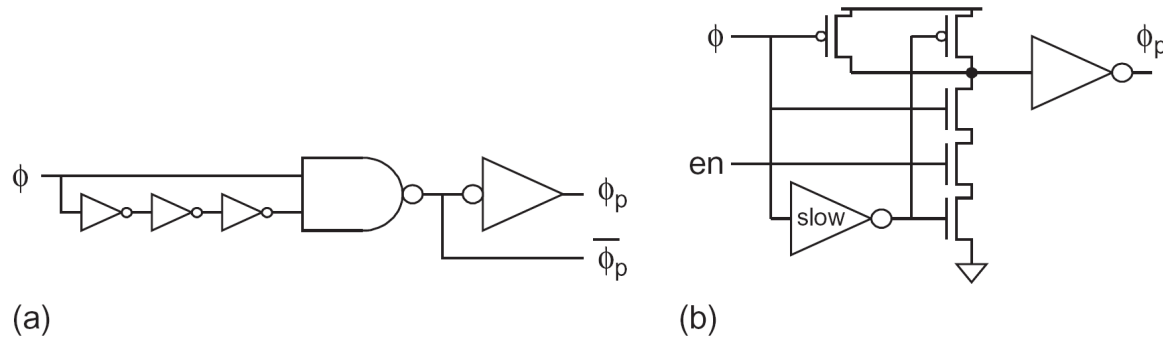

Pulsed Latch using Pulse Generators


 
- Pulsed generator + Latch = pulsed latch
- ◆ Edge-sensitive





Enable

- Enable: ignore clock when $en = 0$
 - ◆ Mux: increase latch D-Q delay
 - ◆ Clock Gating: increase en setup time, skew



Symbol

  

Multiplexer Design

  


Clock Gating Design

  


Reset

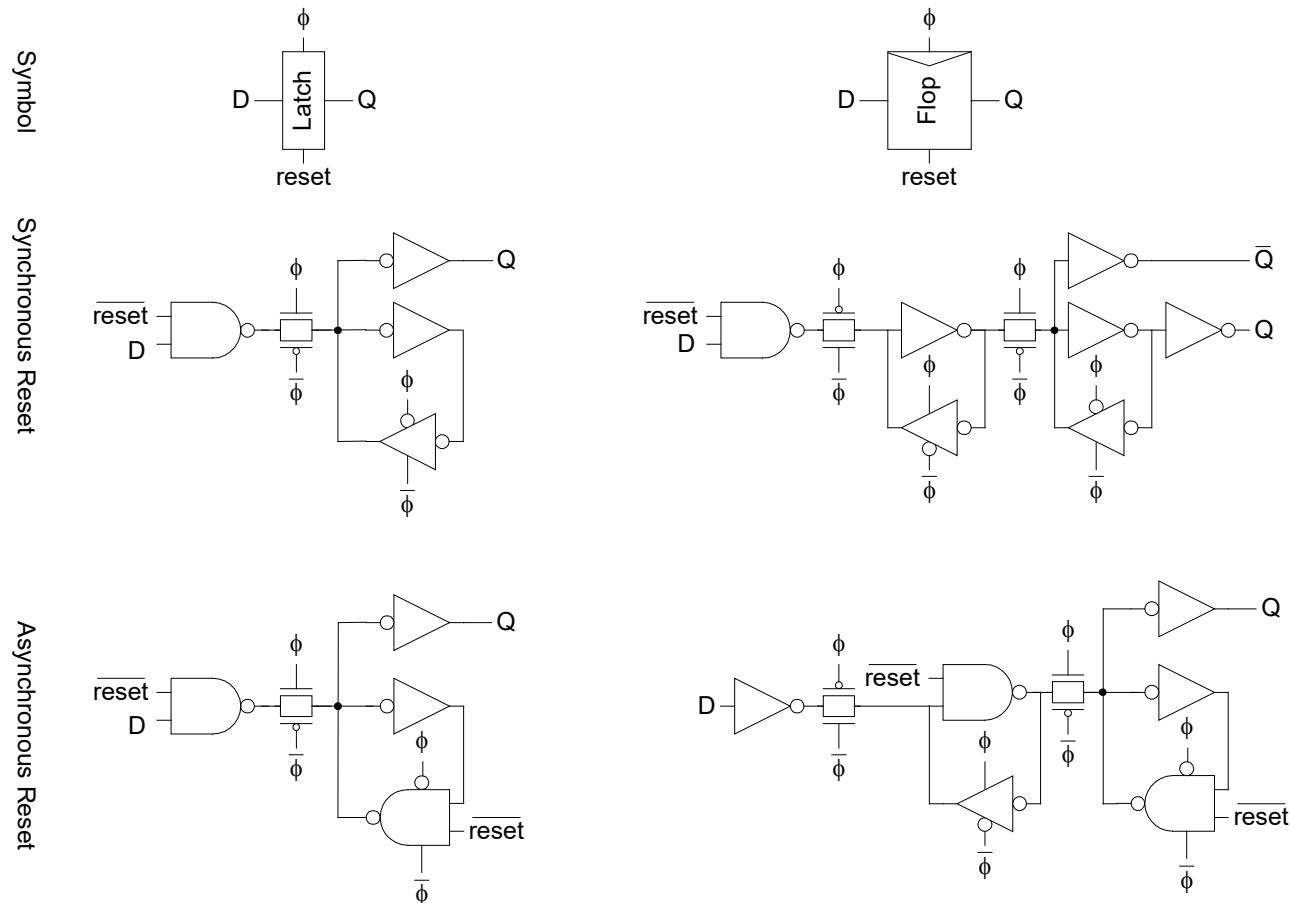- Force output low when reset asserted
- Synchronous vs. asynchronous




Set / Reset

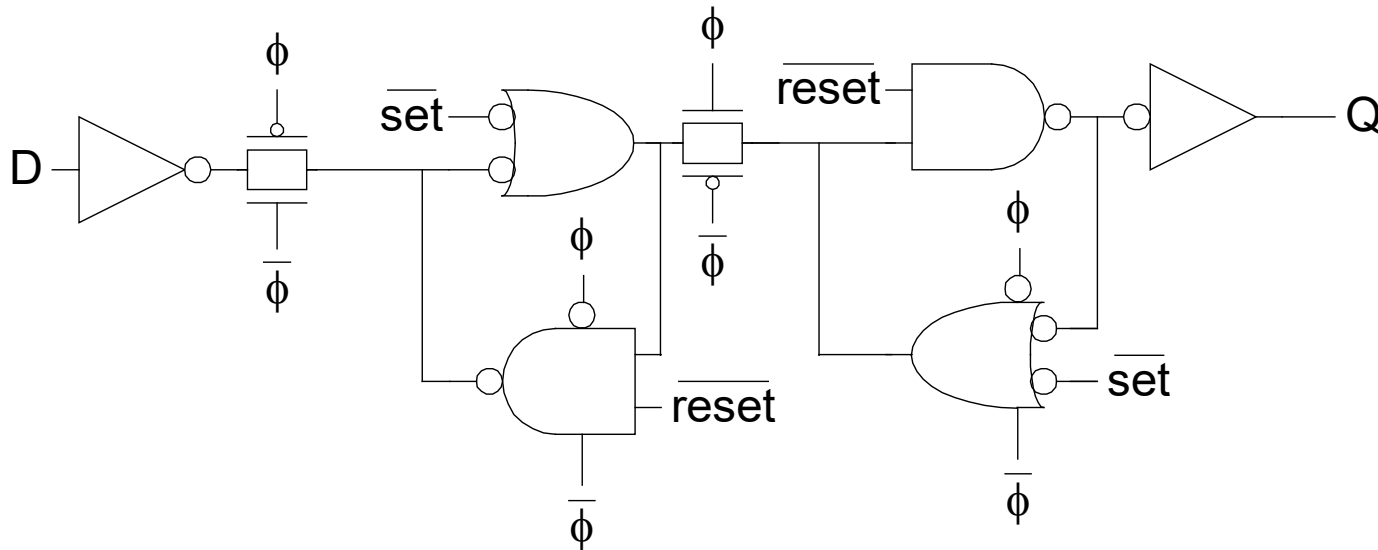- Set forces output high when enabled
- Flip-flop with asynchronous set and reset




Max-Delay: Flip-Flops

 - Maximum delay of the combination logic
- Avoid setup time violation




$$t_{pd} \leq T_c - \underbrace{\left(t_{setup} + t_{pcq} \right)}_{\text{sequencing overhead}}$$

Max Delay: 2-Phase Latches

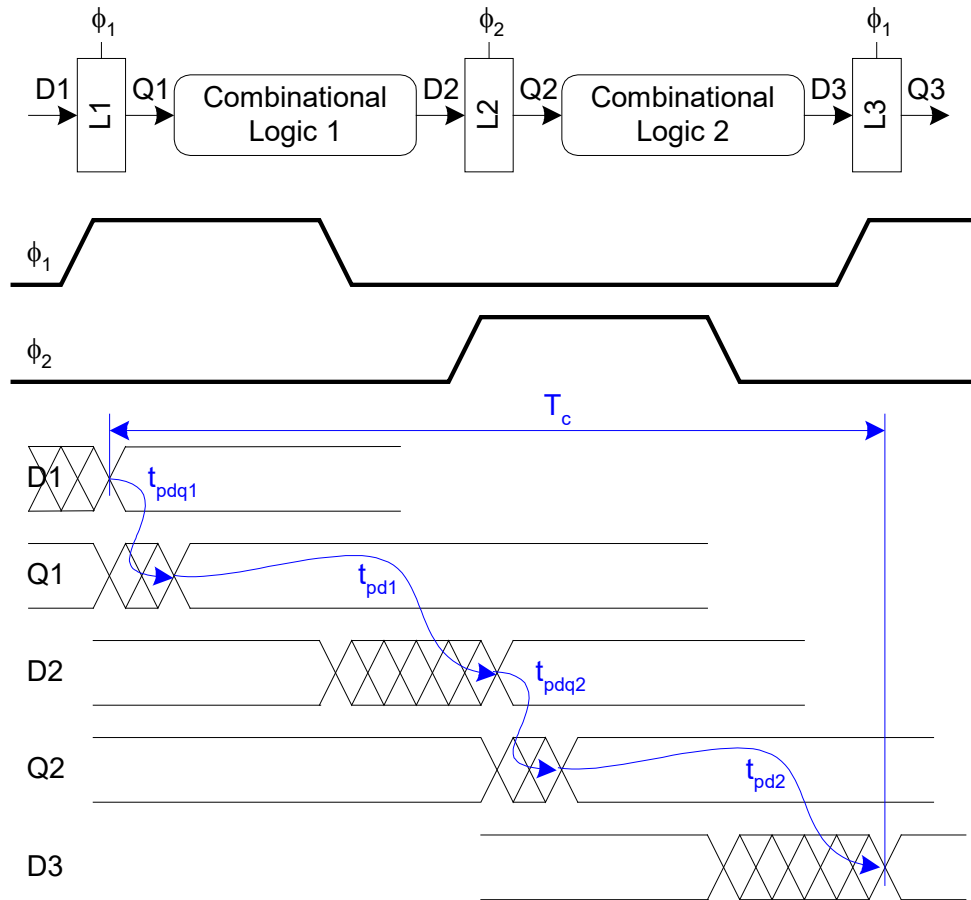

$$t_{pd} = t_{pd1} + t_{pd2} \leq T_c - \underbrace{(2t_{pdq})}_{\text{sequencing overhead}}$$


Max Delay: Pulsed Latches

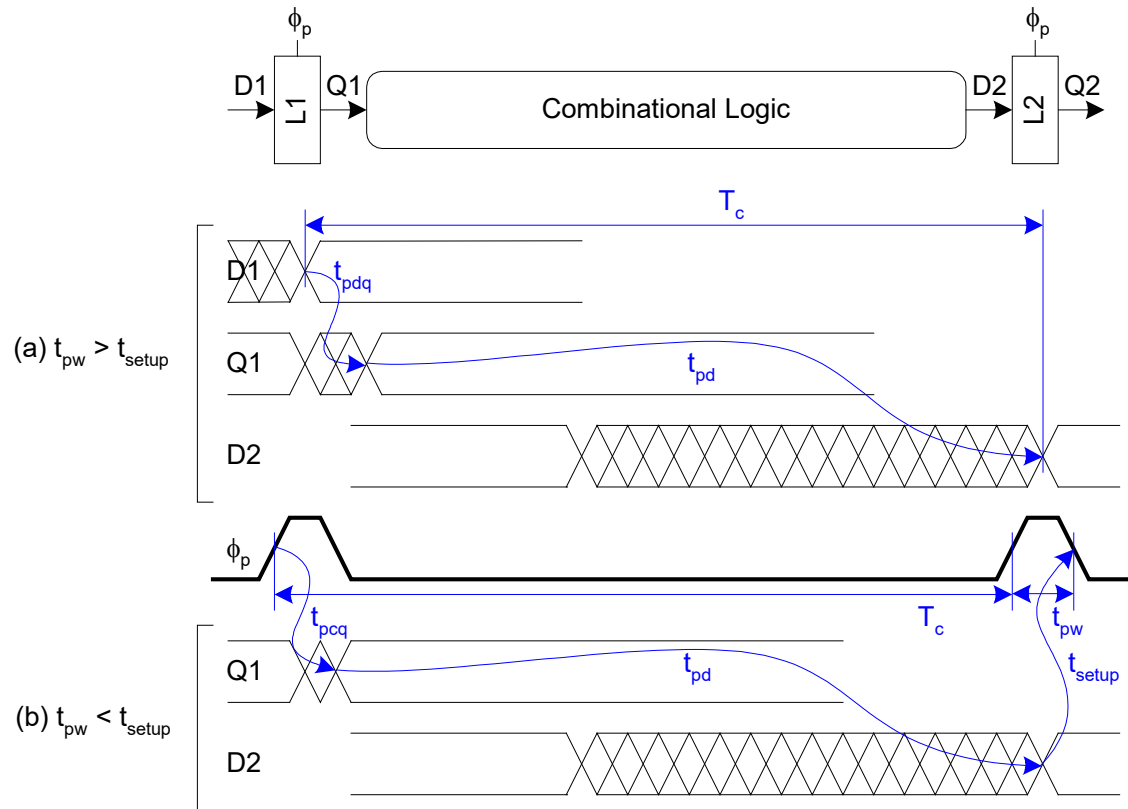

$$t_{pd} \leq T_c - \underbrace{\max(t_{pdq}, t_{pcq} + t_{setup} - t_{pw})}_{\text{sequencing overhead}}$$

Min-Delay: Flip-Flops

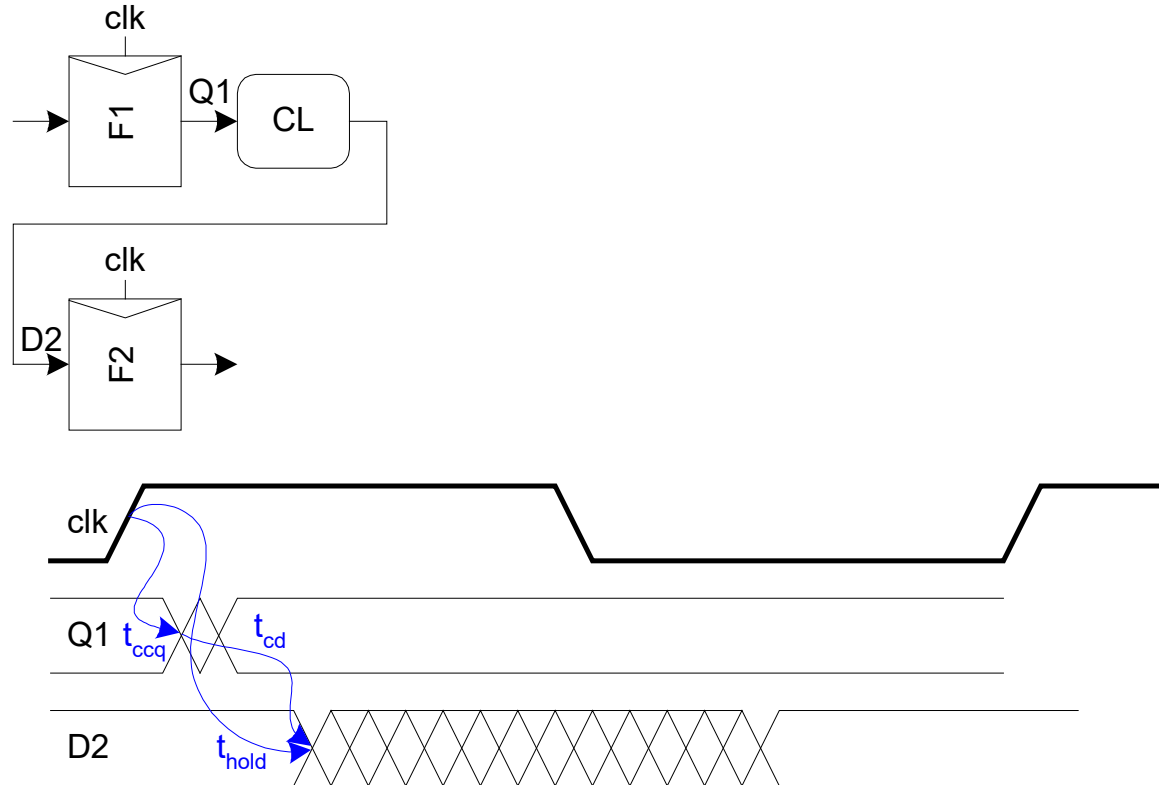
- Minimum delay of the combination logic
- Avoid hold-time violation




$$t_{cd} \geq t_{\text{hold}} - t_{ccq}$$

Min-Delay: 2-Phase Latches

 - Hold time reduced by nonoverlap
- Paradox: hold applies twice each cycle, vs. only once for flops.
- But a flop is made of two latches!



 
$$t_{cd1}, t_{cd2} \geq t_{\text{hold}} - t_{ccq} - t_{\text{nonoverlap}}$$



Min-Delay: Pulsed Latches


- Hold time increased by pulse width

 

Time Borrowing

- In a flop-based system:
 - ◆ Data launches on one rising edge
 - ◆ Must setup before next rising edge
 - ◆ If it arrives late, system fails
 - ◆ If it arrives early, time is wasted
 - ◆ Flops have hard edges
- In a latch-based system
 - ◆ Data can pass through latch while transparent
 - ◆ Long cycle of logic can borrow time into next
 - ◆ As long as each loop completes in one cycle

Time Borrowing Example

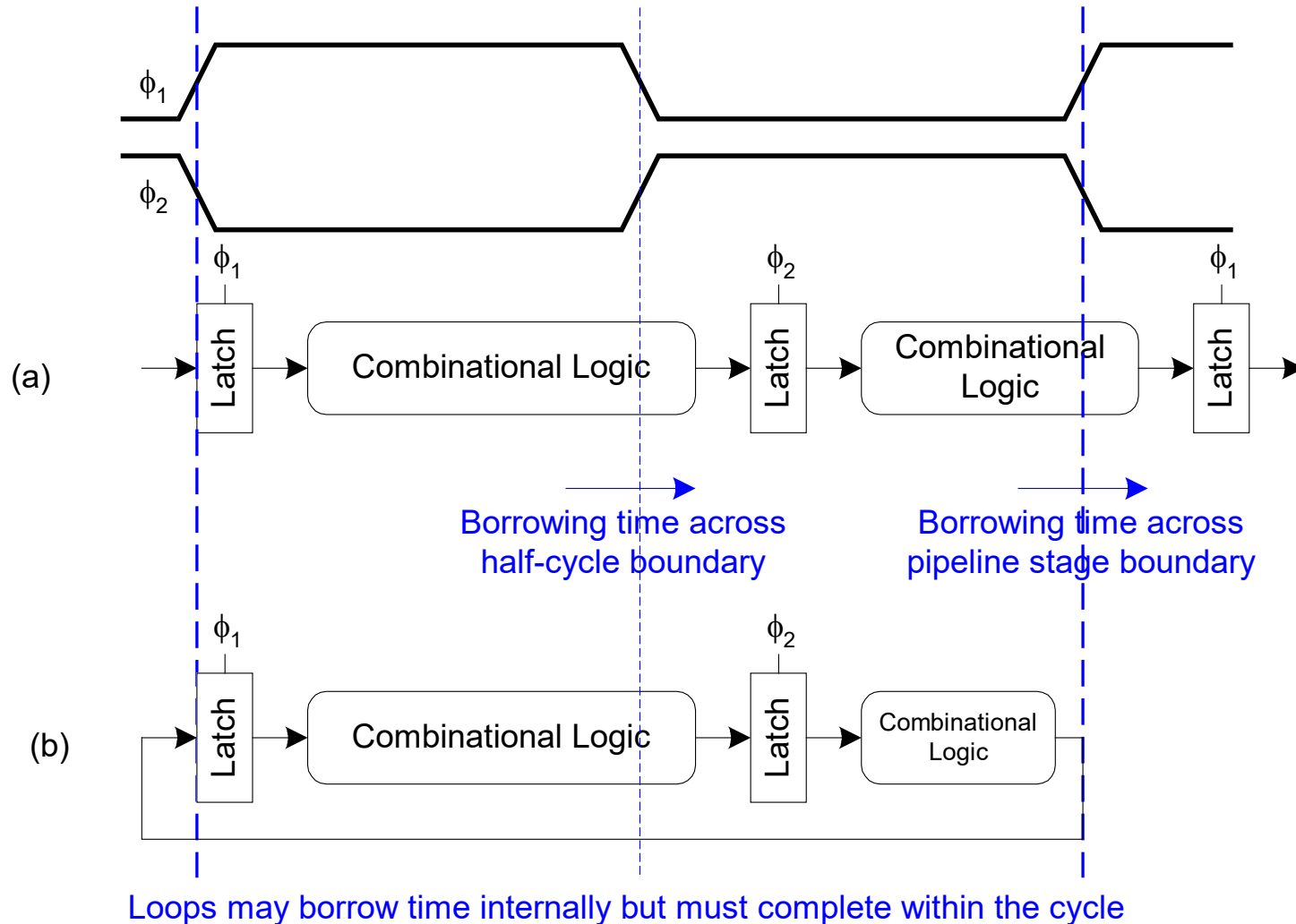


How Much Borrowing?

2-Phase Latches

$$t_{\text{borrow}} \leq \frac{T_c}{2} - (t_{\text{setup}} + t_{\text{nonoverlap}})$$

Pulsed Latches
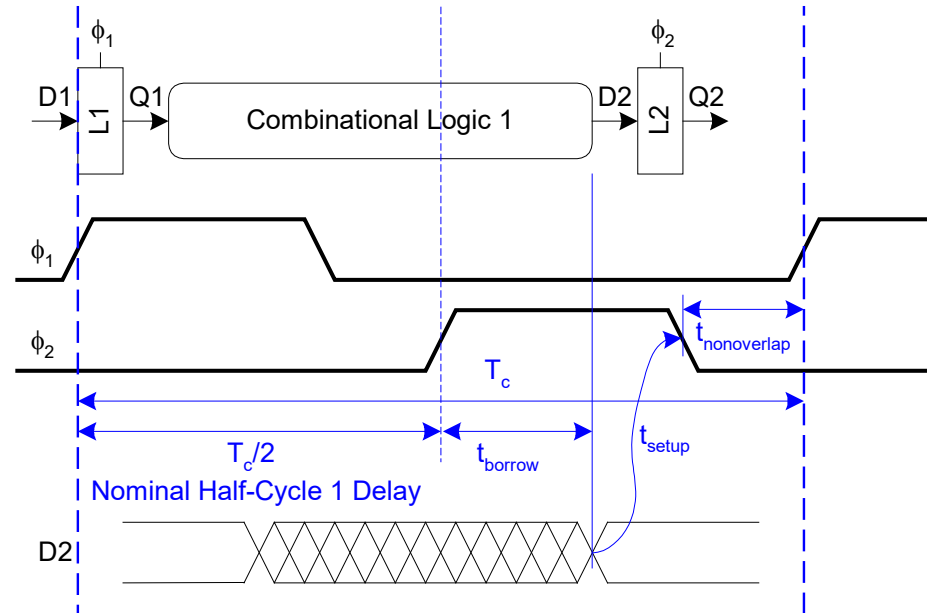
$$t_{\text{borrow}} \leq t_{pw} - t_{\text{setup}}$$



Time borrowing can be used to balance logic within a pipeline
But did not increase the amount of time available in a clock cycle



Clock Skew

- We have assumed zero clock skew
- Clocks really have uncertainty in arrival time
 - ◆ **Decreases** maximum propagation delay
 - ◆ Increases minimum contamination delay
 - ◆ Decreases time borrowing

Skew: Flip-Flops

$$t_{pd} \leq T_c - \underbrace{(t_{pcq} + t_{setup} + t_{skew})}_{\text{sequencing overhead}}$$
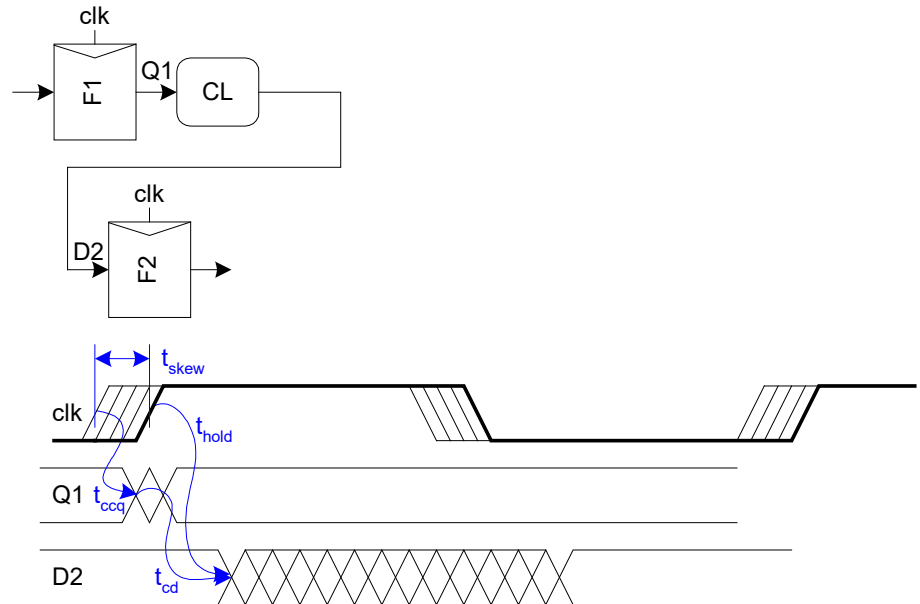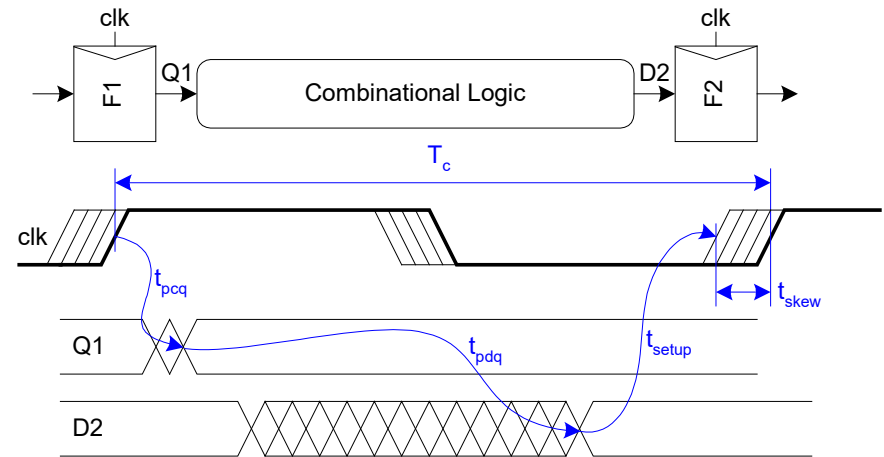
$$t_{cd} \geq t_{hold} - t_{ccq} + t_{skew}$$




Skew: Latches

2-Phase Latches

$$t_{pd} \leq T_c - \underbrace{(2t_{pdq})}_{\text{sequencing overhead}}$$

$$t_{cd1}, t_{cd2} \geq t_{\text{hold}} - t_{ccq} - t_{\text{nonoverlap}} + t_{\text{skew}}$$
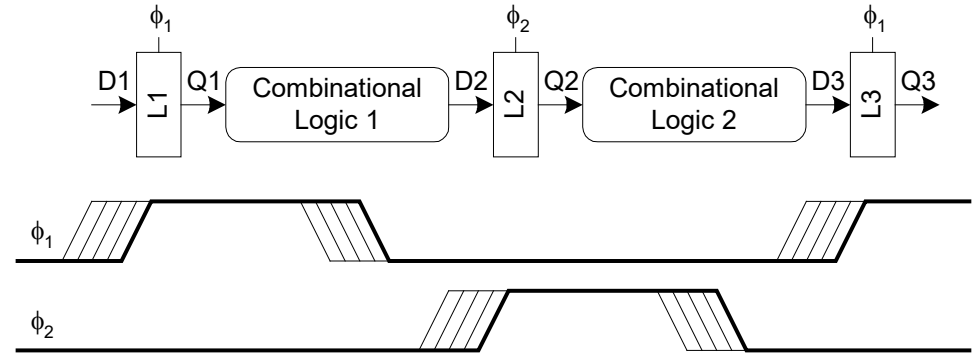
$$t_{\text{borrow}} \leq \frac{T_c}{2} - (t_{\text{setup}} + t_{\text{nonoverlap}} + t_{\text{skew}})$$



Pulsed Latches

$$t_{pd} \leq T_c - \underbrace{\max(t_{pdq}, t_{pcq} + t_{\text{setup}} - t_{pw} + t_{\text{skew}})}_{\text{sequencing overhead}}$$

$$t_{cd} \geq t_{\text{hold}} + t_{pw} - t_{ccq} + t_{\text{skew}}$$


$$t_{\text{borrow}} \leq t_{pw} - (t_{\text{setup}} + t_{\text{skew}})$$

Two-Phase Clocking

- If setup times are violated, reduce clock speed
- If hold times are violated, chip fails at any speed (Hold time fix after APR)
- An easy way to guarantee hold times is to use 2-phase latches with big nonoverlap times
- Call these clocks ϕ_1 , ϕ_2 (ph1, ph2)

Safe Flip-Flop

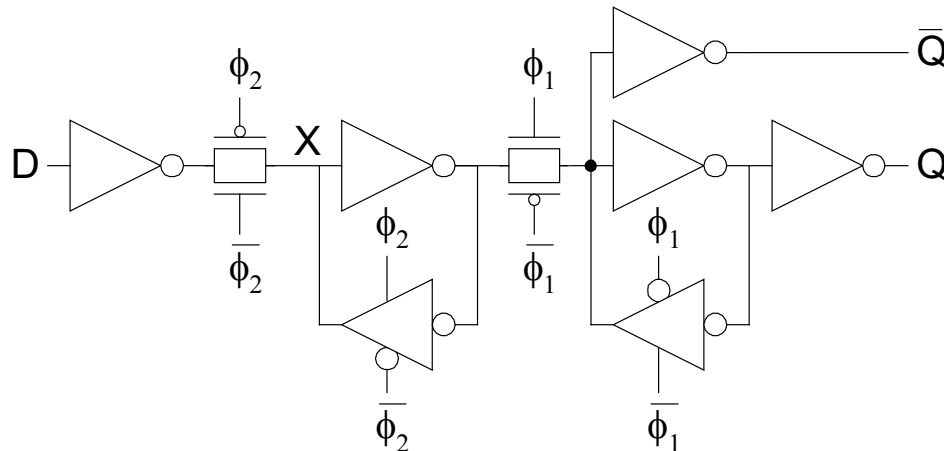
- Past years used flip-flop with nonoverlapping clocks
 - ◆ Slow – nonoverlap adds to setup time
 - ◆ But no hold times
- In industry, use a better timing analyzer
 - ◆ Add buffers to slow signals if hold time is at risk




Adaptive Sequencing

■ Designers include timing margin

 - ◆ Voltage
- ◆ Temperature
- ◆ Process variation
- ◆ Data dependency
- ◆ Tool inaccuracies



Double sampling

 

■ Alternative: run faster and check for near failures

- ◆ Idea introduced as “Razor”
 - Increase frequency until at the verge of error
 - Can reduce cycle time by ~30%

Summary

■ Flip-Flops:

- ◆ Very easy to use, supported by all tools

■ 2-Phase Transparent Latches:

- ◆ Lots of skew tolerance and time borrowing

■ Pulsed Latches:

- ◆ Fast, some skew tol & borrow, hold time risk

	Sequencing overhead ($T_c - t_{pd}$)	Minimum logic delay t_{cd}	Time borrowing t_{borrow}
Flip-Flops	$t_{pcq} + t_{setup} + t_{skew}$	$t_{hold} - t_{ccq} + t_{skew}$	0
Two-Phase Transparent Latches	$2t_{pdq}$	$t_{hold} - t_{ccq} - t_{nonoverlap} + t_{skew}$ in each half-cycle	$\frac{T_c}{2} - (t_{setup} + t_{nonoverlap} + t_{skew})$
Pulsed Latches	$\max(t_{pdq}, t_{pcq} + t_{setup} - t_{p\tau} + t_{skew})$	$t_{hold} - t_{ccq} + t_{p\tau} + t_{skew}$	$t_{p\tau} - (t_{setup} + t_{skew})$