

# Digital IC Design

## Lec 4-2:

### Combinational Circuits – Logic Families

黃柏蒼 Po-Tsang (Bug) Huang

bughuang@nycu.edu.tw

International College of Semiconductor Technology  
National Chiao Tung Yang Ming University

國立陽明交通大學

NATIONAL YANG MING CHIAO TUNG UNIVERSITY

# Logic Family

---

## ■ Static CMOS

- ◆ Complementary CMOS logic
- ◆ Pass Transistor Logic
- ◆ Ratioed circuits
  - Pseudo-nMOS Logic
- ◆ CVSL (Cascode voltage switch logic)

## ■ Dynamic Logic

# Review of Static CMOS



---

- Number of transistor of a logic is  $2N$  where  $N$  is number of inputs
- Capacitance loading of each input is the gate capacitance of one PMOS and one NMOS
- *No DC* current if there is no logic change
- *Rail-to-rail voltage swing, restoring and ratioless design*
- Most *robust* logic style and used in standard cell

# Tristates


- *Tristate buffer* produces Z when not enabled

EN	A	Y
0	0	Z
0	1	Z
1	0	0
1	1	1

  
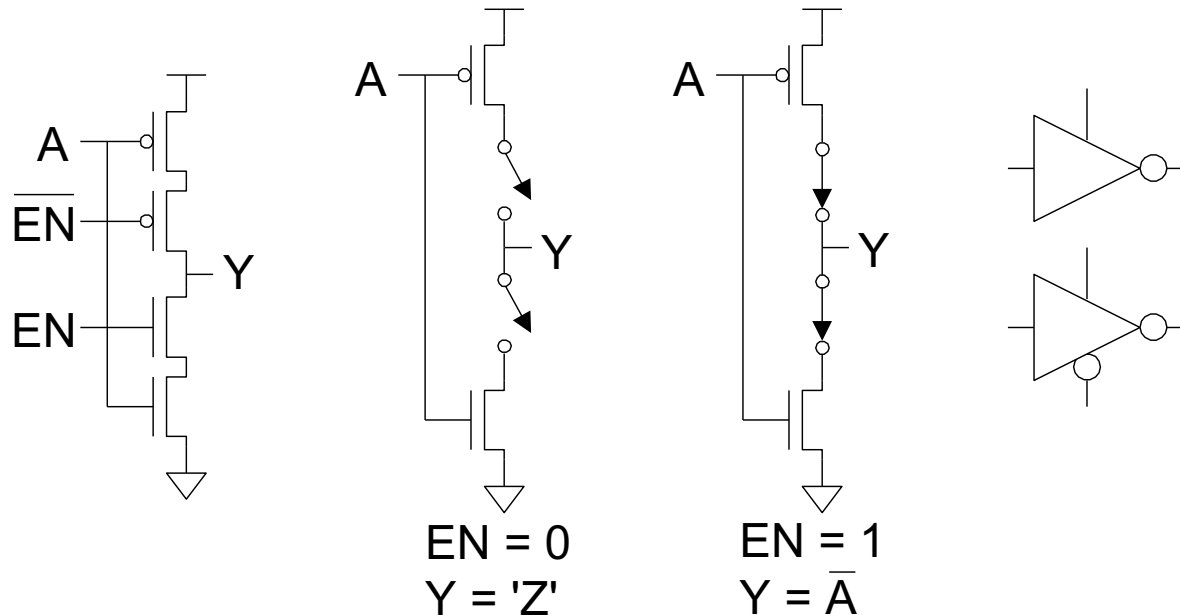
# Tristate Inverter

- Tristate inverter produces restored output
  - ◆ Violates conduction complement rule
  - ◆ Because we want a Z output




# Multiplexers

---

- 2:1 multiplexer chooses between two inputs

S	D1	D0	Y
0	X	0	0
0	X	1	1
1	0	X	0
1	1	X	1

 


# Inverting Mux

## ■ Inverting multiplexer










- ◆ Use compound AOI22
- ◆ Or pair of tristate inverters
- ◆ Essentially the same thing
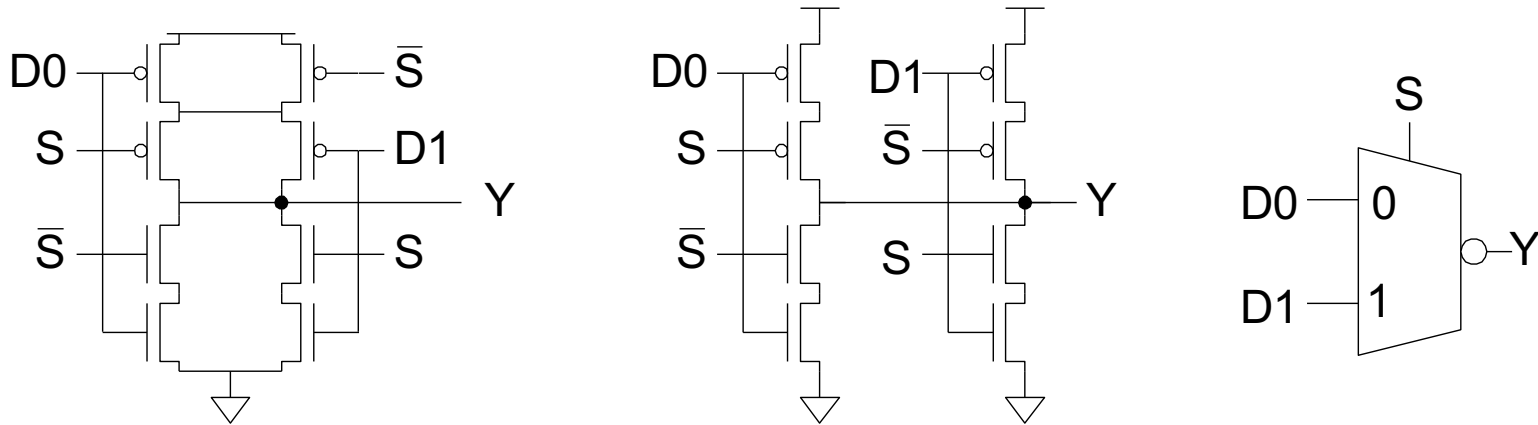
## ■ Noninverting multiplexer adds an inverter



# Pass Transistors


- Transistors can be used as switches

         



 
# NMOS Transistors in Series/Parallel

- Primary inputs drive both gate and source/drain terminals
- NMOS switch closes when the gate input is high



$X = Y$  if A and B

 


$X = Y$  if A or B


- Remember - NMOS transistors pass a **strong** 0 but a **weak** 1
 
# PMOS Transistors in Series/Parallel

- Primary inputs drive both gate and source/drain terminals
- PMOS switch closes when the gate input is low




 
$$X = Y \text{ if } \overline{A} \text{ and } \overline{B} = \overline{A + B}$$



$$X = Y \text{ if } \overline{A} \text{ or } \overline{B} = \overline{A \bullet B}$$



- Remember - PMOS transistors pass a **strong** 1 but a **weak** 0

# Pass Transistor (PT) Logic

  

- Gate is static – a low-impedance path exists to both supply rails under all circumstances
- $N$  transistors instead of  $2N$
- No static power consumption
- Ratioless
- Bidirectional (versus unidirectional)


# VTC of Pass Transistor AND Gate

  



- Pure PT logic is not **regenerative** - the signal gradually degrades after passing through a number of PTs (can fix with static CMOS inverter insertion)
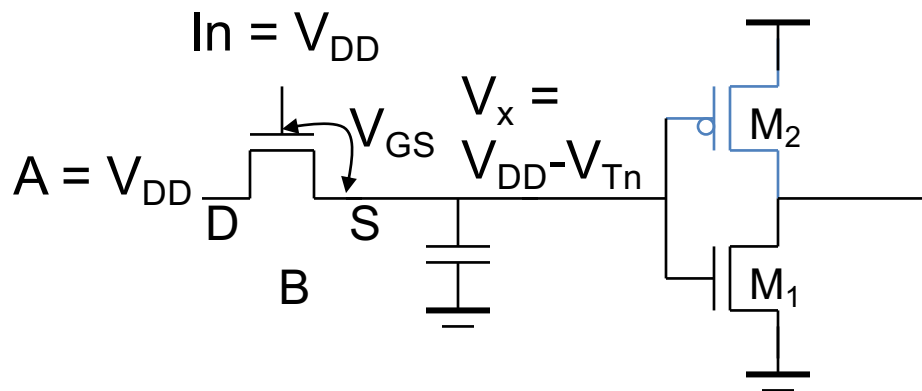
# NMOS Only PT Driving an Inverter

- $V_x$  does not pull up to  $V_{DD}$ , but  $V_{DD} - V_{Tn}$ 
  - ◆ Threshold voltage drop causes static power consumption ( $M_2$  may be weakly conducting forming a path from  $V_{DD}$  to GND)
  - ◆ Notice  $V_{Tn}$  increases for pass transistor due to **body effect** ( $V_{SB}$ )



  
# Voltage Swing of PT Driving an Inverter



- **Body effect** – large  $V_{SB}$  at x - when pulling high (B is tied to GND and S charged up close to  $V_{DD}$ )
- So the voltage drop is even worse

$$V_x = V_{DD} - (V_{Tn0} + \gamma(\sqrt{(|2\phi_f| + V_x)} - \sqrt{|2\phi_f|}))$$

# Cascaded NMOS Only PTs

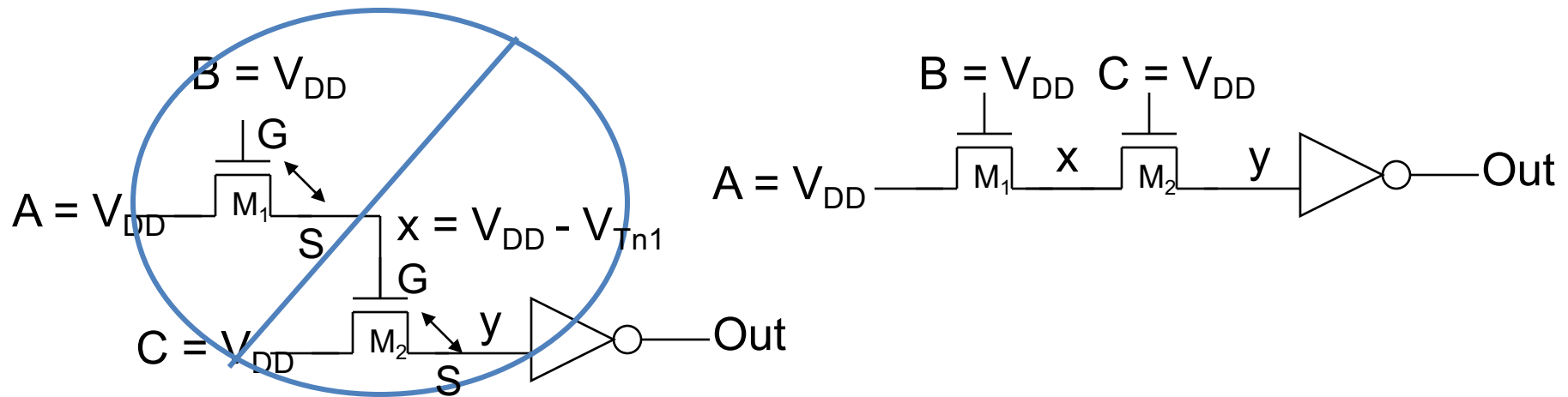


Swing on  $y = V_{DD} - V_{Tn1} - V_{Tn2}$

Swing on  $y = V_{DD} - V_{Tn1}$

- Pass transistor gates should **never** be cascaded as on the left
- Logic on the right suffers from static power dissipation and reduced noise margins

# Solution 1: Level Restorer

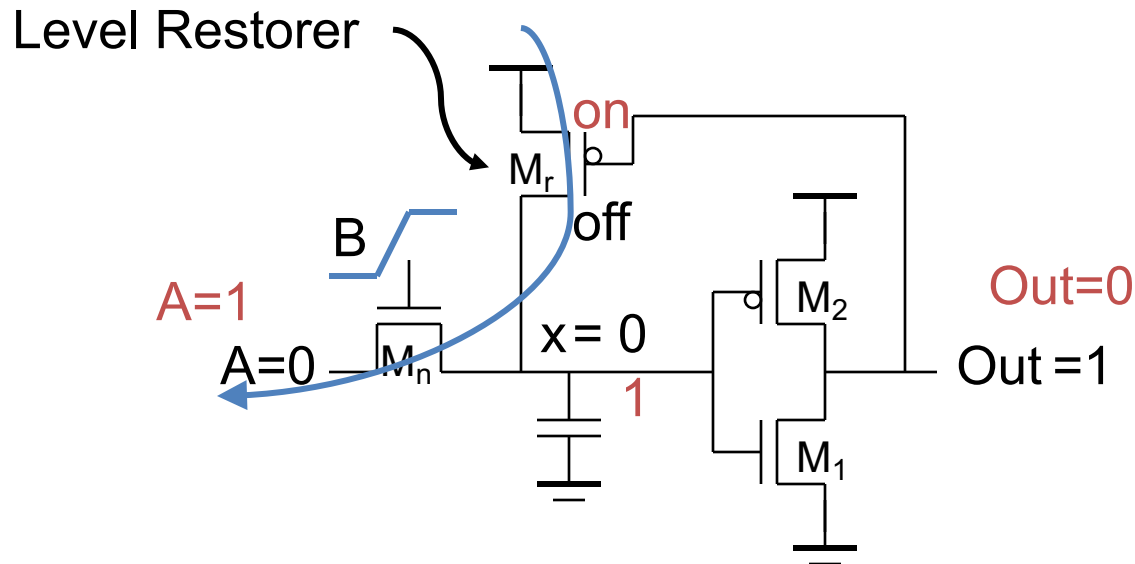


- Full swing on  $x$  (due to Level Restorer) so no static power consumption by inverter
- No static backward current path through Level Restorer and PT since Restorer is only active when  $A$  is high

For correct operation  $M_r$  must be sized correctly (ratioed)


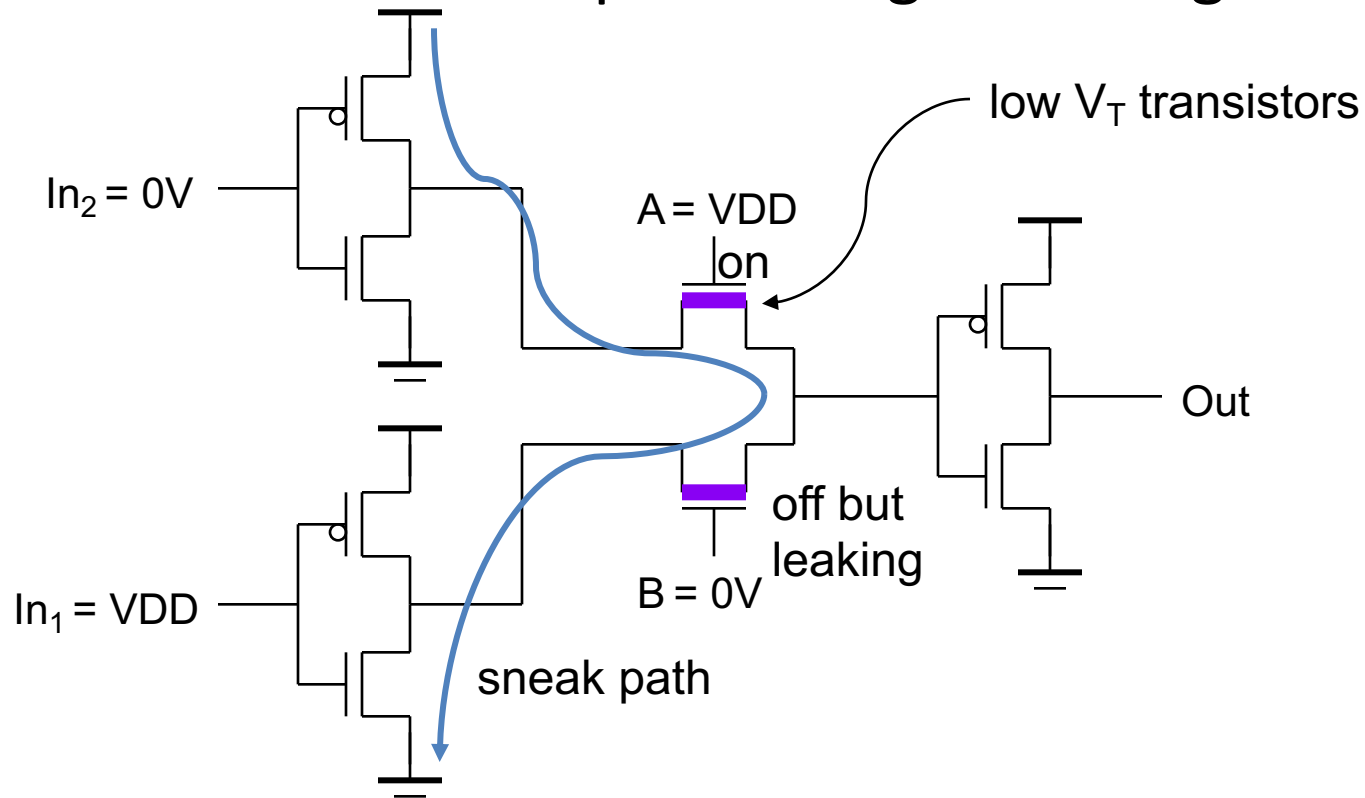
## Solution 2: Multiple $V_T$ Transistors





- Technology solution: Use (near) zero  $V_T$  devices for the NMOS PTs to eliminate *most* of the threshold drop (body effect still in force preventing full swing to  $V_{DD}$ )



- Impacts static power consumption due to subthreshold currents flowing through the PTs (even if  $V_{GS}$  is below  $V_T$ )

# Solution 3: Transmission Gates (TGs)


- Most widely used solution

    


- Full swing *bidirectional* switch controlled by the gate signal  $C$ ,  $A = B$  if  $C = 1$
 
# Transmission Gates


- Pass transistors produce degraded outputs
- *Transmission gates* pass both 0 and 1 well



$g = 0, gb = 1$

 

$g = 1, gb = 0$

 

Input




Output

$g = 1, gb = 0$


$0 \rightarrow \text{strong } 0$

$g = 1, gb = 0$


$1 \rightarrow \text{strong } 1$

   



# TG Multiplexer

 

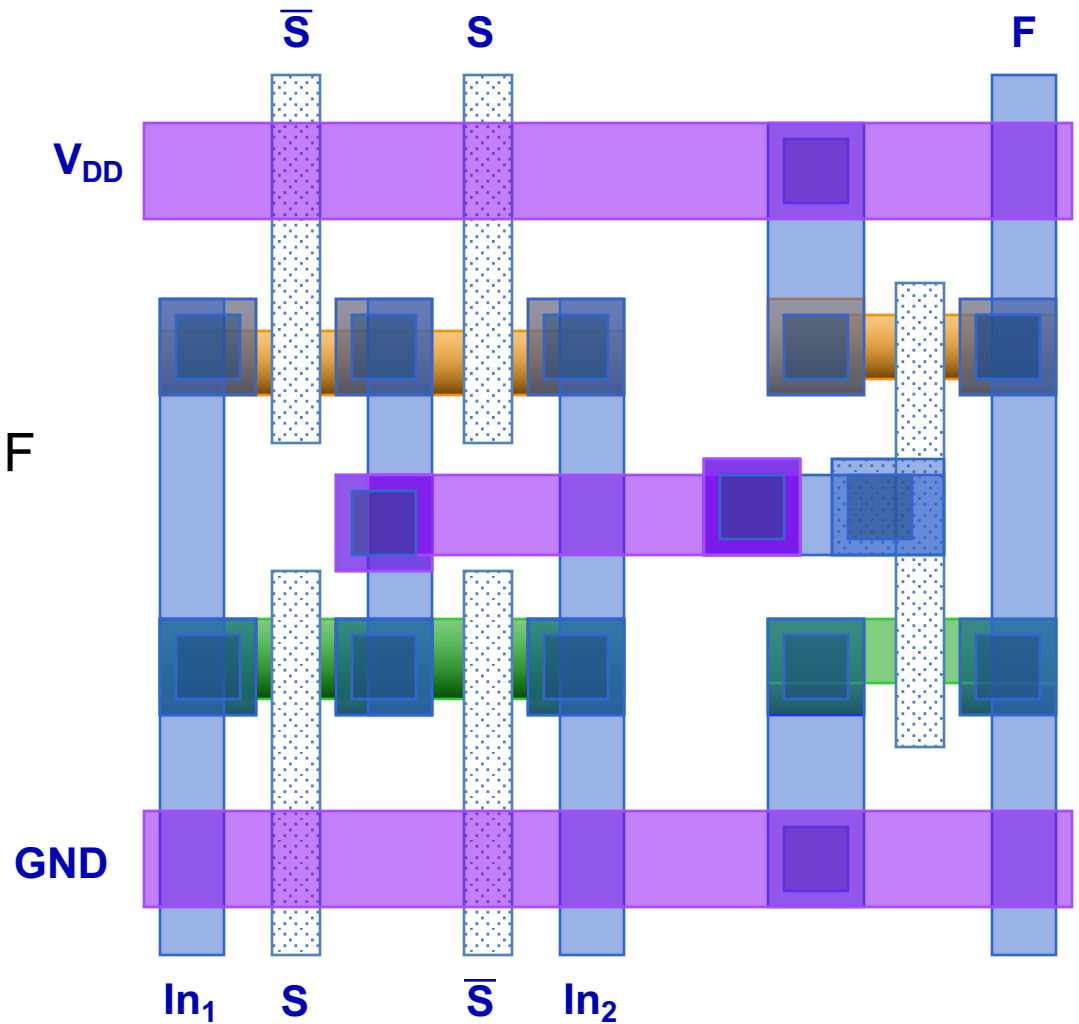
$$F = \overline{(In_1 \bullet S + In_2 \bullet \overline{S})}$$





# TG-Based XOR function

  

# TG Full Adder


 


# Differential TG Logic (DPL)

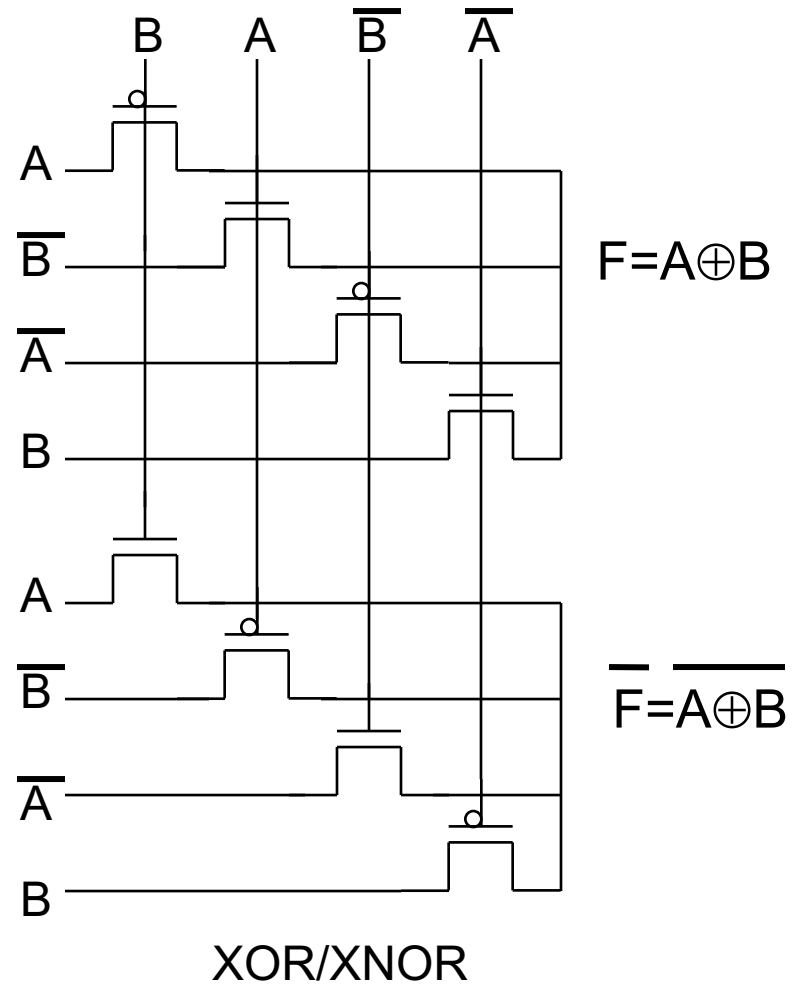
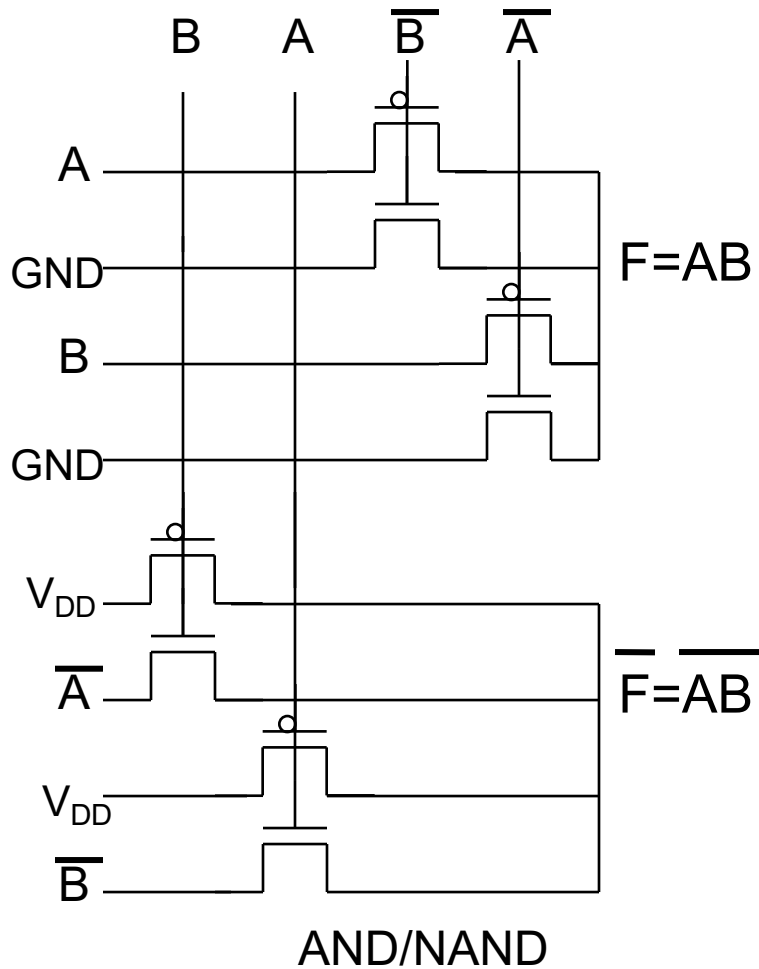


# Double Pass-Transistor Logic (DPL)

AND/NAND



 
 


XOR/XNOR

  




    
# Differential/Complemental PT Logic (CPL)



# CPL NAND2/NOR2 gates

 


CPL NAND2

 

CPL NOR2
 
# CPL XOR and Sum

- NMOS logic network ( $V_T$  drop)
- Fast
- Efficient implementation of arithmetic




# CPL Properties


---

- **Differential** so complementary data inputs and outputs are always available (so don't need extra inverters)
- Still static, since the output defining nodes are always tied to  $V_{DD}$  or GND through a low resistance path
- Design is **modular**; all gates use the same topology, only the inputs are permuted.
- Simple XOR makes it attractive for structures like **adders**
- Fast (assuming number of transistors in series is small)
- Additional routing overhead for complementary signals
- Still have static power dissipation problems


# CPL Full Adder

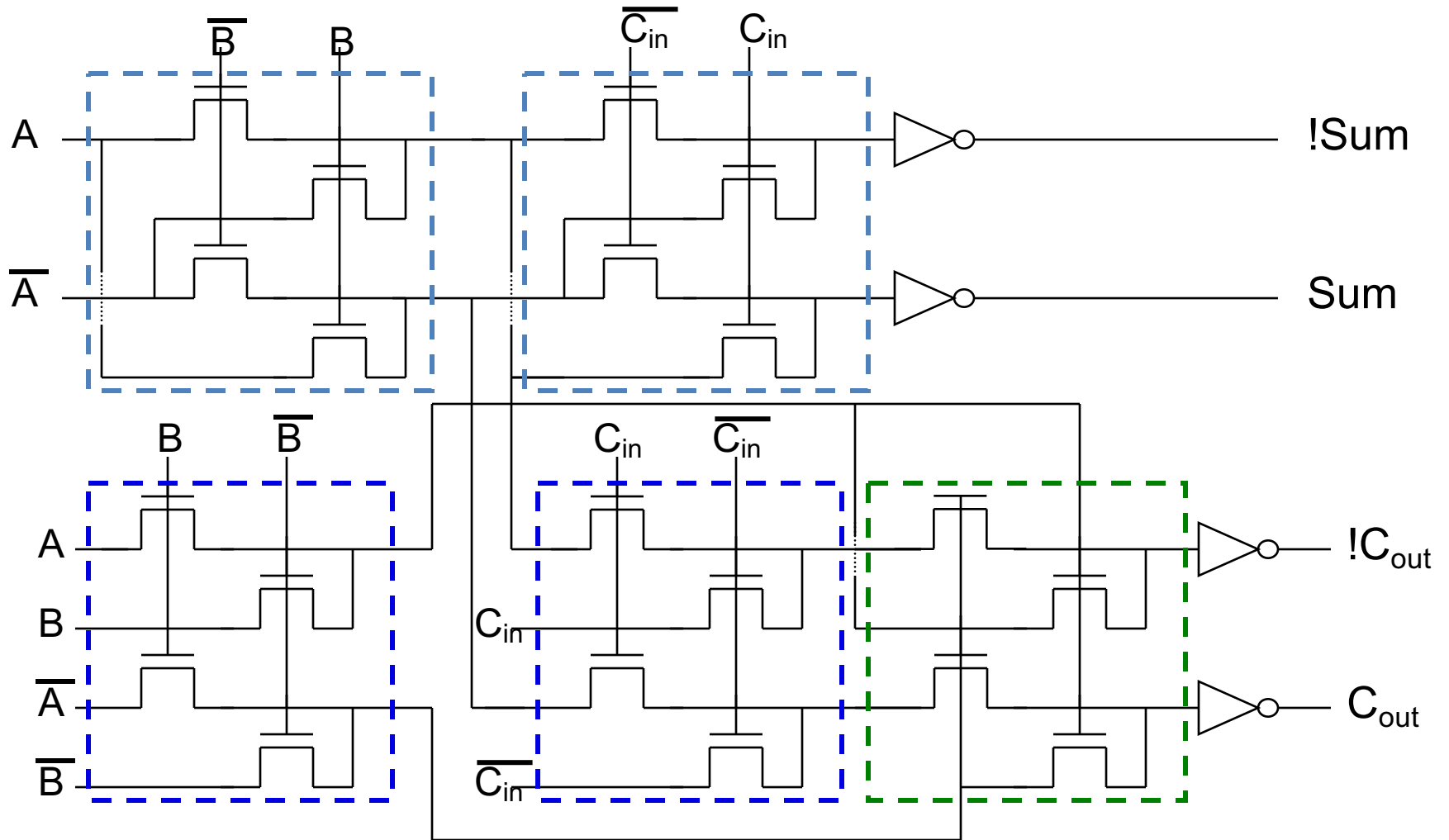

# Circuit Diagram of a CPL full adder

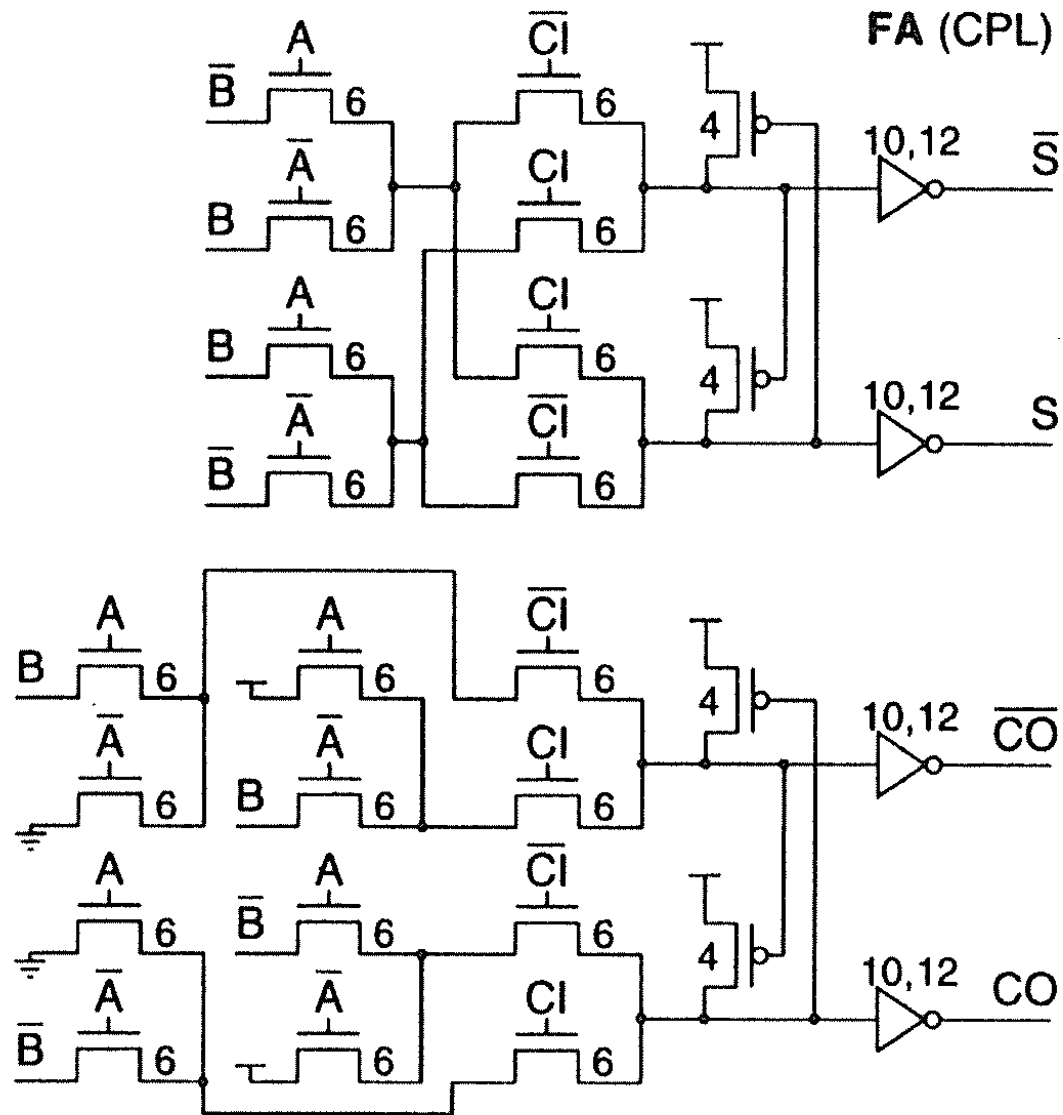



# Ratioed Logic

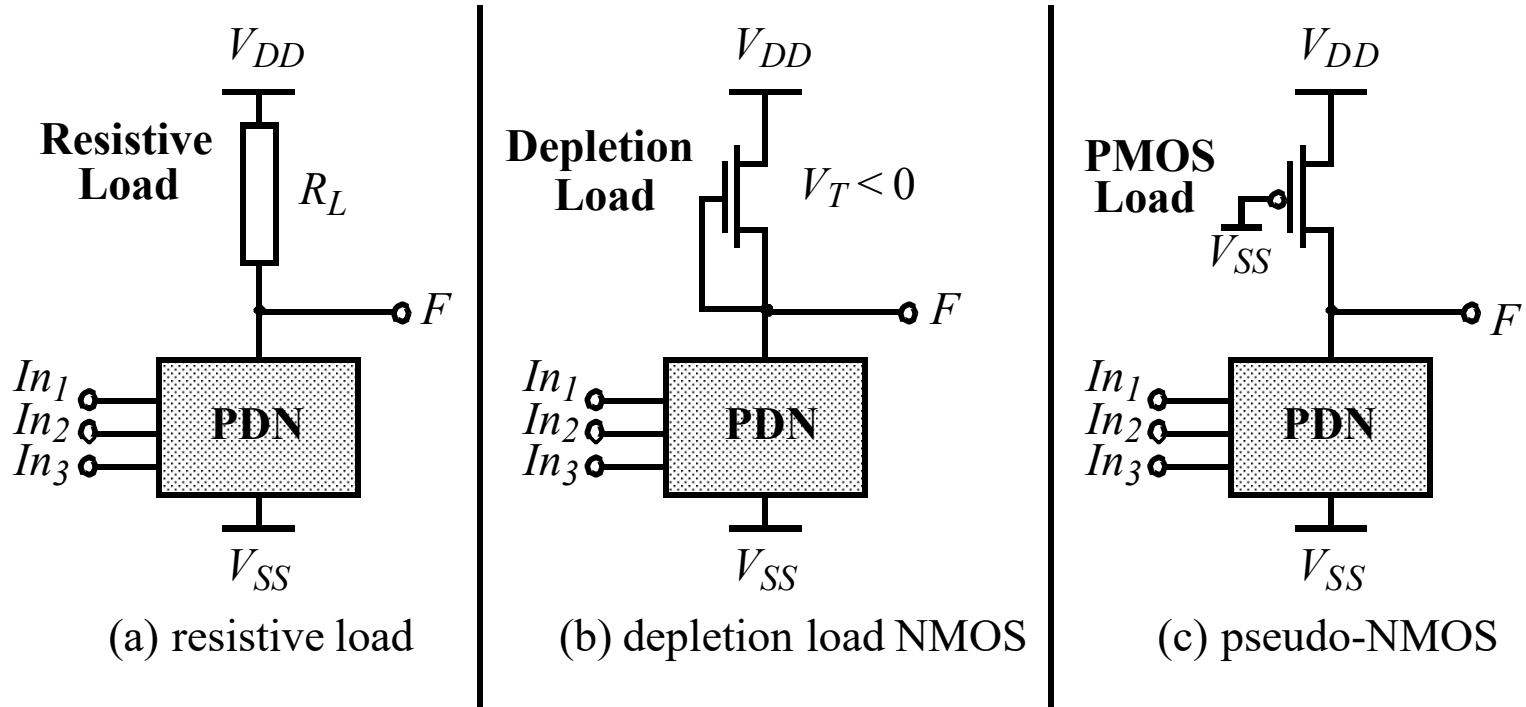

**Goal: to reduce the number of devices over complementary CMOS**
  
# Pseudo-nMOS

- In the old days, nMOS processes had no pMOS
  - ◆ Instead, use pull-up transistor that is always ON
- In CMOS, use a pMOS that is always ON
  - ◆ *Ratio* issue
  - ◆ Make pMOS about  $\frac{1}{4}$  effective strength of pulldown network




**pMOS fights nMOS**


 
# Pseudo-nMOS Power




---

- Pseudo-nMOS draws power whenever  $Y = 0$ 
  - ◆ Called static power  $P = I_{DD}V_{DD}$
  - ◆ A few mA / gate \* 1M gates would be a problem
  - ◆ Explains why nMOS went extinct
- Use pseudo-nMOS sparingly for wide NORs
- Turn off pMOS when not in use




# Different Restoration Schemes
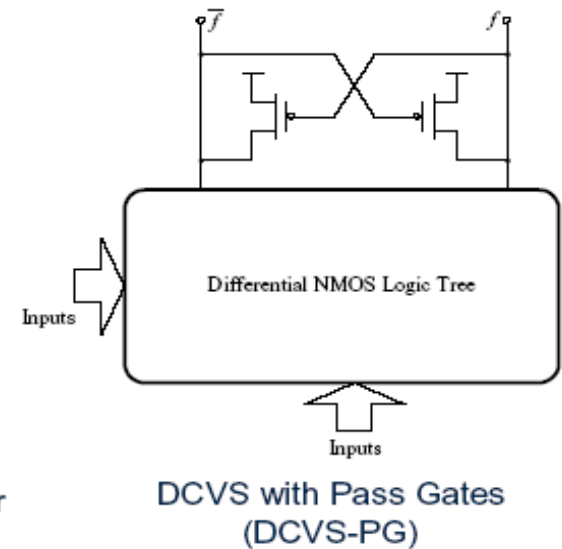 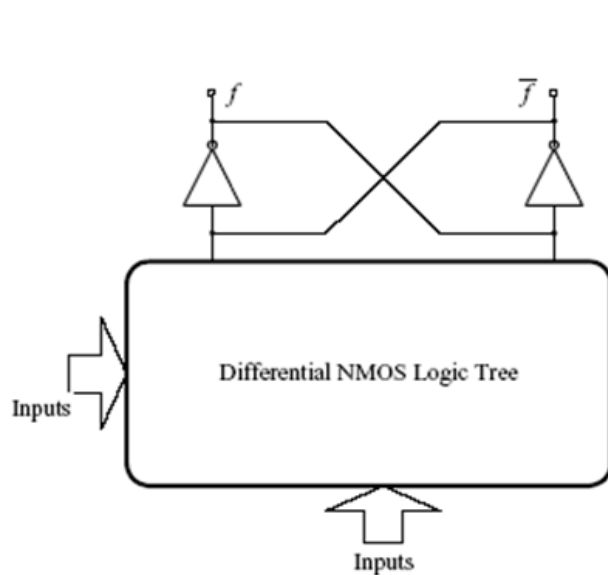
## ■ Swing-restored pass-transistor logic



 
# Differential Cascode Voltage Switch Logic

- Differential Cascode Voltage Switch (DCVS)
  - ◆ Differential Level Restoring
  - ◆ Complement outputs


 
# DCVS Logic

- PDN1 and PDN2 are mutually exclusive
  - ◆ No DC power dissipation
  - ◆ Regenerative action sets PMOS latch to static outputs Q and Q' of full VDD and GND logic level
  - ◆ NMOS rich => increasing current and reducing load capacitance



# DCVS Concept

---

$$Y(A,B,C,D,E,E,F,G) = \overline{G}\overline{A}\overline{F} + \overline{G}\overline{B}\overline{D}\overline{E} + \overline{G}\overline{B}\overline{C}\overline{F} + \overline{G}\overline{B}\overline{C}\overline{E} + \overline{G}\overline{C}\overline{D}\overline{E}$$

◆ Using complementary static logic : 38 transistor


$$Y(A,B,C,D,E,E,F,G) = \overline{G}(\overline{A}\overline{F} + \overline{B}\overline{D}\overline{E} + \overline{C}(\overline{B}\overline{F} + \overline{E}(\overline{B} + \overline{D})))$$

◆ Using complementary static logic with cascade tree : 24 transistor

■ The cascade tree can be used in any logic type : try to extract as many common subexpression as possible.
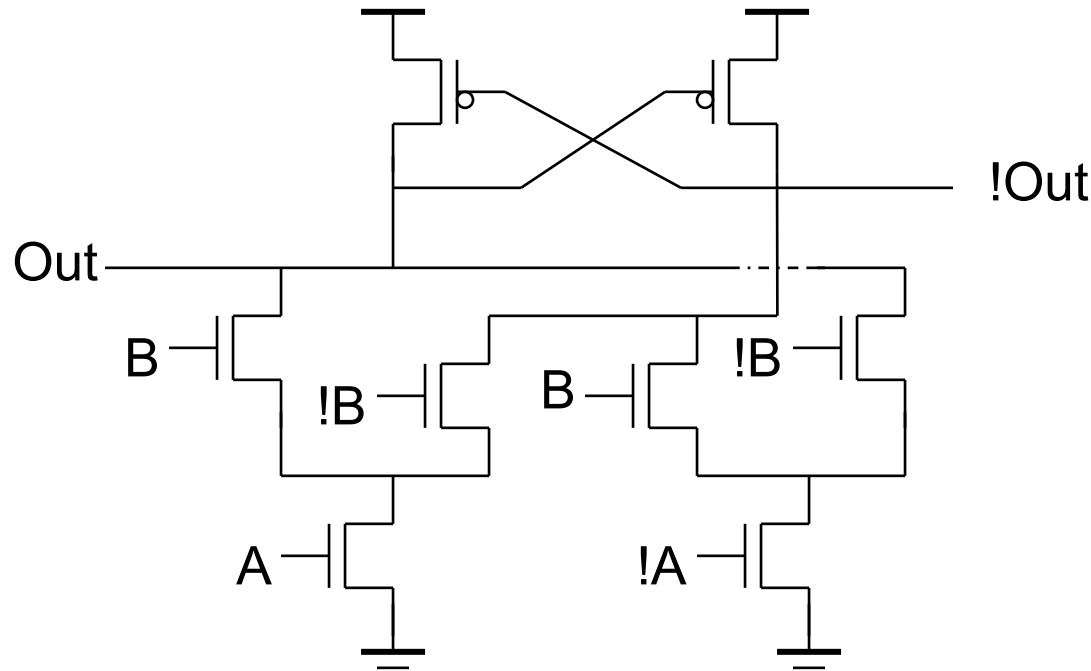
# DCVS Example

- XOR-XNOR gate in only 8 transistors as opposed to 10 in complement static CMOS



# DCVS+CPL XOR gate

## ■ DCVS+CPL

◆ or called DCVS + pass gate (DCVSPG)

